

Analog filter

Date 6-Oct
Page



Reference book :- Analog filters design
by M.E.

passive (R, L & C)

- if we design the filter by using op-amp, $\xrightarrow{\text{transistor}}$ Active filter
- if we design the filter by using passive components as R, L & C $\xrightarrow{\text{"Passive filter"}}$

Advantage of Active over Passive filters

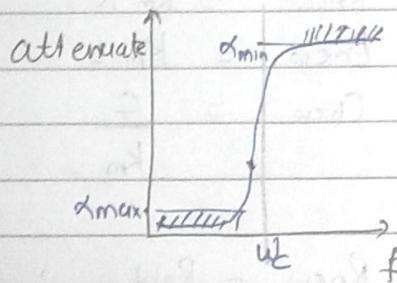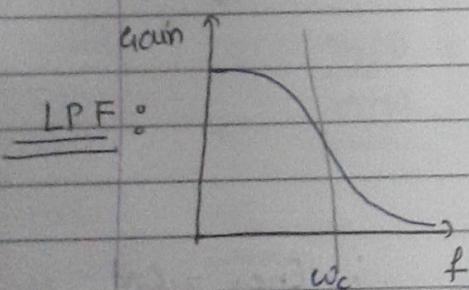- After the cut off freq. signal is attenuate in passive filters
- Gain is change as per our requirement in Active.
- Gain & attenuation are inversely proportional.
in inverting amp or inverting amp configuration is used because gain is change as per requirement. $\text{Gain} > 1 \& G < 1$.



$\alpha > \alpha_{\max} \rightarrow$ stop band

(i) $\alpha > \alpha_{\min}$ or ↓

(ii) $\alpha \leq \alpha_{\min}$ (Gain low
att. High)

$\alpha > \alpha_{\min} \rightarrow$ passband



(Gain High
att. Low)

$$\Rightarrow \alpha_{\text{stop}} > \alpha_{\min} \quad \text{or} \quad \alpha_{\text{stop}} < \alpha_{\min}$$

Stopband Gain = 0.5



$$\alpha_{\text{stop}} = 110.5 = 2$$

Ex: Design the LPF, f' Design specification

sol:

channel
spec

specification \rightarrow

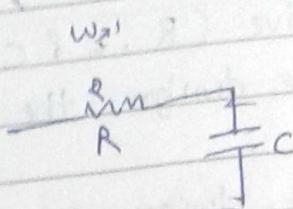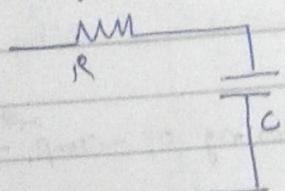

$$\Rightarrow R_{\text{new}} = K_m R \quad | \frac{x_L}{wL} = \frac{x_L}{w' L'} \\ L_{\text{new}} = K_m \cdot L \\ C_{\text{new}} = \frac{C}{K_m}$$

Magnitude Scaling R, L & C :

$K_m \rightarrow$ Scaling factor

$$|x_L| = wL \\ |x_C| = \frac{1}{wC}$$

- $R_{\text{new}} = K_m R$
- $L_{\text{new}} = K_m L$
- $C_{\text{new}} = \frac{C}{K_m}$

- $R_{\text{new}} = R_{\text{old}} ; \quad L_{\text{new}} = \frac{L_{\text{old}}}{K_F} ; \quad C_{\text{new}} = \frac{C_{\text{old}}}{K_F}$

$$X_L = wL \\ = w \left(K_F \cdot \frac{L}{K_F} \right) \\ X_C = \frac{1}{wK_F (C/K_F)}$$


- $R = K_m R_{\text{old}} ; \quad C = \frac{C_{\text{old}}}{K_m K_F} ; \quad L = \frac{K_m L_{\text{old}}}{K_F}$

When we designed filter then we take the values of R, L, C which are not practically available, so by using scaling we can used that filter.

— and also by using the frequency scaling we can change the pass band & stop band frequencies as per the already designed of ^{LPF} filter.

filter Design:

① Design Parameter Q & ω_0

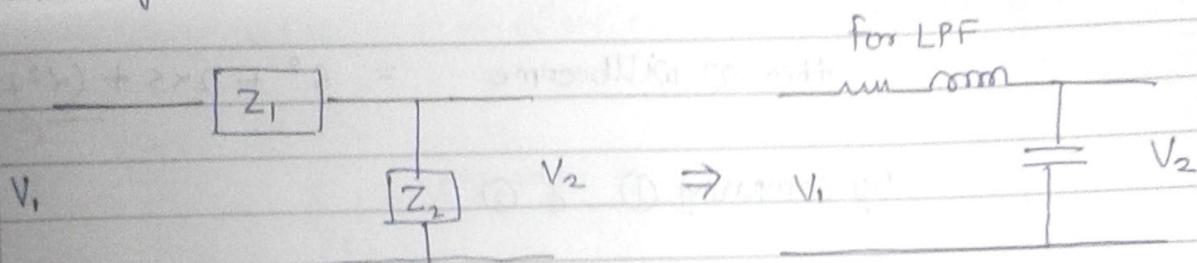

When High Freq. then cap. passes the signal.

$$\begin{aligned}
 \frac{V_2(s)}{V_1(s)} &= \frac{Z_2}{Z_1 + Z_2} \\
 &= \frac{1/\omega C}{1/\omega C + R + LC} = \frac{1/cs}{1/cs + R + LC} \\
 &= \frac{1}{1 + RCS + LCS^2}
 \end{aligned}$$

$$T(s) = \frac{1/LC}{s^2 + (R/L)s + 1/LC}$$

if $R=0 \rightarrow$ that means less loss coil is there

$$\frac{s^2 + 1}{LC} = 0$$

resonance freq. $\omega_0 = \frac{1}{\sqrt{LC}}$

; resonance freq. $X_L = X_C$

Quality factor $Q = \frac{\omega_0 L}{R} \approx \frac{1}{R\sqrt{LC}}$

$$T(s) = \frac{\omega_0^2}{s^2 + \left(\frac{\omega_0}{\alpha}\right)s + \omega_0^2} \quad (1)$$

If this equation having two complex conjugate pairs of roots then

$$-\alpha \pm j\beta$$

$$\text{then eqn will become } = s^2 + 2s + (\alpha^2 + \beta^2) \quad (2)$$

By comparing (1) & (2)


$$\alpha = \frac{\omega_0}{2\alpha}$$

$$\alpha^2 + \beta^2 = \omega_0^2$$

$$\beta^2 = \omega_0^2 - \frac{\omega_0^2}{4\alpha^2}$$

$$\beta^2 = \omega_0^2 \left(1 - \frac{1}{4\alpha^2}\right)$$
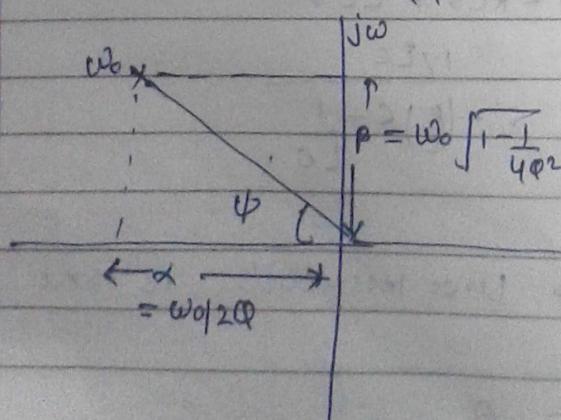
$$\text{so, } \beta = \frac{\omega_0 \sqrt{4\alpha^2 - 1}}{2\alpha} = \omega_0 \sqrt{1 - \frac{1}{4\alpha^2}}$$



$$\psi = \tan^{-1}(\beta/\alpha)$$

$$= \tan^{-1} \left[\sqrt{4\alpha^2 - 1} \right]$$

$$\cos \phi = \frac{\omega_0 / 2\alpha}{\omega_0}$$

$$\phi = \cos^{-1} \left(\frac{1}{2\alpha} \right)$$

$$T(s) = \pm H \omega_0^2$$

$$s^2 + (\omega_0/\alpha)s + \omega_0^2$$

$\omega_0 = 1$, inverting amp or opamp is used so $H = -H$

$$T(s) = \frac{-H}{s^2 + s/\alpha + 1} = \frac{V_2(s)}{V_1(s)}$$


$$-V_1 H = V_2 \left[s \left(s + \frac{1}{\alpha} \right) + 1 \right]$$

$$V_2 \left[1 + \frac{1}{s(s + 1/\alpha)} \right] = -\frac{V_1 H}{s(s + 1/\alpha)}$$

$$V_2 + \frac{V_2}{s(s + 1/\alpha)} = \frac{-V_1 H}{s(s + 1/\alpha)}$$

$$V_2 = \frac{-H V_1}{s(s + 1/\alpha)} - \frac{V_2}{s(s + 1/\alpha)}$$
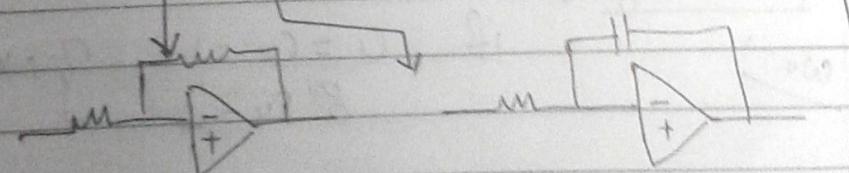
$$V_2 = (-1) \left(\frac{-1}{s} \right) \left[-\frac{1}{(s + 1/\alpha)} V_2 + \frac{-H}{(s + 1/\alpha)} V_1 \right]$$



$$\frac{R \cdot 1/C s}{1/C s + R} = \frac{R}{R C s + 1} = \frac{R_{FBG}}{R_{FBG}}$$


$$= \frac{1/C}{s + 1/R C}$$


$$\text{so; } C = 1$$

$$R = 1 \times \infty$$

$$\& R_1 = 1$$

$$R_2 = 1/H$$

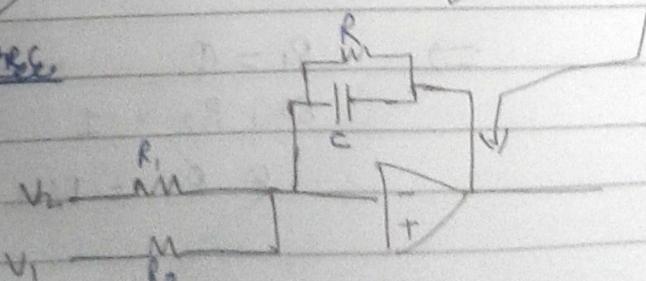

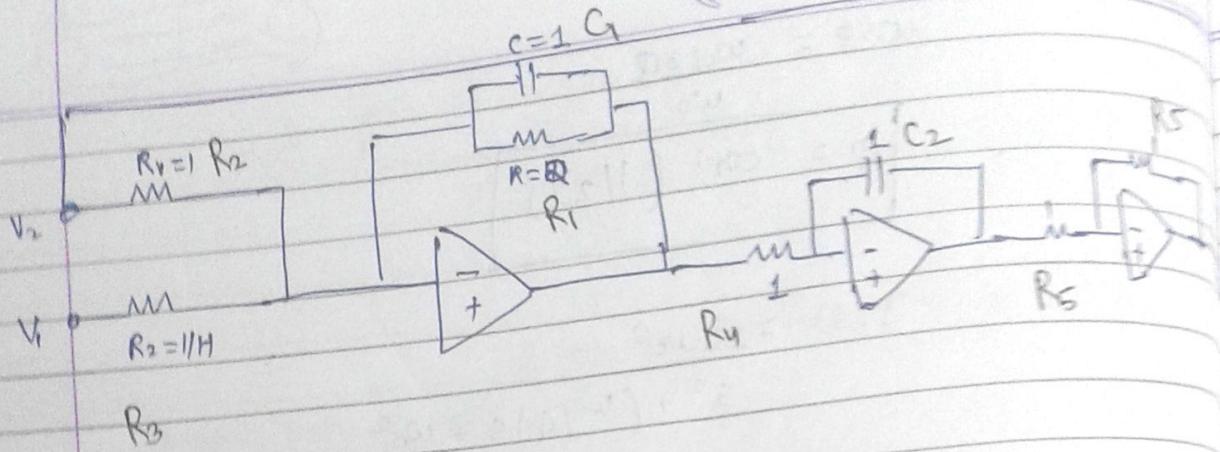

$$T(s) = \frac{-R_2 R_3 R_4 C_1 C_2 R_2}{s^2 + \left(\frac{1}{R_1 C_1}\right)s + \frac{1}{R_2 R_4 C_1 C_2}}$$

$$\omega_0 = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}$$

$$\varrho = \sqrt{\frac{R_1^2 C_1}{R_2 R_4 C_2}}$$

$$H = R_2 / R_3$$

for design:

$$\omega_0 \rightarrow \text{if } C_1 = C_2 = 1 \quad \left. \begin{array}{l} \\ & \end{array} \right\} \text{Normalized values}$$

$$\& R_4 = 1$$

$$\Rightarrow R_1 = \varrho \rightarrow \omega_0$$

$$\text{so, } R_2 = 1$$

$$\& R_3 = 1/H \rightarrow \text{gain}$$

By changing the R_1 , R_2 & R_3 we can change ω_0 , gain & ϱ .

Butterworth LPF response:

$$T(j\omega) = \left[\frac{1}{1 + (\omega/\omega_0)^{2n}} \right]^{1/2}$$

butterworth pole location:

$$s \text{ plane} = j\omega$$

$$\omega_0 = 1$$

$$\text{so, } T(s) = \left[\frac{1}{1 + (s/j)^{2n}} \right]^{1/2}$$

$$= \left[\frac{1}{1 + s^{2n}(-1)^n} \right]^{1/2}$$

$$\text{for pole location } 1 + s^{2n}(-1)^n = 0 = D(s)$$

$$\hookrightarrow \text{when } n=1; \quad 1 - s^2 = 0$$

for stable:

$$T(s) = \frac{1}{s+1}$$

$$s \rightarrow s/\omega_0$$

$$T(s) = \frac{1}{1 + s/\omega_0} = \frac{\omega_0}{s + \omega_0}$$

$$\hookrightarrow \text{when } n=2; \quad 1 + s^4 = 0$$


① if n is odd

one of the pole = 0°

if n is even

pole at = $\pm 90^\circ / n$

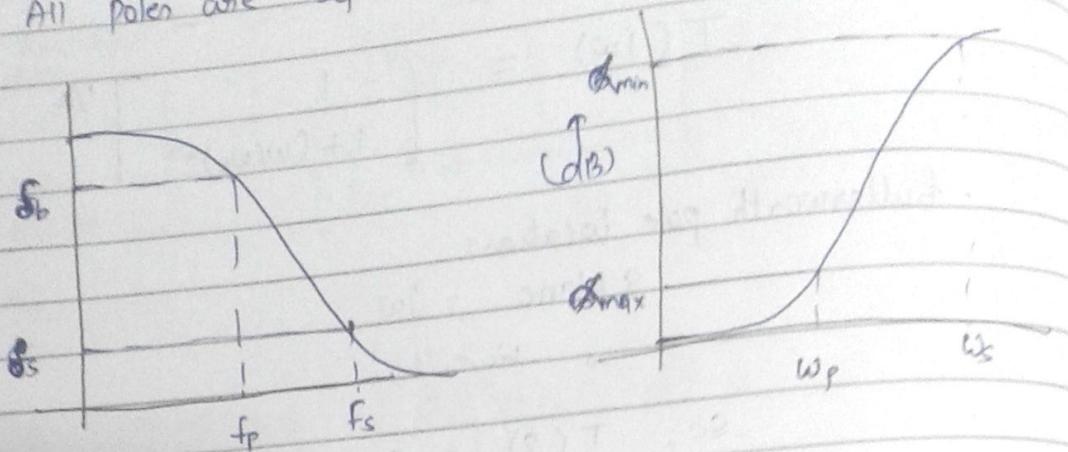② All poles are separated by $\frac{180}{n}$



$$\omega_p \rightarrow \alpha_p(\text{dB}) \text{ or } S_p$$

$$\omega_s \rightarrow \alpha_s(\text{dB}) \text{ or } S_s$$

- Gain A(dB)

$$\alpha_{dB} = -A(\text{dB})$$

- attenuation = 1/Gain

$$A = 10 \log |T^2(j\omega)|$$

$$\alpha = -A = -10 \log |T^2(j\omega)|$$

$$\alpha = -10 \log \frac{1}{1 + (\omega/\omega_0)^{2n}}$$

$$\frac{\alpha}{10} = \log [1 + (\omega/\omega_0)^{2n}]$$

$$10^{\alpha/10} - 1 = (\omega/\omega_0)^{2n}$$

$$\frac{\omega}{\omega_0} = (10^{\alpha/10} - 1)^{1/2n}$$

When $\omega \rightarrow \omega_p$ $\alpha \rightarrow \alpha_p$

$$\frac{\omega_p}{\omega_0} = (10^{\alpha_p/10} - 1)^{1/2n}$$

①

$$\frac{w_p}{w_s} = (10^{\alpha P/10 - 1})^{1/2n}$$

②

$$\frac{w_p}{w_c} = \left(\frac{10^{\alpha P/10} - 1}{10^{\alpha S/10} - 1} \right)^{1/2n}$$

$$\log\left(\frac{w_p}{w_s}\right) = \frac{1}{2n} \log\left(\frac{10^{\alpha P/10} - 1}{10^{\alpha S/10} - 1}\right)$$

$$m = \frac{1}{2} \cdot \frac{\log\left(\frac{10^{\alpha P/10} - 1}{10^{\alpha S/10} - 1}\right)}{\log\left(\frac{w_p}{w_s}\right)}$$

Ex 8-

$$w_p = 1000 \text{ rad/s}$$

$$w_s = 2000 \text{ rad/s}$$

$$\alpha P \text{ dB} = 0.5 \text{ dB}$$

$$\alpha S \text{ dB} = 20 \text{ dB}$$

find the order of
filter and w_c (cut off
frequency)

$$m = \frac{1}{2} \log\left(\frac{10^{\alpha P/10} - 1}{10^{\alpha S/10} - 1}\right)$$


Soln.

$$m = \frac{1}{2} \cdot \frac{\log\left(\frac{10^{\alpha P/10} - 1}{10^{\alpha S/10} - 1}\right)}{\log\left(\frac{w_p}{w_s}\right)} \approx 4.8 = 5$$

$$\frac{w_p}{w_s} = (10^{\alpha S/10} - 1)^{1/2n}$$

$$\frac{w_s}{w_c} = (99)^{1/2 \times 5}$$
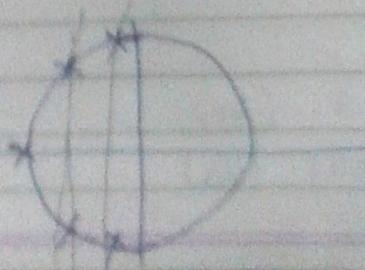
$$w_c = 1263.18 \text{ rad/s} \rightarrow w_s$$



order is odd

then $\rightarrow 0^\circ$

$$180^\circ = 36^\circ$$

Date _____
Page _____

$$\Rightarrow \Psi = 0^\circ, +36^\circ, +72^\circ$$

2nd order: $T(s) = \frac{\omega_0^2}{s^2 + (\frac{\omega_0}{\alpha})s + \omega_0^2}$

when $\omega_0 = 1$

$$T(s) = \frac{1}{s^2 + s/\alpha + 1}$$

$$\Psi = \cos^{-1} \left(\frac{1}{2\alpha} \right) \quad \& \quad \alpha = \frac{1}{2 \cos \Psi}$$


$$T(s) = \frac{1}{(s+1)(s^2 + s/\alpha + 1)(s^2 + s/\alpha + 1)}$$

$$T(s) = \frac{1}{(s+1)(s^2 + 2\cos\psi s + 1)(s^2 + 2\cos\psi s + 1)}$$

\downarrow \downarrow
 36° 72°

$$= \frac{1}{(s+1)(s^2 + 2\cos 36^\circ s + 1)(s^2 + 2\cos 72^\circ s + 1)}$$

5th order LTF

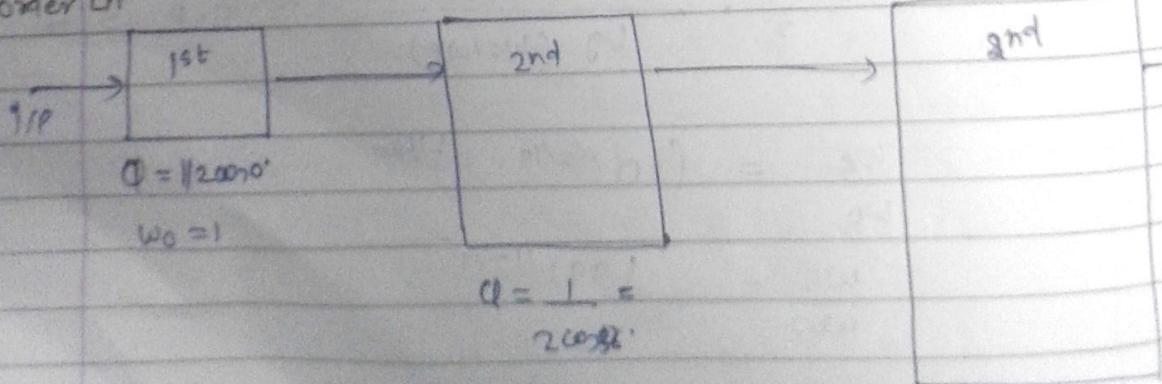


$$\Psi = 1/2 \cos 36^\circ$$

$\omega_0 = 1$

$$\omega_0 = 12.63 \text{ (tip)}$$

$$\omega_0 = 12.21 \text{ (w.s.)}$$


Byquist circuit:

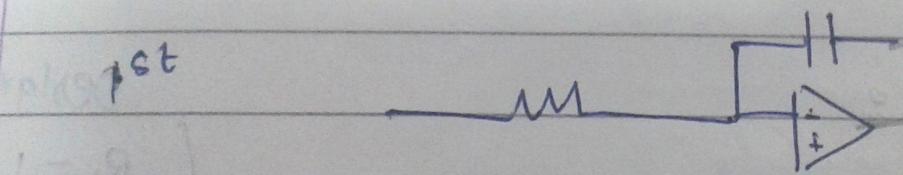

Date
Page

Analog filter Design:

Sallen and Key circuit :

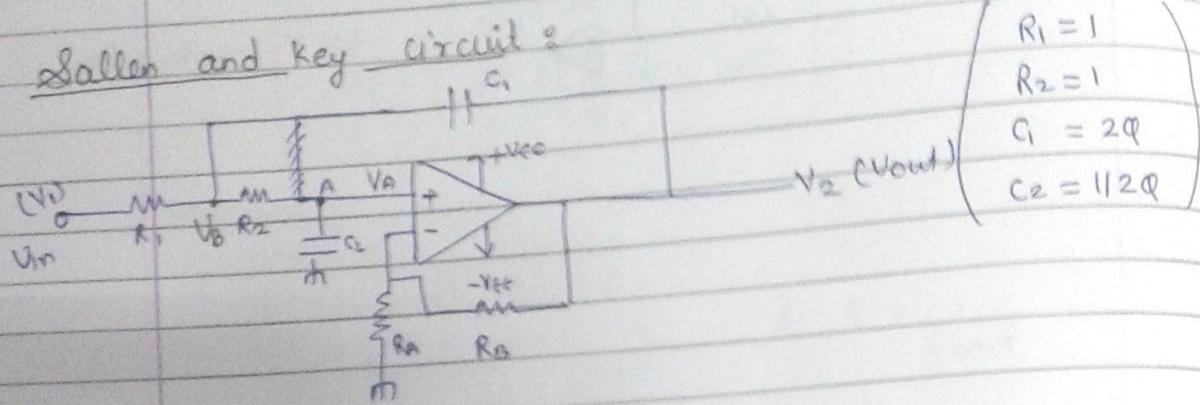

Design-2

$$\begin{cases} R_1 = 1 \\ R_2 = 1 \\ C_1 = 2\Omega \\ C_2 = 1/2\Omega \end{cases}$$

$$T(s) = \frac{V_{out}}{V_{in}} = \frac{V_2}{V_1}$$

$$\frac{V_2}{V_A} = \frac{1 + R_B}{R_A} = K \quad (\text{non inverting})$$

$$V_A = \frac{V_2}{K}$$

$$\text{KCL at node A: } \frac{V_A - V_B}{R_2} + V_A \cdot (sC_2) = 0 \quad \text{---(1)}$$

$$\text{node B: } \frac{V_B - V_A}{R_2} + \frac{V_B - V_1}{R_1} + (V_B - V_2) \cdot C_1 s = 0 \quad \text{---(2)}$$

$$\text{In eqn (1)} \quad V_A = V_2/K$$

$$\frac{V_2}{K} - V_B = - \frac{V_2}{K} (sC_2) \cdot R_2$$

$$V_B = \frac{V_2}{K} (1 + sC_2 R_2)$$

in eqn (2)

$$\frac{1}{R_2} \left[\frac{V_2}{K} (1 + sC_2 R_2) - \frac{V_2}{K} \right] + \frac{V_2 (1 + sC_2 R_2) - V_1}{K R_1} + \frac{V_2 (1 + sC_2 R_2) G_S}{K} - V_2 G_S = 0$$

$$\frac{V_2}{K} \left[\frac{1}{R_2} + \frac{C_2 s - 1}{R_2} + \frac{1}{R_1} + \frac{C_2 s R_2 + C_1 s + C_1 C_2 s^2 R_2 - K s}{R_1} \right] = \frac{V_1}{R_1}$$

$$\boxed{\frac{V_2}{V_1} = \frac{K \cdot 1 / R_1 R_2 C_1 C_2}{s^2 + \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} - \frac{K}{R_2 C_2} \right) s + \frac{1}{R_1 R_2 C_1 C_2}}} \quad \text{--- (A)}$$

$$T(s) = \frac{K w_0^2}{s^2 + \left(\frac{w_0}{\varphi} \right) s + w_0^2} \quad (\text{second order LPF eqn}) \quad \text{--- (B)}$$

By comparing (A) & (B)

$$w_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \quad \text{--- (2)}$$

$$\frac{w_0}{\varphi} = \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} - \frac{K}{R_2 C_2} \quad \text{--- (3)}$$

for designing the filter:

Design-18

$$w_0 = 1$$

$$\& \text{ if } R_1 = R_2 = 1$$

$$\& \quad C_1 = C_2 = 1$$

Then eqn (A)


$$\text{transfer func: } T(s) = \frac{K}{s^2 + (3-K)s + 1}$$

$$\text{so, } \varphi = 1/3-K$$

Date _____
 Page _____

for the value of Ω as per our choice, we
 have to only change in K .

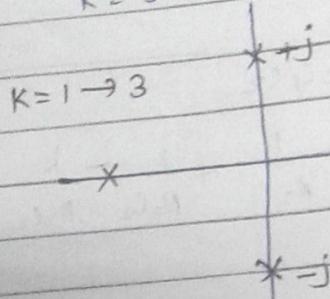When $K = 1 \rightarrow$ real axis (Poles)
 $K = 3 \rightarrow$ imag. axis (Poles)



By changing the value of K , poles locus is also change.

$$K = 1 + \frac{R_B}{R_A}$$

$$\Omega = \frac{1}{3-K}$$

$$3-K = \frac{1}{\Omega}$$

$$K = -1/\Omega + 3$$

$$\frac{-1}{\Omega} + 1 + 2 = 1 + \frac{R_B}{R_A}$$

$$\frac{-1}{\Omega} = \frac{R_B - 2}{R_A}$$

if $R_A = 1$ (let we assume)

$$\frac{-1}{\Omega} = R_B - 2$$

$$R_B = 2 - 1/\Omega$$

Design-2 :

Let assume $K = 1$

w_0 & Ω are given

if $R_1 = R_2 = 1$ & $w_0 = 1$

$$C_1 = ?$$

$$C_2 = ?$$

$$C_1 \cdot C_2 = 1 \quad (\text{By } ③ \text{ eqn})$$

$$\frac{1}{Q} = \frac{1}{C_1} + \frac{1}{C_1} + \frac{1}{C_2} - \frac{1}{C_2} \quad (\text{By } ④)$$

$$\frac{2}{C_1} = \frac{1}{Q}$$

$$C_1 = 2Q$$

$$\text{So, } C_2 = 1/2Q$$

Design-3

$$\text{if } R_A = R_B ; K = 2$$

$$B_{W0} = 1$$

$$\text{let } C_1 = 1 \& R_1 C_1 = R_2 C_2$$

$$R_1 = ? ; R_2 = ? ; C_1 = ? ; C_2 = ?$$

$$1 = \frac{1}{R_1 C_1} \Rightarrow R_1 C_1 = 1 \quad (\text{By } ③)$$

$$\text{so, } R_1 = 1$$

$$\frac{1}{Q} = \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1}{R_1 C_1} - \frac{2}{R_1 C_1} \quad (\text{By } ④)$$

$$\frac{1}{Q} = \frac{1}{R_2 C_1}$$

$$R_2 C_1 = Q$$

$$R_2 = Q$$



$$C_2 = 1/Q$$

$$T(s) =$$

$$(s+1)(s^2 + s(\alpha + 1))(s^2 + s(1/\alpha + 1))$$

$$\alpha = 5 ; \quad \psi = 0, \pm 36, \pm 92$$

$$\alpha = 1/2 \cos \psi$$

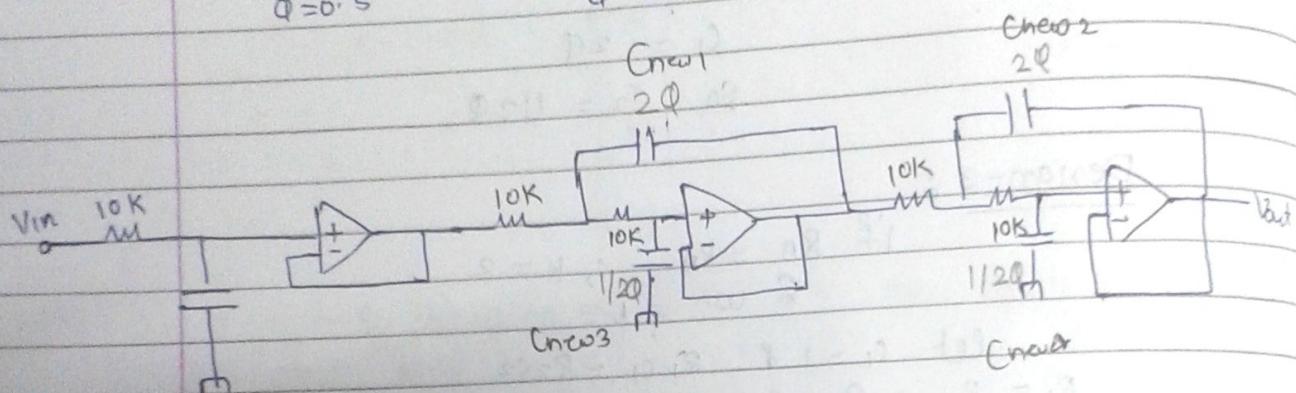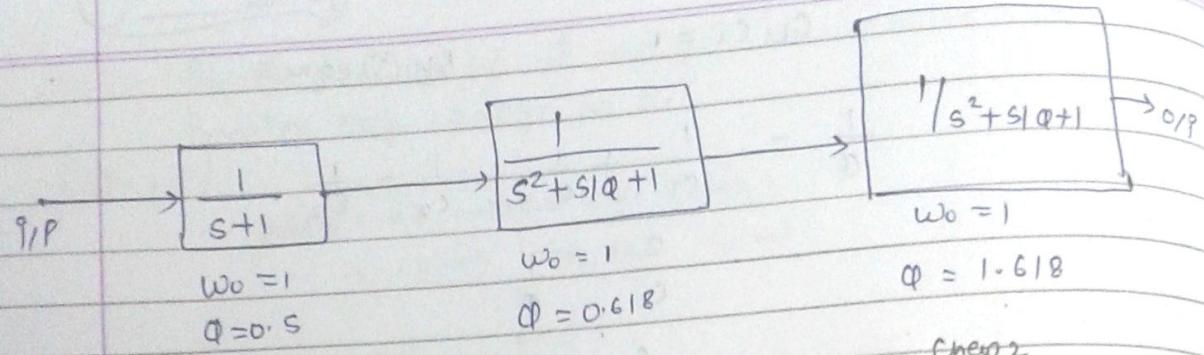

specifications are given: $\omega_p = 0.5 \text{ rad/s}$

$$\omega_s = 20 \text{ rad/s}$$

$$\omega_p = 1000 \text{ rad/s}$$

$$\omega_s = 2000 \text{ rad/s}$$

$$\omega_0 = 1263$$

freq. selective $K_F = \frac{\omega_0 \text{ new}}{\omega_0 \text{ old}} = \frac{1263}{1} = 1263$

mag.

$$R_{\text{new}} = K_m R_{\text{old}}$$

$$10K = K_m \times 1 \quad \text{if } R_{\text{new}} = 10K\Omega$$

$$K_m = 10K$$

$$C_{\text{new}} = \frac{1}{K_m K_F} C_{\text{old}}$$

$$C_{\text{new}} = \frac{1}{1000 \times 10 \times 1263} \times 2 \times 0.618$$

$$C_{\text{new}} = \frac{1}{10^4 \times 1263} \times 2 \times 0.618$$

Date _____
Page _____

$$C_{new \$/L} = \frac{1}{10^4 \times 12.63} \times \frac{1}{2 \times 1.618}$$

$$C_{new \$/L} = \frac{1}{10^4 \times 12.63} \times \left(\frac{1}{2 \times 0.618} \right)$$

Non linear application of op-amp

Topics:

- Comparator (non linear application)

- Schmitt trigger

- Square and gen^r

- triangular and gen^r

wave shaping
Clipper - Rectifier


- Clamper

- Sample & hold

- Peak detector

- Log and antilog are non linear


Comparator:

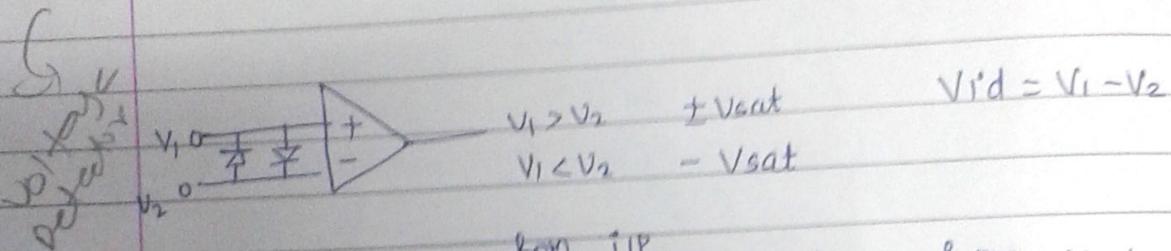

- to protect the ^{from OIP} high voltage from we used diode.

- OIP of comparator is square wave.


- when $V_2 = 0$, $V_d = 0$

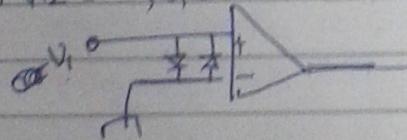



reference voltage is zero

then "zero-detector".


crossing

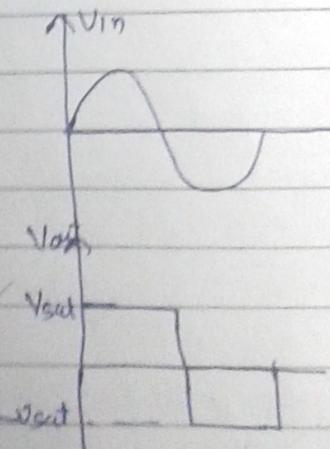

- when $V_{ref} \neq 0$

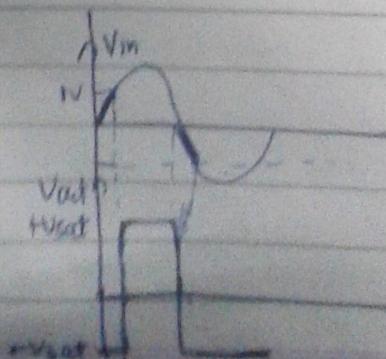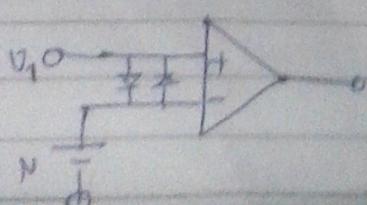

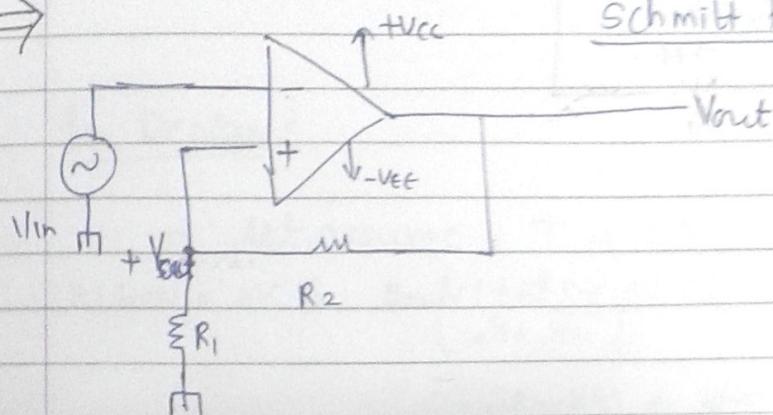we can't connect the O/P of comparator to digital circuits because Digital IC \rightarrow 5V \rightarrow and its comparator O/P is 13V \rightarrow then we have to clip that comparator O/P




Schmitt trigger circuit 8

$V_{out} = +Vs_{sat}$

$$V_{out} = \frac{R_1}{R_1 + R_2} (+Vs_{sat})$$


$V_{out} = -Vs_{sat}$
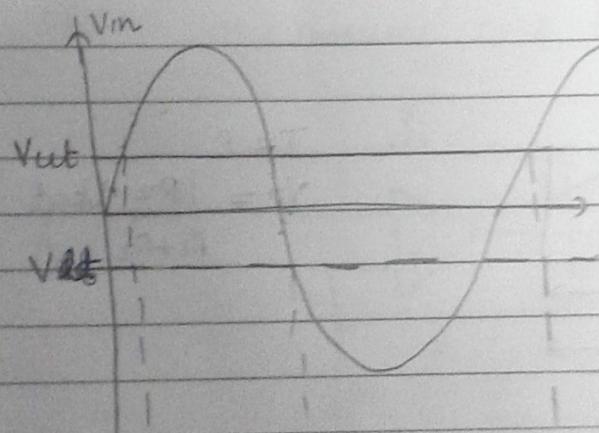
$$V_{out} = \frac{R_1}{R_1 + R_2} (-Vs_{sat})$$




$\Delta V_{th} = V_{out} - V_{in}$
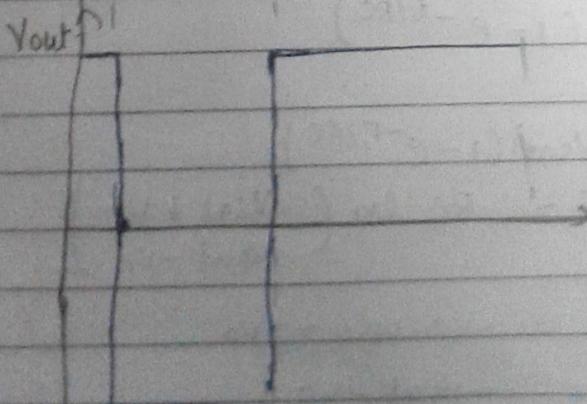
$$= \frac{R_1}{R_1 + R_2} (Vs_{sat} - Vs_{sat})$$



\rightarrow open loop configuration, BW is very high so noise is the (false triggering → unwanted transient)
when CMRR is very large it is possible to avoid false triggering

Oscillator

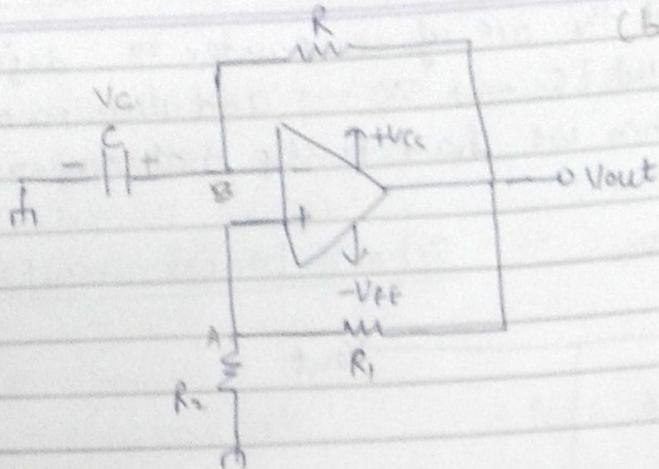


$$\text{when } V_{\text{out}} = V_{\text{sat}} ; V_A = \frac{R_2}{R_1 + R_2} V_{\text{out}} \text{ & } V_B = V_{\text{out}} / R$$

→ then cap. starts to change

$$V_c > V_m \rightarrow \text{then } V_{\text{out}} = -V_{\text{sat}} \text{ & } V_A = \frac{-R_2}{R_1 + R_2} V_{\text{sat}}$$

cap. starts to discharge.

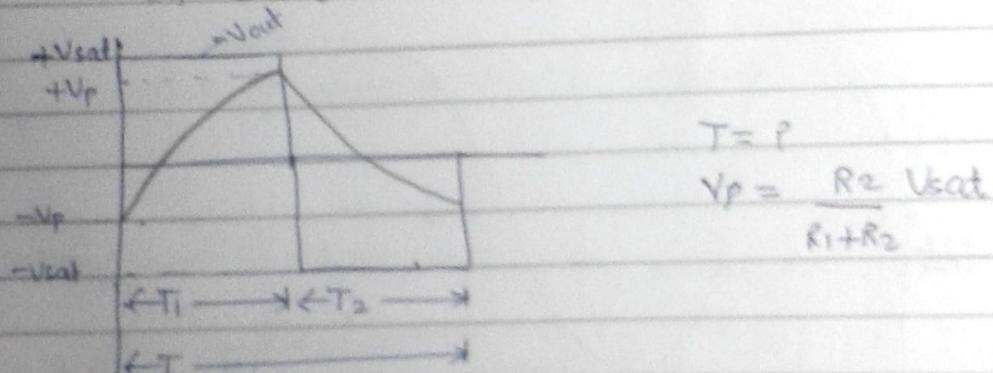

$$V_c = V(1 - e^{-t/RC})$$

$$\text{when cap. is changing: } 2V_p = (V_A - V_{\text{sat}})(1 - e^{-T_1/RC})$$

$$T_1 = RC \ln \left(\frac{V_{\text{sat}} + V_p}{V_{\text{sat}} - V_p} \right)$$

$$\text{when cap. is discharging: } V_c = -V_p - V_p = -2V_p$$

$$V = -V_{\text{sat}} - V_p$$

$$-2V_p = (-V_{\text{sat}} - V_p) [1 - e^{T_2/RC}]$$

$$T_2 = RC \ln \left(\frac{V_{\text{sat}} + V_p}{V_{\text{sat}} - V_p} \right)$$

$$T = T_1 + T_2$$

$$= 2RC \ln \left(\frac{V_{sat} + V_p}{V_{sat} - V_p} \right)$$

$$T = 2RC \ln \left(1 + \frac{2R_2}{R_1} \right)$$

for Design :


- let assume $T = 2RC$

$$\ln \left(1 + \frac{2R_2}{R_1} \right) = 1$$


$$1 + \frac{2R_2}{R_1} = e^1$$

$$\frac{2R_2}{R_1} = 2 \cdot 3 - 1 = 1 \cdot 7 \Rightarrow R_2 = R_1 (0.85)$$

- assume C & find R

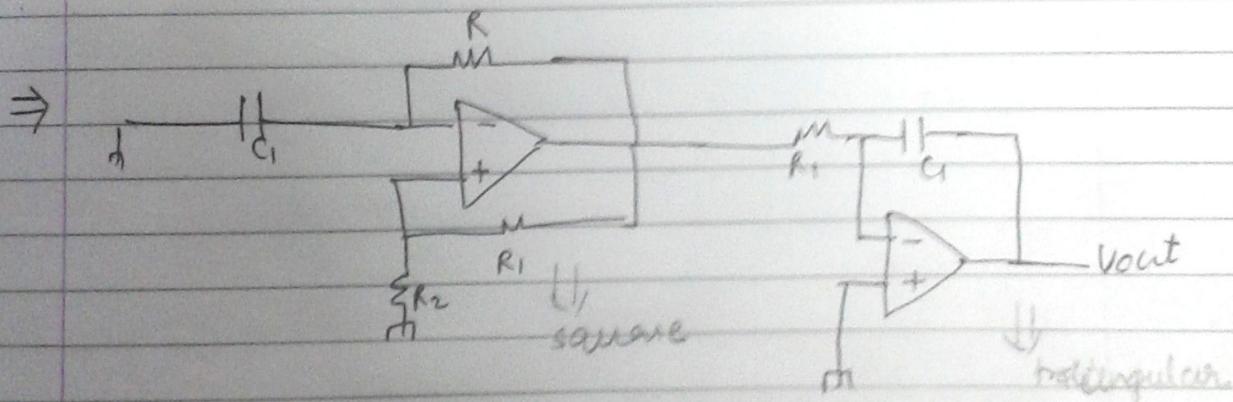

O/P of this is triangular wave

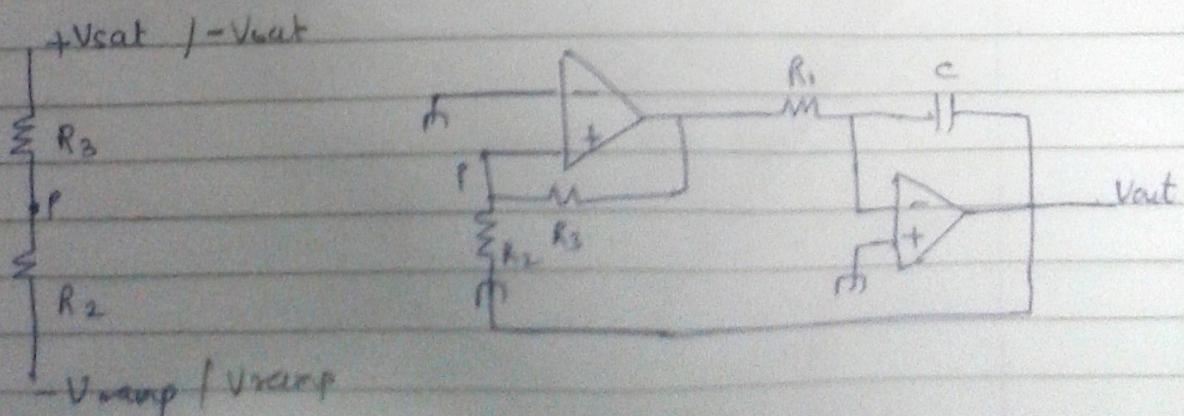

$$T = \frac{4 R_1 C_1 R_2}{(R_1 + R_2)}$$

$$V_{DIP} = \frac{2 R_2 V_{sat}}{(R_1 + R_2)}$$