

Ideal Characteristics of amplifiers

ideal : gain = ∞

$$BW = \infty$$

$$Z_{in} = \infty$$

$$Z_{out} = 0$$

Slew rate : change of O/P wrt ^{time} input = ∞

practically

q_{min} = finite


$$B \cup = \text{finite}$$

z^{∞} = finite (z^{∞} in MD) \leftarrow 100%

$$z_{\text{out}} = (\leq 100 \Omega)$$


$$SR = (0.5 - 100 \text{ V}/\mu\text{sec})$$

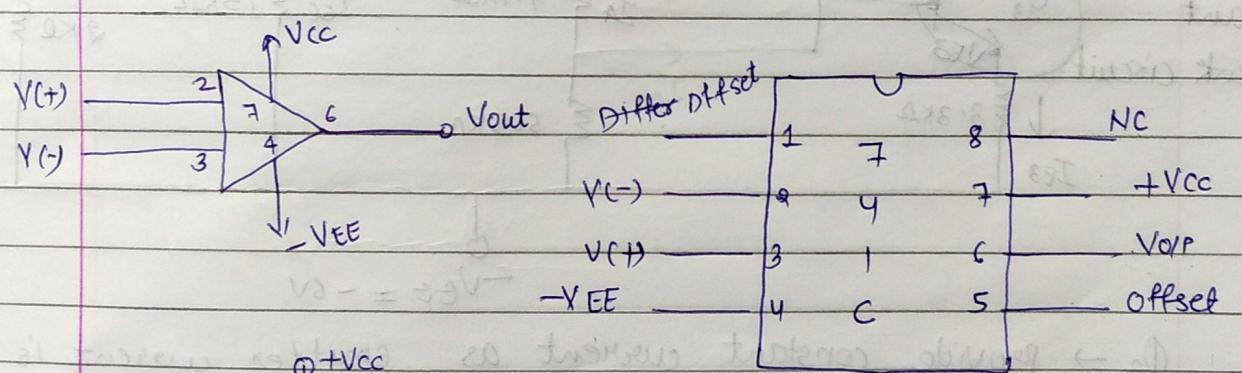Block Diagram & circuit symbol of OP-amp :




74) C → commercial
↓ ↗ single O/P

7 terminals is used

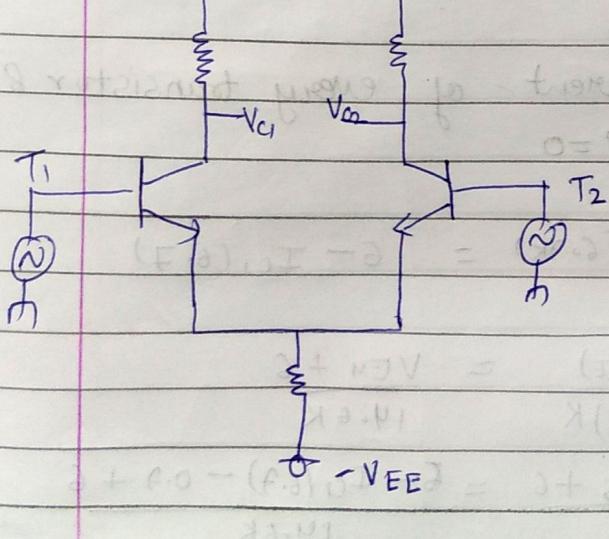


dual PIP dual balanced OIP ($OIP^* V_{C18} N_6$)

Unbalanced O/P

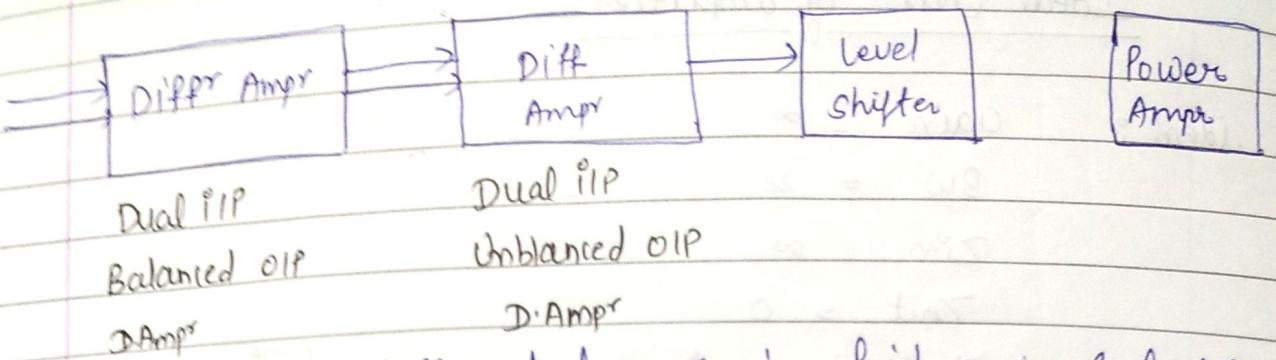

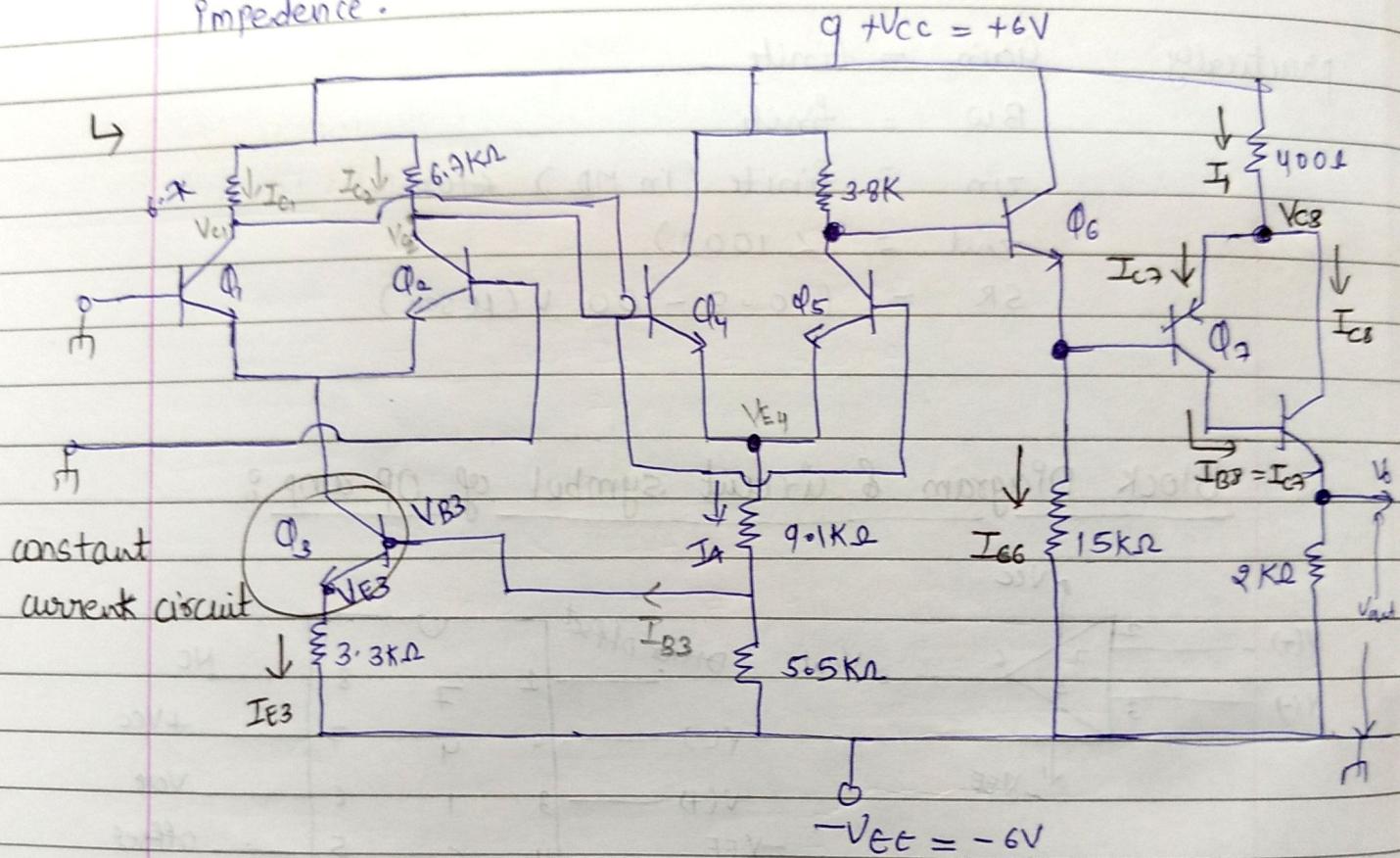* purpose of two differential amp is high gain & high OIP impedance.



$\Phi_3 \rightarrow$ provide constant current as emitter current is constant.


Q1 Determine collector current of every transistor & dc OIP voltage ; when OIP = 0

$$V_{CI} = V_{CC} - I_{C1} (6.7K) = 6 - I_{C1} (6.7)$$

$$V_{E4} = V_{CI} - V_{BE5}$$

$$I_4 = \frac{V_{E4} - (-V_{EE})}{(9.1 + 5.5)K} = \frac{V_{E4} + 6}{14.6K}$$
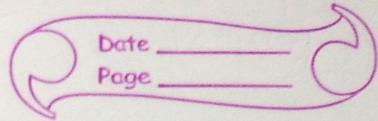
$$= \frac{V_{CI} - V_{BE5} + 6}{14.6K} = \frac{6 - I_{C1}(6.7) - 0.7 + 6}{14.6K}$$



$$I_4 = \frac{11.3 - (6.7K) I_C}{14.6K}$$

$$V_{B3} = (5.5K) I_4 - V_{EE} = \frac{5.5}{14.6} [11.3 - 6.7K I_C] - 6 \\ V_{E3} = V_{B3} - V_{BE3} = 10.25 - 2.52K I_C \\ = V_{B3} - 0.7 = 9.55 - 2.52K I_C$$

$$V_{E3} = (5.5K) I_4 + (-6) - 0.7$$


$$I_{E3} = \frac{V_{E3} - (-V_{EE})}{3.3K\Omega} = \frac{3.55 - 2.52K I_C}{3.3K}$$


$$I_{E3} = 1.07 \times 10^{-3} - 0.75 I_C$$

$$I_{E3} = 2 I_C \quad 2.75 I_C = 1.07 \times 10^{-3}$$

$$I_C = 388.02 \mu A$$

Op-amp IC-741 parameters

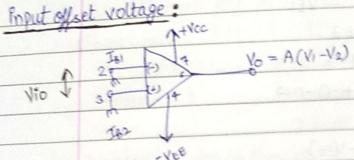Input offset voltage:

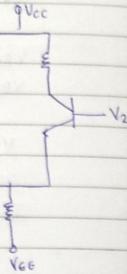 - Input offset is dc voltage
 for IC 741 $V_{IO} = 5mV$



TIP offset current:

$$\text{offset current } I_{IO} = |I_{B1} - I_{B2}| = 200nA$$

$$\text{bias current } I_B = \frac{I_{B1} + I_{B2}}{2} = 500nA$$

$$R_{IP} = 1\Omega$$

$$R_{OP} = < 100\Omega$$


$$\text{open loop voltage gain} = \frac{\text{OIP Voltage}}{\text{diff IP voltage}}$$

$$= \frac{V_O}{V_{ID}}$$

$$= 2 \times 10^5$$

Slew rate \rightarrow is defined in data sheet at unity gain.

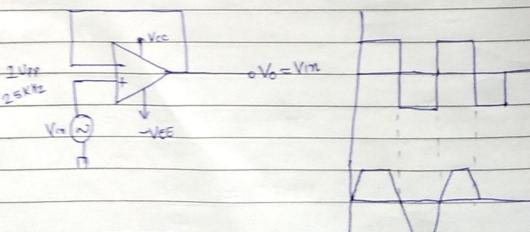
$$SR = \frac{dV_{out}}{dt} \text{ V/μs} = 0.5 \text{ V/μs}$$



Output Voltage $|V_{OL}| < |V_{OC}|$

$$V_{out} = \pm 13V$$

CMRR:

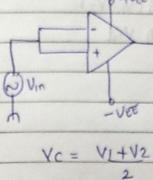

$$V_o = Ad(V_1 - V_2) + Ac V_c$$

practically $Ad = \infty$ & $Ac = 0$

$$\text{CMRR} = \frac{Ad}{Ac} = 90 \text{ dB}$$

$$V_c = \frac{V_1 + V_2}{2}$$

SVRR & PSRR:

SVRR \rightarrow Supply voltage rejection ratio

PSRR \rightarrow Power supply rejection ratio

$$[SVRR = PSRR] = \frac{\Delta V_{IO}}{\Delta V} \text{ microvolt/volt}$$

$\Delta V \rightarrow$ supply voltage

$$SVRR_{dB} = \left(\frac{1}{\Delta V_{IO}/\Delta V} \right)$$

Short circuit Protection:

$$I_{SC} = 25mA$$

$$\text{Power dissipation } I_{source} = 2.8mA$$

- its analogue ic's \rightarrow we supply only 5-15V.


- $\xrightarrow{\text{IP+noise}} \boxed{\text{Amp}}$ \rightarrow amplify the noise also!

$\xrightarrow{\text{IP+noise}} \boxed{\text{Op-Amp}}$ \rightarrow only amplify the signal - when CMRR is high

- CMRR gives the knowledge about the how efficient the op-amp for rejection of noise.




Date 25-July
Page

Equivalent circuit 8

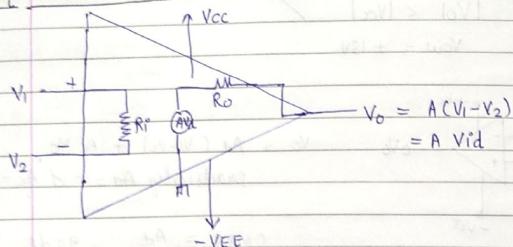


open loop configurations

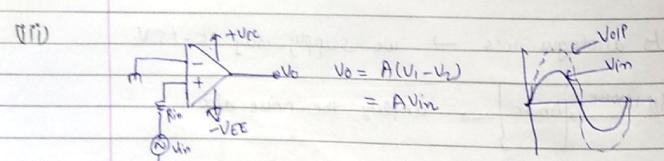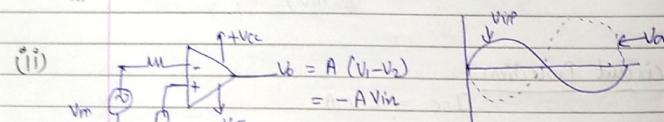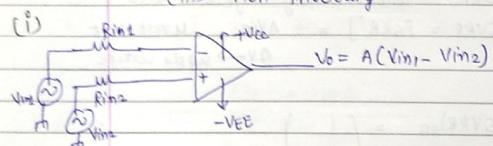- (i) Differential Amp
- (ii) Inverting
- (iii) Non-inverting



$$\begin{aligned} \text{Vo} &= A(V_1 - V_2) = AV_d \\ |V_o| &< |V_{cc}| \\ |V_{id}| &< |V_{cc}| = 75 \text{ mV} \end{aligned}$$

Charging

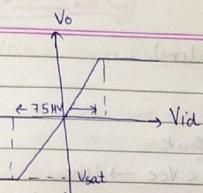


- for linear application, $|Vid| < 75 \text{ mV}$
 $|Vid| > 75 \text{ mV}$, then op-amp will go on saturation region.

- for linear application, open loop conf. is not used because for linear application $|Vid| < 75 \text{ mV}$, which is difficult to achieve (very small range).

Ex8- (i) $V_{in1} = 5 \text{ mV DC}$ (ii) $V_{in1} = 10 \text{ mV sine}$
 $V_{in2} = -7 \text{ mV}$ $A = 2 \times 10^5$ $V_{in2} = 20 \text{ mV wave}$

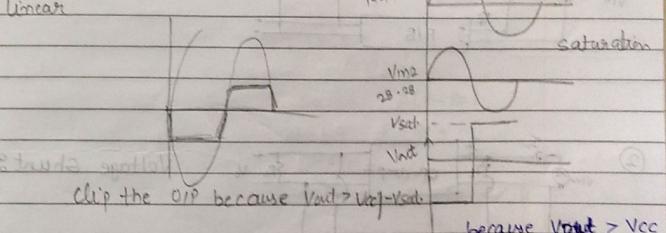
Sol: $V_{out} = A[V_{in1} - V_{in2}]$
 $= 2 \times 10^5 [5 + 7] \mu\text{V}$
 $= 24 \times 10^5 \times 10^{-6}$
 $= 2.4 \text{ V DC}$



Clip the OIP because $|V_{out}| > |V_{cc}|$

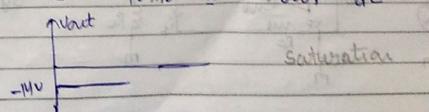(iv) $V_{in1} = 20 \text{ mV DC}$ (Inverting amp)

$$\begin{aligned} V_{out} &= A(V_{in1} - V_{in2}) \\ &= -AV_{in2} \\ &= -2 \times 10^5 \times 20 \times 10^{-3} \\ &= -40 \times 10^2 = -4000 \text{ mV DC} \end{aligned}$$






single power
dual power supply

Date 28-July
Page

(iv) $V_{in} = -50 \text{ mV Peak}$ (inverting)
 $V_o = -A V_{in}$
 $= 2 \times 50 \times 10^{-6} \times 10^5$
 $= 100 \times 10^{-1} = 10 \text{ V Peak}$

$V_o < V_{cc} \rightarrow \text{linear}$
 $V_o > V_{cc} \rightarrow \text{saturation}$

feedback configurations

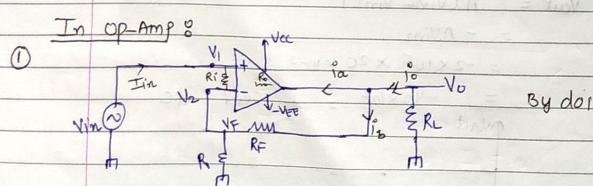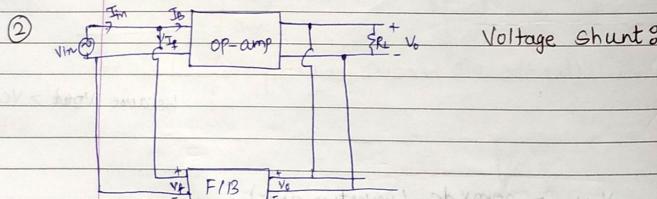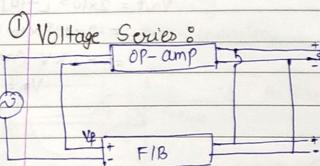

Voltage Series FB OP-amp / Non-inverting amp

gain

A - Open loop gain
AF - Close loop or Feedback gain
 $AF = \frac{V_o}{V_{in}}$

A $V_1 = V_{in}$
 $V_2 = V_F = \frac{R_1}{R_1 + R_F} V_o$
 $V_o = A(V_1 - V_2)$

so, $AF = A \left(\frac{V_1 - V_2}{V_1} \right) = A \left(1 - \frac{V_2}{V_{in}} \right)$

$AF = A \left(1 - \frac{R_1 V_o}{V_{in} (R_1 + R_F)} \right)$

$AF = A - A \frac{R_1}{R_1 + R_F} AF$

$AF \left(1 + A \frac{R_1}{R_1 + R_F} \right) = A$

$AF = \frac{A(R_1 + R_F)}{R_1 + R_F + A R_1}$

So, $AF = \frac{R_1 + R_F}{R_1} = \frac{1 + R_F}{R_1} = AF$


If $AF = 11$

then $R_F = 10 R_1$

(i) $R_1 = 1K \Rightarrow R_F = 10K$

(ii) $R_1 = 5K \Rightarrow R_F = 50K$

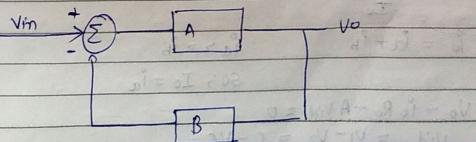(iii) $R_1 = 100\Omega \Rightarrow R_F = 1K$



$$B = \frac{V_F}{V_O} = \frac{R_1}{R_1 + R_F}$$

$$A_F = A = \frac{A}{1 + AB} = \frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_{in} - A}$$

In ideal condition :

$$V_o = A V_{id}$$

ideally A is infinite

$$V_{id} = \frac{V_o}{A} \approx 0 \quad (V_o - V) / A = 0$$

$$(V_1 - V_2) = 0 \Rightarrow (V_o - V) / A = 0 \Rightarrow A = \infty$$

$$V_{in} = V_F = \frac{R_1}{R_1 + R_F} V_o$$

$$(V_o - V) / A = V_o / (R_1 + R_F)$$

$$A_F = \frac{V_o}{V_{in}} = 1 + R_F$$

$$V_{in} = V_o / R_1$$

OIP impedance :

$$R_{if} = \frac{V_{id}}{I_{in}}$$

$$(V_o - V) / I_{in}$$

$$V_o = A V_{id}$$

$$A(V_1 - V_2) = V_{out} = \frac{A}{1 + AB} V_{in}$$

$$\frac{V_o - V_{id}}{V_{in}} = \frac{1}{AB + 1} \frac{V_{id}}{I_{in}} = \frac{V_{id}}{R_{if}}$$

$$R_{if} = (1 + AB) R_i$$

OIP impedance :

$$R_{of} = \frac{V_o}{I_o}$$

$$I_o = i_a + i_b$$

$$i_a > i_b$$

$$\text{so, } I_o = i_a$$

$$V_o - i_o R_o - A V_{id} = 0$$

$$V_{id} = V_1 - V_2 \approx 0 - V_F$$

Date _____
Page _____


$$\Rightarrow V_{id} = -V_F$$

$$\beta = \frac{V_F}{V_o}$$

$$R_{of} = \frac{R_o}{1 + AB}$$

Date 1-Aug
Page _____

Bandwidth

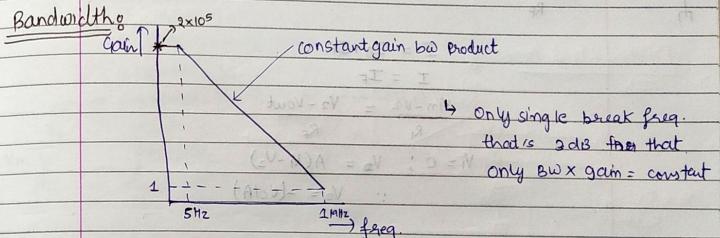

for open loop op-amp : $A = 2 \times 10^5$; $f_o \rightarrow$ single break away freq.

$$BW = 5 \text{ Hz}$$

Bandwidth is Ties in non-inverting feedback ampr

$$2 \times 10^5 \times 5 = 1 \text{ MHz} = \text{for open loop}$$


$$\text{Unity gain BW} = 1 \times 1 \text{ Hz}$$

* $\boxed{UGB \text{ (Unity gain Bandwidth)} = A f_o \\ = A F F_F}$

$$\frac{f_o}{A} = \frac{A f_o}{A F} = f_o (1 + BA)$$


$$V_{to} = \pm V_{sat} \quad (OIP \text{ offset voltage})$$

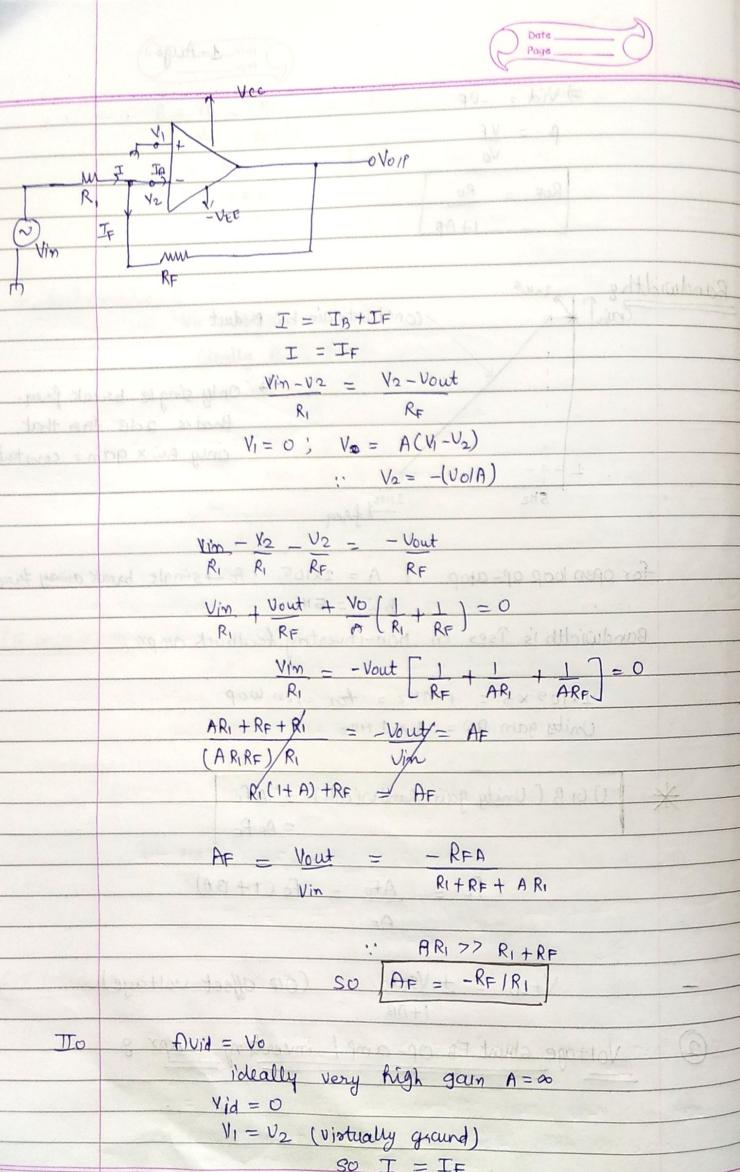② Voltage shunt FB op-amp / inverting ampr :



On Impedance:
 - V_{in} is shorted
 - same as non-inverting
 $R_{of} = \frac{R_o}{1+BA}$

Pip impedance:

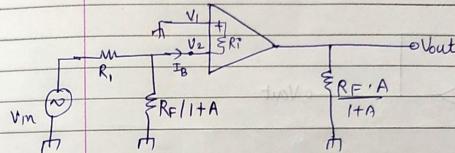

$$R_{if} = R_i + \left(\frac{R_F}{1+A} \parallel R_i \right) \quad : A \approx \infty$$

$$R_{if} \approx R_i$$

Gains

$$A F = \frac{V_{out}}{V_{in}} = -\frac{R_F A}{R_i + R_F}$$

$$A F = -\frac{A K}{1+AB} = \left(K \rightarrow R_F \right)$$

frequency

$$f_f = (AB+1)f_0$$

$$U_{GB} = A f_0 \Rightarrow f_0 = \frac{U_{GB}}{A}$$

$$\text{so, } f_f = \frac{U_{GB}}{A K} (1+AB) K$$

$$f_f = \frac{U_{GB} \cdot K}{A F} \rightarrow \text{inverting}$$


$$f_f = \frac{U_{GB}}{A F} \rightarrow \text{non-inverting}$$

Date 4-Aug
Page

- BW is higher for non-inverting amplifiers because $0 < K < 1$
- so $f_{T\text{ non}} = \frac{U_{GB}}{2}$; if $R_F = R_1$

By eqn ① & ②

Differential Amplifier

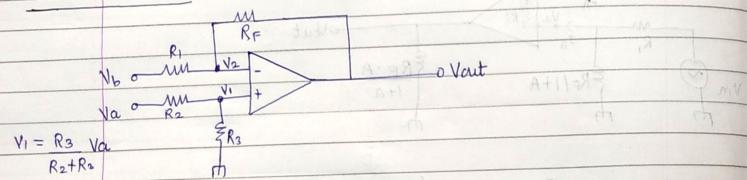

By Superposition theorem

$\rightarrow V_b$ active (inverting); V_a grounded

$$V_{ob} = -\frac{R_F}{R_1} V_b$$

$\rightarrow V_a$ active (non-inverting); V_b grounded

$$V_{oa} = \left(1 + \frac{R_F}{R_1}\right) V_a$$

$$V_{oa} = \left(1 + \frac{R_F}{R_1}\right) \frac{R_2}{R_2 + R_3} V_a$$

Let assume $R_2 > R_F$ & $R_3 > R_1$

$$V_{oa} = \left(1 + \frac{R_F}{R_1}\right) \frac{R_F}{R_1 + R_F} V_a$$

$$V_{oa} = \frac{R_F}{R_1} V_a$$

Hence we get diff. i/p impedance when connected to different terminals.

Hence while we connect $V(+)$ & $V(-)$ together impedance won't match. So avoid this problem some modification is done.

Date 4-Aug
Page

non-invert $V(+)$: $R_{IF1} = R_1(1+AF)$


inverting $V(-)$: $R_{IF2} = R_1$

1st

Differ. Amp

2nd

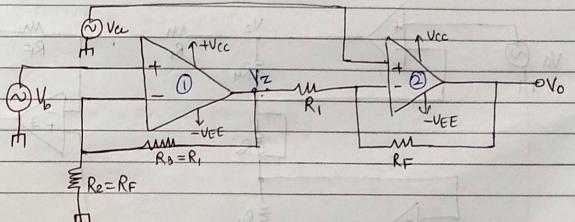- Loading impedance matching is not done for Differ. Amp



OP-amp ① is non-inverting amp

OP-amp ② is differential amp

$$V_z = \left(1 + \frac{R_1}{R_F}\right) V_b$$

$$V_{out} = -\frac{R_F}{R_1} V_z + V_a \left(1 + \frac{R_F}{R_1}\right)$$

(when $V_a = 0$) (when $V_z = 0$)
superposition theorem

$$V_{out} = -\frac{R_F}{R_1} \left[1 + \frac{R_1}{R_F}\right] V_b + V_a \left(1 + \frac{R_F}{R_1}\right)$$


$$= -\frac{R_F}{R_1} V_b - V_b + V_a + V_a \frac{R_F}{R_1}$$

$$= \left(1 + \frac{R_F}{R_1}\right) (V_a - V_b)$$


$$R_{IFa} = R_i(1 + AB)$$

$$R_{IFb} = R_i(1 + AB)$$


$$R_{IFa} \neq R_{IFb}$$

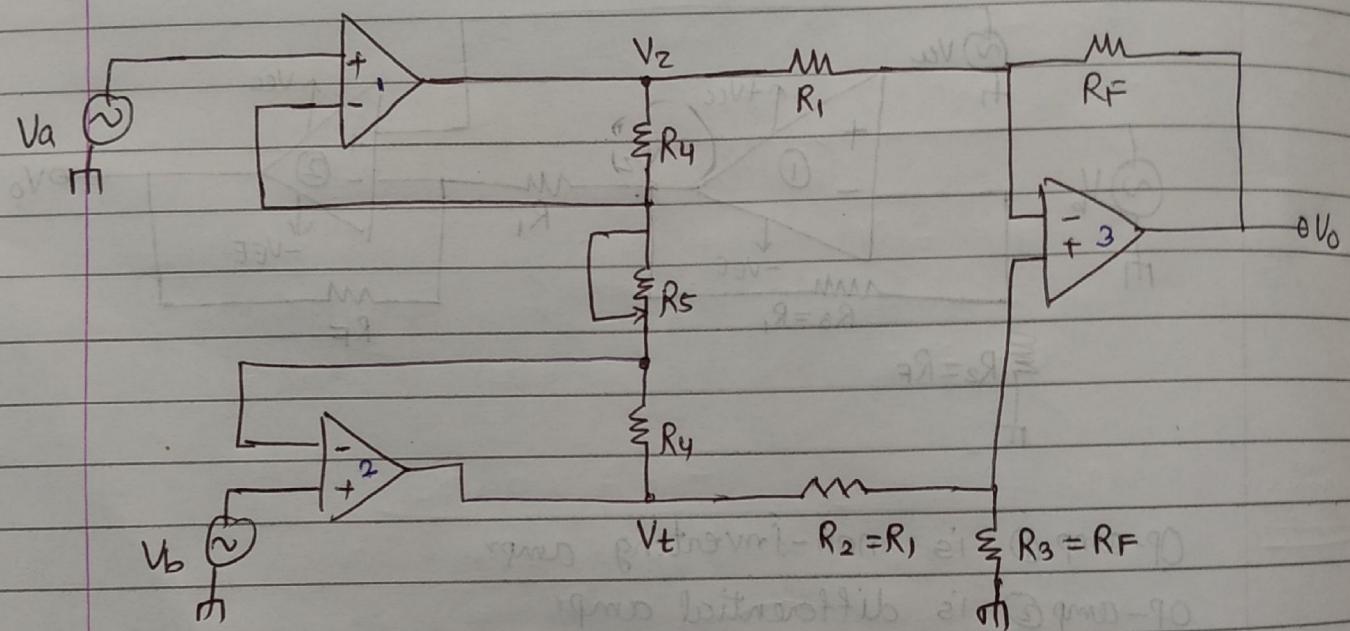

① When $V_b = 0$

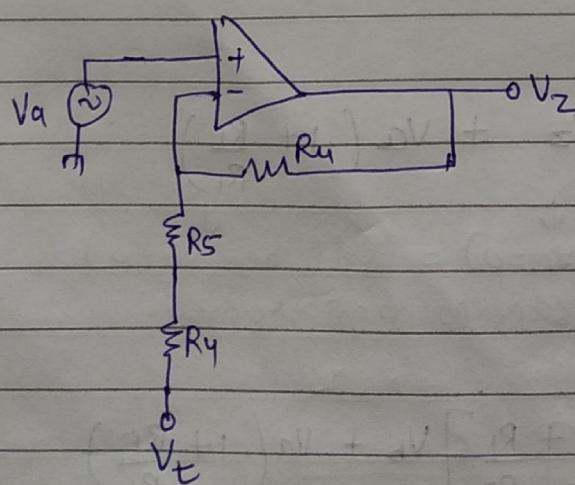


② When $V_a = 0$

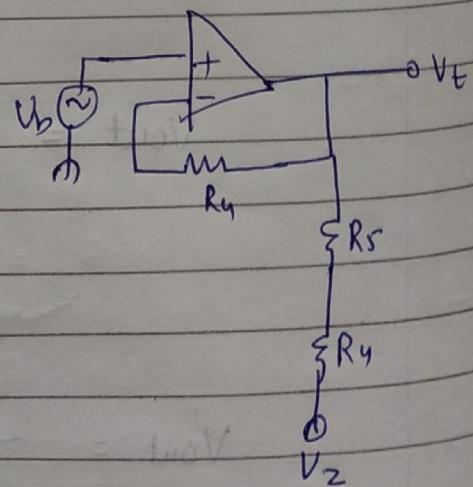

$$\textcircled{1} \quad V_z = V_a \left[1 + \frac{R_y}{R_4 + R_5} \right] + V_t \left[-\frac{R_y}{R_4 + R_5} \right]$$
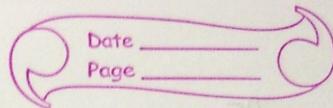
$$\textcircled{2} \quad V_t = V_b \left[1 + \frac{R_y}{R_4 + R_5} \right] + V_z \left[-\frac{R_y}{R_4 + R_5} \right]$$



$$R_{ifa} = R_1(1 + AB)$$

$$R_{ifb} = R_1(1 + AB)$$

~~Reason~~ $R_{ifa} = R_{ifb}$ (both are coming from op-amp)

becuz same value of B , $R_{ifa} = R_{ifb}$


$$\frac{AV}{AV - 1} = \frac{AV}{B} \rightarrow \frac{R_4}{R_4 + R_5} \xrightarrow{\text{approximate } B \rightarrow} \frac{R_4}{R_4 + R_5}$$

$$(3) V_{out} = V_z \left(-\frac{RF}{R_1} \right) + V_t \left(1 + \frac{RF}{R_1} \right)$$

$$V_o = - \left(1 + \frac{2R_4}{R_5} \right) \frac{RF}{R_1} V_{ab}$$

$$V_{ab} = V_a - V_b$$

Date _____
Page _____

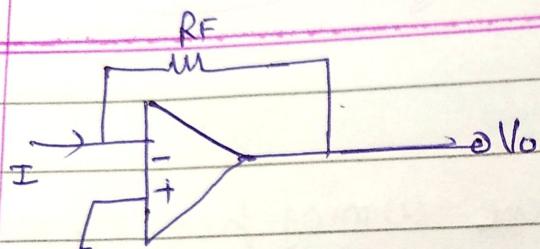

PIP → current

OIP → voltage

Application : d7.8
d7.9

- Solar Panel

- fiber optic comm^m


- DAC

$$V_O = -\frac{R_F}{R_I} V_{in}$$


$$= -R_F \cdot I_{in}$$

$$\left(\frac{-R_F + 1}{R_F}\right) + V + \left(\frac{-R_F - 1}{R_F}\right) - V = twoV$$

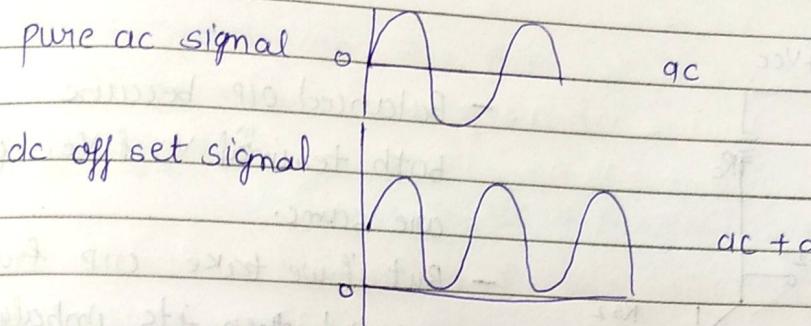⇒ By Using level shifter, we can remove dc from ac



Block Diagram of OP-AMP

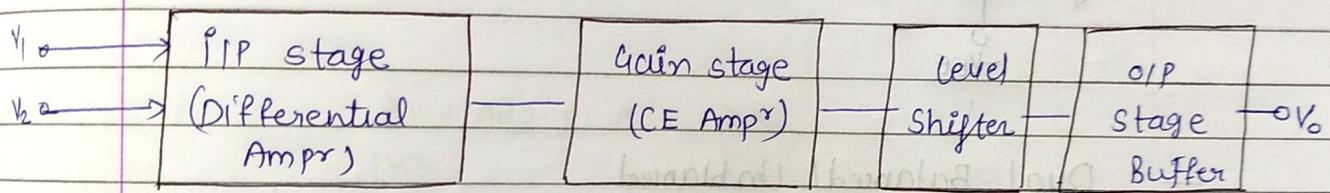

$$\hookrightarrow \text{common mode signal } V_{cm} = \frac{V_1 + V_2}{2}$$


$$\hookrightarrow \text{differential signal } V_{id} = V_1 - V_2$$

\hookrightarrow Differential gain A_d is high [10^4 to 10^5]
Common mode gain A_{cm} is low [0]

$$\hookrightarrow \text{Common mode regulation ratio (CMRR)} = \frac{A_d}{A_{cm}} \approx \infty$$


$$\hookrightarrow Z_{in} = (1 \text{ to } 2 \text{ M}\Omega)$$

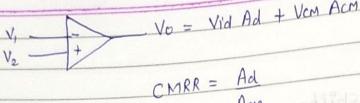- In op-amp we don't have coupling capacitor so op-amp can amplify the ac and dc both.
- A_{cm} is attenuation, not gain
- op-amp would always amplify the $V_{id} = V_1 - V_2$



$$CMRR = \frac{Ad}{Acm}$$

Differential Amplifier

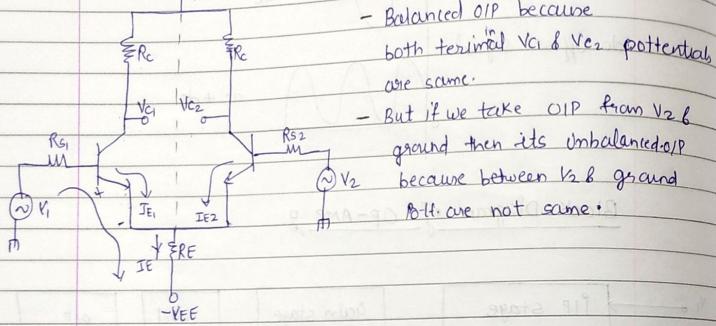

- Balanced OIP because both terminal V_{c1} & V_{c2} potentials are same.
- But if we take OIP from V_2 & ground then its unbalanced OIP because between V_2 & ground both are not same.

Dual Balanced / Unbalanced

Single " " "

dc analysis:

I_{EQ}

$$\star V_1 \& V_2 \text{ ac supply} = 0$$

$$- I_{E1} = I_{E2}$$

$$IE = I_{E1} + I_{E2}$$

$$- IC = IE (x=1)$$

$$IE = \beta I_B$$

$$\text{Applying Kirchhoff's Law } I_B R_S + V_{BE} + I_E R_E - V_{EE} = 0$$

$$\frac{IE}{\beta} R_S + I_E R_E + V_{BE} - V_{EE} = 0$$

$$IE \left(\frac{R_S + R_E}{\beta} \right) = V_{EE} - V_{BE}$$

$$I_{EQ} = \frac{V_{EE} - V_{BE}}{(R_E + R_S/\beta)}$$

Date _____
Page _____

$$V_{CF} = V_C - V_E$$

$$= V_{CC} - I_C R_C - (V_{BE})$$

$$\boxed{V_{CF} = V_{CC} + V_{BE} - I_C R_C}$$

ac analysis:

- Small Signal gain Ad, Acm
all dc value are ground.

(1) for calculating Ad :

$$V_o = Ad V_d + Acm V_{cm} \quad (1)$$

$$V_1 = V_{S1/2} \& V_2 = -V_{S1/2}$$


$$V_{id} = \frac{V_S + V_S}{2} = V_S$$

$$V_{cm} = 0$$

$$\text{So then } Ad = \frac{V_o}{V_{id}}$$


Load balanced

$$Ad_1 + Ad_2 = Ad = 2 Ad_1$$

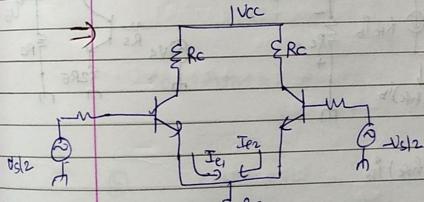

$I_{E1} \downarrow, I_{E2} \uparrow$
so potential drop across $R_E = 0$
so emitter terminal will be ground.

equivalent circuit:

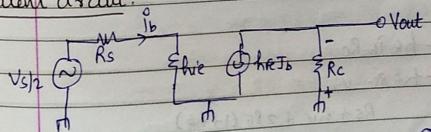

$$V_{out} = - h_{FE} I_B R_C \quad (1)$$

$$V_S = \frac{I_B}{2} (R_S + h_{FE} R_C) \quad (2)$$

$$\text{So, } V_{out} = - \frac{h_{FE} R_C}{2} \frac{V_S}{R_S + h_{FE} R_C}$$

$$A_d = \frac{V_{out}}{V_s} = -\frac{h_{FE} R_c}{2(R_s + h_{FE})}$$

(B) for calculating A_{CM}:


$$V_{id} = 0$$

$$V_1 = V_s; V_2 = V_s$$


$$V_{CM} = V_s$$

$$V_{out} = V_{CM} A_{CM}$$

$$V_{out} = V_s A_{CM}$$

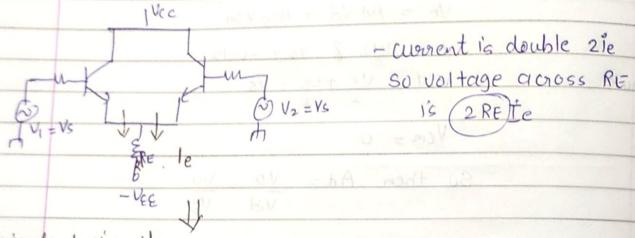

Equivalent circuit:

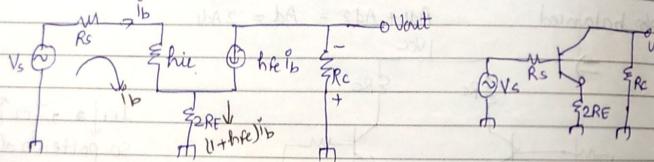

$$i_e = (1 + h_{FE}) i_b$$

$$V_s = [R_s + h_{FE}] i_b + [(1 + h_{FE}) i_b \cdot 2R_E]$$

$$V_s = [R_s + h_{FE} + 2R_E(1 + h_{FE})] i_b$$

$$V_{out} = -h_{FE} i_b R_c$$

$$= -h_{FE} R_c; V_s$$

$$R_s + h_{FE} + 2R_E(1 + h_{FE})$$

$$\frac{V_{out}}{V_s} = A_{CM} = -\frac{h_{FE} R_c}{R_s + h_{FE} + 2R_E(1 + h_{FE})}$$

(C) OIP impedance :

$$Z_{out} = R_c$$

(D) SIP impedance :

$$i_b = V_s$$

$$2(R_s + h_{FE})$$

from (A)

$$Z_{in} = 2(R_s + h_{FE})$$

- By removing the second signal $V_2 = 0$
 $V_1 = V_s$

Example : Determine diff. amp's OIP voltage when $V_1 = 300 \mu V$
 $V_2 = 240 \mu V$; diff. gain = 5000; CMRR = (A) 100 (B) 105
Calculate OIP voltage.

Sol:

$$V_{id} = V_1 - V_2 = 60 \mu V$$

$$V_{CM} = \frac{V_1 + V_2}{2} = 270 \mu V$$

(A)

$$CMRR = 100 = \frac{A_d}{A_{CM}}$$

$$\Rightarrow A_{CM} = 500$$

$$So, V_o = 60 \times 500 + 270 \times 500$$

$$= 141 \text{ mV} + 135 \text{ mV} = 276 \text{ mV} = 0.276 \text{ V}$$

(B)

$$CMRR = 105 = \frac{A_d}{A_{CM}}$$

$$\Rightarrow A_{CM} = \frac{5000}{105} = 5 \times 10^{-3} \times 5 \times 10^{-2}$$

$$V_o = 60 \times 5000 + 5 \times 10^{-3} \times 270$$

$$= 30000 + 4.5 + 30,000$$

$$= 30 \text{ mV} = 0.3 \text{ V}$$

Example : dual iIP balanced OIP Diff. amp's $h_{FE} = 2.8 \text{ K}\Omega$

$$V_{S1} = 70 \mu V \text{ P-P } 1 \text{ KHz}$$

$$V_{S2} = 40 \mu V \text{ P-P } 1 \text{ KHz}$$

$$V_{CC} = 15 \text{ V}; V_{EE} = -15 \text{ V}$$

$$R_C = 10 \text{ K}; R_E = 6.8 \text{ K}; R_S = 100 \text{ }\Omega; h_{FE} = 100$$

Calculate A_D , A_{CM} , Operating Point, CMRR, V_{out} , R_{in} , R_{out}

Sol:

Operating Point

$$I_E = \frac{V_{EE} - V_{BE}}{(R_E + R_S)\beta}$$

$$= \frac{-15 - 0.7}{(6.8K + 100)/100} = 2.30 \text{ mA}$$

$$I_C \approx I_E$$

$$V_{CE} = V_{CC} - I_C R_C + V_{BE}$$

$$= 15 + 0.7 - 4.7K \times 2.30 \text{ m}$$

$$= 4.89 \text{ V}$$

$$A_D = -\frac{h_{FE} R_C}{2(R_S + h_{FE})}$$

$$= -\frac{100 \times 4.7K}{2[2.3K + 100]}$$

$$V_{H.D.E.} = -81.03 \text{ mV}$$

$$A_{CM} = \frac{h_{FE} R_C}{R_S + h_{FE} + 2R_E [1 + h_{FE}]}$$

$$= -\frac{100 \times 4.7K}{2 \times 0.8 + 0.012 \times 100 + 2.3K + 2 \times 6.8K (1 + 100)}$$

$$V_{EB} = V_{CE} + E = 15 + 0.34 = 15.34 \text{ V}$$

$$CMRR = \frac{A_D}{A_{CM}} = 238.32$$

$$R_{in} = 2(R_S + h_{FE})$$

$$= 2[100 + 2.3K] = 5.6 \text{ k}\Omega$$

$$R_{out} = R_C = 4.7K$$

$$V_{out} = A_D V_{id} + V_{cm} A_{CM}$$

$$V_{id} = V_{S1} - V_{S2} = 30 \text{ mV}$$

$$V_{cm} = \frac{30 + 40}{2} = 35 \text{ mV}$$

$$V_{out} = 2.4 \text{ V}$$

