

Hardware description language

Verilog → hardware description language

Why HDL's?

- in software everything is sequential.
- in chip transistors are used not the gate.
RTL → register transfer language.

Abstractions

Behavioral (how I/O will be behave for a particular O/P)



Data flow (boolean expression)



Structural (if we want 4 bit adder by using one struc. and connect them we can make it)



Switch (in SW NAND gate → How many CMOS are required)

- Behavioral methods are more preferable for design the chip.

Advantages of HDL :

- designs can be described at various level of abstraction.
 - Top-down approach
 - functional simulation early in design flow
 - automatic conversion of HDL to gates
 - testing of various design implementation
 - design reuse
- VHDL → very high speed integrated circuit hardware description language.
- verilog HDL (verification of logic)

Digital SIS design flow :

(from slide)

synthesis → our design to technology design.

Types of simulation:

- ① Event-driven : when a change on an i/p causes a change on o/p, which cause a further change on another i/p

Verilog HDL :

- verification of logic
- used in simulation and synthesis.
- Verilog is case sensitive.
- Keywords are lowercase
- statement end with semicolon.

Verilog program structure:


module < module_name > (Port list)

- ① port declaration

(How much i/Ps or o/Ps, clock, enable Pin are in coming in the port decl)

- ② data type declaration
data type int, float

Wise & register

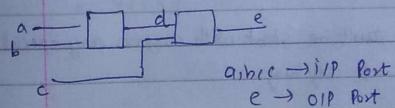

a,b,c → can't write bcoz they don't have any value.

d → having the value register

③ Circuit functionality
(logic of program)

④ Time specification
end module

for example:

```
module and2(a,b,C); * module useless;
  input = a,b;
  input in;
  O/P = C;
  assign C = a & b;
  assign out = ~in;
  end module
```

operator	Name	* module useless;
&	and	initial keyword
	OR	# Display("Hello!");
^	XOR	endmodule
&&	NAND	
~	NOR	
~&&	NOT XOR	
~	NOT	

- module name can't be start with any no. any special char and it can be anything.

Number System

$$N = 2, 8, 10, 16$$

↓ octal ↓ hexadecimal
binary decimal

$$\text{any base} \rightarrow \text{decimal}$$
$$[a_n g^n + a_{n-1} g^{n-1} + a_{n-2} g^{n-2} + \dots + a_1 g + a_0]$$

↓ base position

for example

$$(1010.011)_2 \rightarrow (\quad)_{10}$$

$$\begin{aligned} & 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 0 \times 2^0 + 0 \times 2^{-1} + 2^{-2} + 2^{-3} \\ & = 8 + 0 + \frac{1}{4} + \frac{1}{8} \\ & = 10 + \frac{3}{8} = 10 + 0.375 \\ & = 10.375 \end{aligned}$$

$$(1021.2)_5$$

$$4 \times 5^3 + 2 \times 5^2 + 1 + 2 \times \frac{1}{5}$$

$$= 511.4$$

$$(B65F)_{16}$$

$$\begin{aligned} & 11 \times 16^3 + 6 \times 16^2 + 5 \times 16^1 + 15 \\ & = 46687 \end{aligned}$$

Method ①

Why we do complement to
do subtraction?

Page: _____
Date: _____

(41) $\rightarrow ()_2$

divided by that particular base, which we required
to convert

9's and (9-1)'s complement addition

for ex: i) $72532 - 03250$

$$\begin{array}{r} M \quad N \\ 03250 \rightarrow 96749 \\ +1 \\ 10's \text{ comp} \rightarrow 96750 \end{array}$$

$$\begin{array}{r} 72532 \\ + 96750 \\ \hline 169282 \end{array}$$

carry is ignored

- if carry is generated \rightarrow ignored
- if carry is not generated then take the 9's complement of the ans and put -ve sign in front of the ans.

ii) $1010100 + 1000100 = 0011000$

$$\begin{array}{r} + 1000100 \\ \hline 00011000 \end{array}$$

Ignored

(9-1)'s complement method:

iii) $1010100 - 1000100$ (9's complement)

$$\begin{array}{r} 1000100 \rightarrow 2's \text{ comp.} \\ 0111011 \\ +1 \\ \hline 0111100 \end{array}$$

$$\begin{array}{r} 1010100 \rightarrow m \\ + 0111100 \rightarrow 2's \\ \hline 0010000 \rightarrow \end{array}$$

Ignored

By method 2's 8
(9-1)'s ans would be
same.

(9-1)'s complement:

$$\begin{array}{r} 1010100 \rightarrow m \\ + 0111011 \rightarrow 2's \text{ comp.} \\ \hline 00001111 \\ +1 \\ \hline 00010000 \rightarrow \end{array}$$

- if carry is generated \rightarrow add carry to LSB position of ans.
- if carry is not generated \rightarrow take (9-1)'s comp. of ans and put (-) sign.

Sign magnitude	2's comp.	1's comp.
1) +51	00110011	01100111
	+001101	-001100

ii) -51 1110011 001101 001100

* sign bit same rethegi

* 2's and its complement of
+ve no. can't be find
its also same as binary representation of 2's no.

$$\begin{array}{r}
 3 | 51 \\
 2 | 25 \quad 1 \\
 2 | 12 \quad 1 \\
 2 | 6 \quad 0 \\
 2 | 3 \quad 0 \\
 \hline
 & 1 \quad 1 \\
 & 0 \quad 1
 \end{array}
 \quad (51)_{10} = (110011)_2$$

Ex: +73.75 12 bit 2's comp form
-73.75

$$\begin{array}{r}
 3 | 73 \\
 3 | 36 \quad 1 \\
 3 | 18 \quad 0 \\
 3 | 9 \quad 0 \\
 3 | 4 \quad 1 \\
 \hline
 & 2 \quad 0 \\
 & 1 \quad 0 \\
 & 0 \quad 1
 \end{array}
 \quad \begin{array}{l}
 75 \times 2 = 1.5 \\
 5 \times 2 = 1.0 \\
 0 \times 2 = 0
 \end{array}
 \quad (01001001.1100)_2$$

$$\textcircled{-73.75} \rightarrow 01001001.1100$$

$$\begin{array}{r}
 10110110.0011 \rightarrow 1's \text{ comp.} \\
 \downarrow \quad \quad \quad 0100 \\
 +1 \quad +1 \\
 \hline
 10110111.0100
 \end{array}$$

for 2's comp treat integral and fractional part separately.

$$\begin{array}{r}
 1100 \leftarrow 01001001 \leftarrow \\
 0100 \quad 10110111 \text{ (by flipping)}
 \end{array}$$

$$\begin{array}{r}
 8 \times 8 \quad 110 \longdiv{101101} (111.1 \\
 \quad \quad \quad 110 \\
 \quad \quad \quad 1010 \\
 \quad \quad \quad \overline{1011} \\
 \quad \quad \quad 1011 \\
 \quad \quad \quad \overline{000}
 \end{array}$$

$$\begin{array}{r}
 101 \longdiv{110^0101111} (101011 \\
 \quad \quad \quad 101 \\
 \quad \quad \quad \overline{00100} \\
 \quad \quad \quad 101 \\
 \quad \quad \quad \overline{0011} \\
 \quad \quad \quad 101 \\
 \quad \quad \quad \overline{000}
 \end{array}$$

$$\text{Ex: } 1101 \times 110$$

$$\begin{array}{r}
 101 \\
 \times 110 \\
 \hline
 000 \\
 11010 \\
 \hline
 1001110
 \end{array}$$

Why much

Date: 10-juin

Page:
Date:

Boolean Algebra:

Demorgans $\overline{A+B+C+\dots} = \overline{A}\cdot\overline{B}\cdot\overline{C}\dots$

$$A\cdot B\cdot C = \overline{A} + \overline{B} + \overline{C}$$

OR: $A+0 = A$ AND: $A\cdot 0 = 0$
 $A+\overline{A} = 1$ $A\cdot 1 = A$
 $1+A = 1$ $A\cdot\overline{A} = 0$
 $A+A = A$ $A\cdot A = A$

commutative: $A+B = B+A$ $A\cdot B = B\cdot A$

Associative: $(A+B)+C = A+(B+C)$ $(A\cdot B)\cdot C = (A\cdot B\cdot C)$

$$\begin{aligned} A(A+C) &= AB+AC \\ A+BC &= (A+B)(A+C) \\ \overline{A} &= A \\ A+AB &= A \quad ? \text{ Absorption law} \\ A(A+B) &= A \end{aligned}$$

Example:

i) $A[B+C(\overline{AB}+\overline{AC})]$

$$\overline{AB} + \overline{AC}$$

$$A[B+C(\overline{A}+\overline{B})(\overline{A}+\overline{C})]$$

$$A(B+\overline{C}(\overline{A}+\overline{B}))$$

$$A(B+\overline{AC})$$

$$AB$$

② $A\overline{B}C + A\overline{B}\overline{C} + A\overline{B}C$
③ $\overline{A}\overline{C} + B\overline{C} + \overline{A}BC + ABC$
④ $A\overline{B}\overline{D} + A\overline{B}C\overline{D} + ABC\overline{D} + A\overline{B}\overline{D} + \overline{A}BCD$
⑤ $BC + A\overline{C} + AB + BCD$
⑥ $(A+C+D)(A+\overline{C}+D)(A+\overline{C}+D)(A+C+\overline{D})(A+\overline{C}+\overline{D})$
⑦ $AD + A\overline{B}\overline{C} + \overline{B}C\overline{D} + \overline{A}CD + \overline{A}BC\overline{D}$

⑧ $A\overline{B}C + A\overline{B}\overline{C} + ABC$
 $A(\overline{B}C + B\overline{C} + \overline{B}C + BC)$
 $A(B+C)$

⑨ $\overline{A}\overline{C} + B\overline{C} + BC$
 $\overline{A}\overline{C} + B$

⑩ $A\overline{B}\overline{D} + A\overline{B}\overline{D} + A\overline{B}\overline{D} + \overline{A}BCD$
 $A\overline{B}\overline{D} + A\overline{B}\overline{D} + \overline{A}BCD$
 $A\overline{B} + \overline{A}BCD$

⑪ $BC + A\overline{C} + AB(C+\overline{C})$
 $= ABC + A\overline{B}\overline{C} + A\overline{C} + BC$
 $= BC + A\overline{C}$

$$A + \bar{B}CD$$

(6) $\begin{aligned} & (A+B)(A+C) = A+BC \\ & (A+C+D)(A+C+\bar{D})(A+\bar{C}+D)(A+\bar{B}) \\ & (A+C)(A+\bar{C}+D)(A+\bar{B}) \\ & (A+\bar{B}C)(A+\bar{C}+D) \\ & A+(BC)(\bar{C}+D) \\ & A + \bar{B}C \cdot \bar{C} + \bar{B}CD \\ & A + \bar{B}CD \end{aligned}$

(7) $AD + A\bar{B}\bar{C} + \bar{B}C\bar{D} + \bar{A}CD + \bar{A}B\bar{C}\bar{D}$

SOP & POS:

x	y	z	min term	max term
0	0	0	$\bar{x}\bar{y}\bar{z}$ m ₀	$x+y+z$
0	0	1	$\bar{x}\bar{y}z$	$x+y+\bar{z}$
0	1	0	$\bar{x}yz$	$x+\bar{y}+z$
0	1	1	$\bar{x}yz$	$x+y+\bar{z}$
1	0	0	xyz	$\bar{x}+y+z$
1	0	1	$x\bar{y}z$	$\bar{x}+y+\bar{z}$
1	1	0	$x\bar{y}\bar{z}$	$\bar{x}+\bar{y}+z$
1	1	1	xyz m ₇	$\bar{x}+\bar{y}+\bar{z}$

NAND $\rightarrow A \cdot B \rightarrow$ min term (more preferable)

NOR $\rightarrow \overline{A+B} \rightarrow$ max term

Example:

(1) $F = A + \bar{B}C$

$$\begin{aligned} A(B+\bar{B}) &= (AB+A\bar{B})(C+\bar{C}) \Rightarrow ABC + A\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C \\ BC(A+\bar{A}) &= A\bar{B}C + \bar{A}\bar{B}C \end{aligned}$$

$$\begin{aligned} A + \bar{B}C &= ABC + AB'C + ABC' + AB'C' + A'B'C + A'B'C' \\ &= \sum m(7, 5, 6, 4, 1) \rightarrow \text{min term} \\ &\text{max term } (0, 2, 3) \end{aligned}$$

(2)

$$\begin{aligned} F &= xy + \bar{x}z \\ &= y(x+z) + \bar{x}z(x+y) \\ &= xy + xyz + \bar{x}z + xyz \end{aligned}$$

Ques:

$$\begin{aligned}
 & xy + \bar{x}z \\
 & = (xy + x')(x'y + z) \\
 & = (x+x')(y+y')(x+z)(y+z) \\
 & = (x'+y)(x+z)(y+z) \\
 & = (x'+y+z)(x'+y+z)(x+y+z)(x+y+z)(x+y+z) \\
 & \quad (x'+y+z)
 \end{aligned}$$

$$\begin{aligned}
 (x'+y)(x+y) &= x' + y + z \cdot \bar{z} \\
 &= (x'+y+z)(x'+y+z)
 \end{aligned}$$

SOPs: $xy + \bar{x}z$


$$xy = xy\bar{z} + xy\bar{z}$$

$$\bar{x}z = \bar{x}yz + \bar{x}y\bar{z}$$

$$xy + \bar{x}z = \Sigma m(7, 6, 3, 1)$$

K-map 0
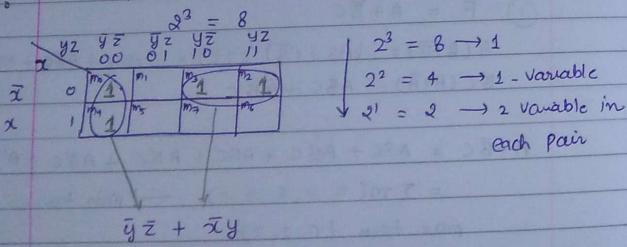
$$F = x'y\bar{z} + x'y\bar{z}' + x'y'\bar{z}' + x'y'\bar{z}$$



4-Variate K-map:

$$F(w, x, y, z) = \Sigma m(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$

wx	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
$\bar{w}\bar{x}$	1	1	0	1
$\bar{w}x$	1	1	0	1
$w\bar{x}$	1	1	0	1
wx	1	1	0	0

ASINVARA
HITHAIKA
ERF HEN

1 pair of 8 = \bar{y}
2 pairs of 4 = $\bar{w}\bar{z}, \bar{x}\bar{z}$

$$F = \bar{y} + \bar{w}\bar{z} + \bar{x}\bar{z}$$

$$= (\bar{y} + \bar{z})(\bar{y} + \bar{w} + \bar{x})$$

Ex:- $F(A, B, C, D) = \Sigma m(0, 1, 2, 5, 8, 9, 10)$

pos & sop

	$\bar{C}D$	$C\bar{D}$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	1	1	0	1
$\bar{A}B$	D	1	0	0
$A\bar{B}$	1	D	0	0
AB	1	1	0	1


$$\begin{aligned}
 F &= \bar{B}\bar{C} + \bar{B}\bar{D} + \bar{A}\bar{C}D \rightarrow \text{min term SOP} \\
 &= (\bar{A}+\bar{B})(\bar{C}+\bar{D})(D+\bar{B}) \rightarrow \text{max term POS}
 \end{aligned}$$

Ex:- $F(w, x, y, z) = \Sigma m(1, 3, 7, 11, 15) + d(0, 2, 5)$

	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
$\bar{w}\bar{x}$	X	1	1	X
$\bar{w}x$	0	X	1	0
$w\bar{x}$	0	0	1	0
wx	0	0	1	0

$$\begin{aligned}
 F &= yz + \bar{w}\bar{x} \rightarrow \text{SOP} \\
 &= z(y + \bar{w}) \rightarrow \text{POS}
 \end{aligned}$$

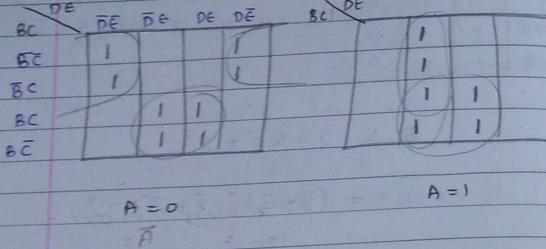Ex:- $F(A, B, C, D, E) = \sum(0, 2, 4, 6, 9, 11, 13, 15, 17, 21, 25, 27, 29, 31)$



$$F = \overline{A}BE + A\overline{B}E + A\overline{B}\overline{E} + \overline{A}\overline{B}\overline{E}$$

$$= BE$$

Map entered variable :-

	A	B	C	D	E	F	G(O/P)
m_0	0	0	0	0	X	X	1
m_1	0	0	0	1	X	X	\leftarrow don't care O/P
m_2	0	0	1	0	X	X	1
m_3	0	0	1	1	X	X	1
m_5	0	1	0	1	(1)	X	1
m_7	0	1	1	1	(1)	X	1
m_9	1	0	0	1	X	(1)	1
m_{11}	1	0	1	1	X	X	1

m_{12}	1	1	0	0	X	X	X	\leftarrow
m_{13}	1	1	0	1	X	X	X	\leftarrow
m_{15}	1	1	1	1	X	X	1	

$$G(A, B, C, D, E, F) = m_0 + m_5 + m_2 + m_3 + m_{15} + E m_7 + F m_9 + m_{11} + d(m_1, m_2, m_3)$$

max. term is $m_{15} \rightarrow$ So \leftarrow variable K-map

\overbrace{AB}^{CD}	1	X	1	1
	E=1	E		
	X	X	1	
	F		1	

Standard equation :-

$P \rightarrow$ is the no. of variables

$$F = (M_{S0} + P_1 \cdot M_{S1} + P_2 \cdot M_{S2} + \dots + P_n \cdot M_{Sn})$$

it would be our ans.
for upper given
problem

M_{S0} is the when E & F are not
there and solve the K map
solution.

	CP	$C\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
M_{S0}	A'B'	1	X	1	1
	$\bar{A}B$				
	A'B	X	X	1	
	$\bar{A}B$				

- do not consider
any variable (E & F)

$$M_{S0} = A'B' + ACD$$

	CP	$C\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
M_{S1}	A'B	X	X	X	X
		1	1		
	X	X	X	X	

$$P_1 M_{S1} = (\bar{A}D)E$$

- ↳ 1 is replaced by don't care
- ↳ don't care same as
- ↳ another variable is not present
- ↳ and that particular variable is replaced by 1

M_{S2}	X	X	X	X	
	X	X	X		
	1	X			

$$P_2 M_{S2} = ADF$$

$$\text{So; } F = A'B' + ACD + \bar{A}DE + ADF$$

$$\begin{aligned} \text{Example } Z(A,B,C,D,E,F,G) = & \sum m(2,5,6,9) + \sum d(1,3,13,14) \\ & + E(m_{11} + m_{12}) \\ & + F(m_{10}) + G(m_0) \end{aligned}$$

$$Z = M_{S0} + P_1 M_{S1} + P_2 M_{S2} + P_3 M_{S3}$$

	CP	$C\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
	A'B	G	X	X	1
			1		1
	A'B	E	X		X
	$\bar{A}B$	-	1	E	F

M_{S0}	X	X	1	
	1	X		
	X		X	

$$M_{S0} = \bar{C}D + \bar{A}C\bar{D}$$

M_{S1}	X	X	X	
	1	X		X
	X		1	

$$P_1 M_{S1} = E[A\bar{B}\bar{C} + \bar{A}\bar{B}D]$$

M_{S2}	X	X	X	
	X		X	
	X		X	
	X		1	

$$P_2 M_{S2} = F C\bar{D}$$

M_{S3}	1	X	X	X	
		X		X	
		X		X	
		X		1	

$$P_3 M_{S3} = G\bar{A}\bar{B}$$

$$Z = C'D + A'CD' + ABC'E + EBD' + FCD' + GA'B$$

Example 8

$$G = C'E'F + DEF + AD'E'F' + BC'E'F + AD'EF$$

Solve using map entered method.

Sol 8

two variable is A & B

$$\begin{aligned}
 &= C'E'FD + C'E'F\bar{D} + CDEF + \bar{C}DEF + \\
 &\quad A[C'D'E'F + C'D'E'F'] + B[C'D'E'F + C'DE\bar{F}] \\
 &\quad + A[C'D'E\bar{F} + CDE\bar{F}] \\
 &= 0101 + 0001 + 1111 + 0111 + B[0001 + 0101] \\
 &\quad + A(1000 + 0000 + 0010 + 1010) \\
 &= \sum m(1, 5, 7, 15) + B(1+5) + A(0+2+8+10) \\
 &= m_1 + m_3 + m_5 + m_{15} + Bm_5 + A(m_0 + m_2 + m_8 + m_{10}) \\
 &= m_1 + m_3 + m_5 + m_{15} + A(m_0 + m_2 + m_8 + m_{10}) \\
 &= \sum m(1, 5, 7, 15) + A(m_0 + m_8 + m_{10} + m_2)
 \end{aligned}$$

CD	EF	EE	EF	EE
$\bar{C}\bar{D}$	A	1	A	
$\bar{C}D$	1	1	1	
CD	1		1	
$C\bar{D}$	A		1	A

$$m_5 = \bar{C}\bar{E}F + DEF$$

m₅

1	x	1
	x	x
0	x	

$$m_5 = \bar{E}\bar{D}$$

$$F = \bar{C}\bar{E}F + DEF + A\bar{E}\bar{D}$$

Example 8

$$Z = A'B'C'DF' + A'CD + A'B'CD'E + BCDF'$$

Sol 8 two variables are E & F

$$\begin{aligned}
 Z &= A'B'CDF' + A'BCD + A'B'CD + A'B'C'D'E \\
 &\quad + ABCDF' + \bar{A}BCDE'
 \end{aligned}$$

$$\begin{aligned}
 &= (0011)F + 0111 + 0011 + (0010) \\
 &\quad F'(1111) + (0111)F
 \end{aligned}$$

$$\begin{aligned}
 &= F_1 m_3 + m_3 + m_3 + E m_2 + F' m_{15} + m_3 F' \\
 &= m_3 + m_3 + E m_2 + F' m_{15}
 \end{aligned}$$

	1	E
	1	F'

$$m_5 = \bar{A}E\bar{D}$$

$$E m_5 = E(\bar{A}\bar{B}C)$$

$$F' m_5 = F'(\bar{C}BCD)$$

$$Z = \bar{A}CD + \bar{A}\bar{B}CE + BCD\bar{F}$$

8421

$$\text{Ex: } W = \bar{A}\bar{B}\bar{E}F + AEF + \bar{B}F\bar{E} + \bar{A}\bar{B}\bar{C}EF + ADF\bar{E} + \bar{A}\bar{B}\bar{C}\bar{E}\bar{F}$$

Sol: Two variables are C & D

$$\begin{aligned} &= \bar{A}\bar{B}\bar{E}F + A\bar{B}E\bar{F} + A\bar{B}EF + \bar{A}\bar{B}F\bar{E} + A\bar{B}F \\ &\quad + \bar{A}\bar{B}EF \cdot C + A\bar{B}EF \cdot D + \bar{A}\bar{B}E\bar{F} \cdot D + \bar{A}\bar{B}CE \\ &= m_5 + m_{14} + m_{10} + m_9 + m_7 + m_3 \cdot C \\ &\quad + m_4 \cdot D + (m_6 \cdot D + m_0 \cdot \bar{C}) \end{aligned}$$

$\bar{A}\bar{B}$	$\bar{E}F$	$E\bar{F}$	$E\bar{F}$	$\bar{C}\bar{F}$	$m_0(\bar{C}+D) \rightarrow z(\bar{C}+D)$
$\bar{A}B$	($\bar{C}+D$)	1		C	
$A\bar{B}$	D	1			
AB				1	
$A\bar{B}$	-	1		1	

assume $\bar{C}+D = z$

$$m_{50} = B\bar{E}F + A\bar{E}F \quad AEF + \bar{A}\bar{E}F + \bar{B}\bar{E}F$$

$$D.m_{51} = D \cdot \bar{A}\bar{B}\bar{E}$$

$$C.m_{52} = C \cdot \bar{A}\bar{B}\bar{E}F$$

$$z.m_{53} = (\bar{C}+D) \cdot \bar{A}\bar{B}\bar{E}F$$

$$\begin{aligned} W = & AEF + \bar{A}\bar{E}F + \bar{B}\bar{E}F + \bar{A}\bar{B}\bar{E}D + \bar{A}\bar{B}FC \\ & + \bar{A}\bar{B}\bar{C}\bar{E} + \bar{A}\bar{B}\bar{E}D \end{aligned}$$

Combinational Circuit:

Ex:

A Hacker does not want anyone to track his data so he wants to design a secure he wants his signal to be transmitted in 16 diff line one by one. at Rx, he wants his data back as it was transmitted. He also wants to make a circuit that helps him in the selecting the channel out of available 16 channels on which he transmit data. This ckt will accept two bit binary no. and the channel which is Tx to the addition of this no. for ex: if two no. are 011 & 100 \rightarrow addition will be 1001 then channel line will be Tx1 the same ckt with the same IP available at the Rx to get back original data back. As an ec engineer design the ckt in the LSI form from to solve hacker problem.

Sol:

PHASING
HARDWARE
VERE

Example: Mr. X is the scientist and wants to design a digital modulator. the I/P in the modulator comes from the digital carrier genr and modulating signal coming from the freq. genr. Modulating signal is totally independent of the carrier and change irrespective of it as any analog signal. In the carrier genr six diff^r OIP are available. So one can generate six diff^r freq. Those freq. are 50 Hz, 75 Hz, 100 Hz, 125 Hz, 150, 175 Hz. And adder ckt is also available with 3-bit OIP namely a_0, a_1, a_2 . The modulator will be provided the carriers signal from the available 6 freq. depending upon the ans of adder. More-ever adder ckt is not simple adder. Mr. X wants OIP in binary form. I/P to the adder ckt is the $xs-3$ form. An ec eng. solve the Mr. X's problem.


Encoder:

- interrupt priority encoder
- 2^n inputs, n outputs


Decoder:

- n inputs, 2^n outputs

multiPlexer
many to one

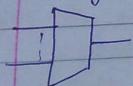

De-mux
one to many

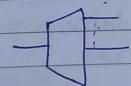


Octal to binary Encoder:

	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	A	B	C
1	0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	1	0	0	1
1	0	0	0	0	0	0	1	0	0	1	0
1	0	0	0	0	0	0	1	0	0	1	1
1	0	0	0	0	0	0	1	0	0	1	1
1	0	0	0	0	0	0	1	0	0	1	1
1	0	0	0	0	0	0	1	0	0	1	1
1	0	0	0	0	0	0	1	0	0	1	1


$$A = \overline{D_4} + \overline{D_5} + D_6 + D_7$$

$$B = D_2 + D_3 + D_6 + D_7$$


$$C = D_1 + D_2 + D_5 + D_7$$

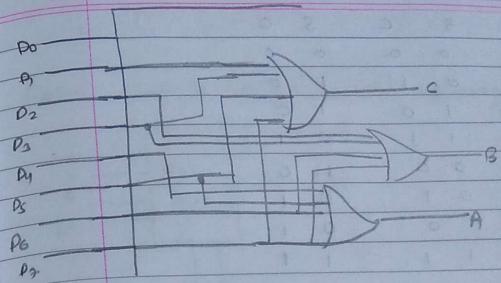

: Design a 2x1 mux internal struc:

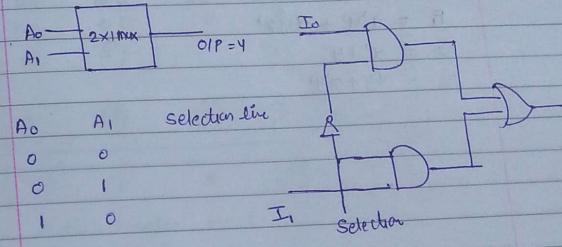

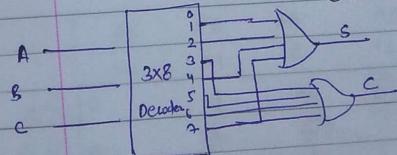Design a full adder using 3 to 8 line decoder and OR gate:
 $S(A, B, C) = \Sigma(1, 2, 4, 7)$
 $C(A, B, C) = \Sigma(3, 5, 6, 7)$



Bubble and \rightarrow NOR
 Bubble OR \rightarrow NAND

	A	B	C	S	C
0	0	0	0	0	0
1	0	0	1	1	0
2	0	1	0	1	0
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	0	1
6	1	1	0	0	1
7	1	1	1	1	1

Ex8 implement this func using decoder and NAND gate


$$F_1 = z'y' + 2yz'$$

$$F_2 = z'y$$

$$F_3 = 2xy + x'y$$

Why in RTL view \rightarrow all if else conditions are converted into Mux

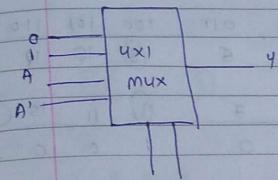Ex8- $f(A, B, C) = \Sigma(1, 3, 5, 6)$ by using 4x1 mux



	B C		I_0	I_1	I_2	I_3
	$B'C'$	$B'C$	$B'C'$	BC'	BC	BC'
0 A'	0	0	01	10	10	10
1 A	1	1	01	10	01	01
			1	2	3	4
			5	6	7	8
p/p	0	1	A	A'		

if two circles $\rightarrow 1$

if not circles $\rightarrow 0$

if one circle \rightarrow irrespective valueable


- $BB \rightarrow$ Selection line

	AB'	$A'B$	AB'	AB	
	00	01	10	11	
$C'(0)$	0	2	4	6	
$C(1)$	1	3	5	7	
	C	C	C	C'	

Diagram of a 4x1 multiplexer (MUX) with inputs A, B, and C. The control input S has three connections: one to the MSB of the address, one to the second bit, and one to ground.

Ex 8 $F(A, B, C, D) = \Sigma(0, 1, 3, 4, 8, 9, 15)$ using 8x1 MUX

	$A\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$\bar{A}BC$	$AB\bar{C}$	ABC
000	001	010	011	100	101
0	2	4	5	8	10
D	0	1	3	7	9
D	1	D	D	0	1
				0	0
				D	D

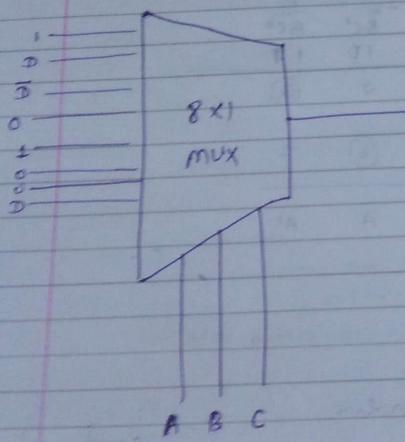

Using 2 (4x1 → mux)

$A'B'$	I_0	I_1	I_2	I_3
0	0	1	2	3
N.B	4	5	6	7
AB'	8	9	10	11
AB	12	13	14	15

A B C D

0 0 0 0
0 0 0 1
0 0 1 0
0 0 1 1
0 1 0 0
0 1 0 1
0 1 1 0
0 1 1 1
1 0 0 0
1 0 0 1
1 0 1 0
1 0 1 1
1 1 0 0
1 1 0 1
1 1 1 0
1 1 1 1

