

Ideal Characteristics of amplifier:

ideal : Gain = ∞

BW = ∞

$Z_{in} = \infty$

$Z_{out} = 0$

Slew rate : change of output w.r.t $\frac{\text{time}}{\text{input}} = \infty$

practically

Gain = finite

BW = finite



Z_{in} = finite ($\sim 100\Omega$)

Z_{out} = ($< 100\Omega$)


SR = (0.5 - 100 V/ μ sec)

- Op-amp can be used for a variety of applications, such as ac & dc amplification, comparator, oscillators, active filters, regulators

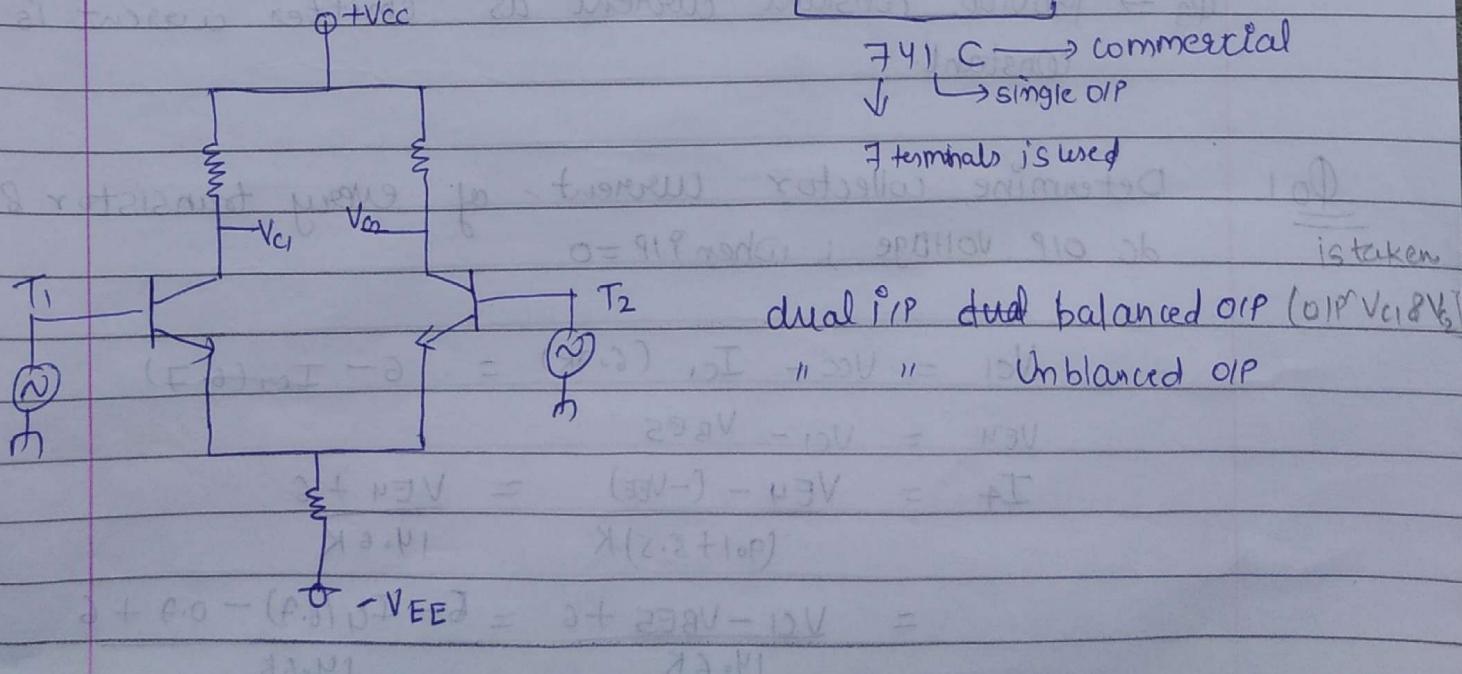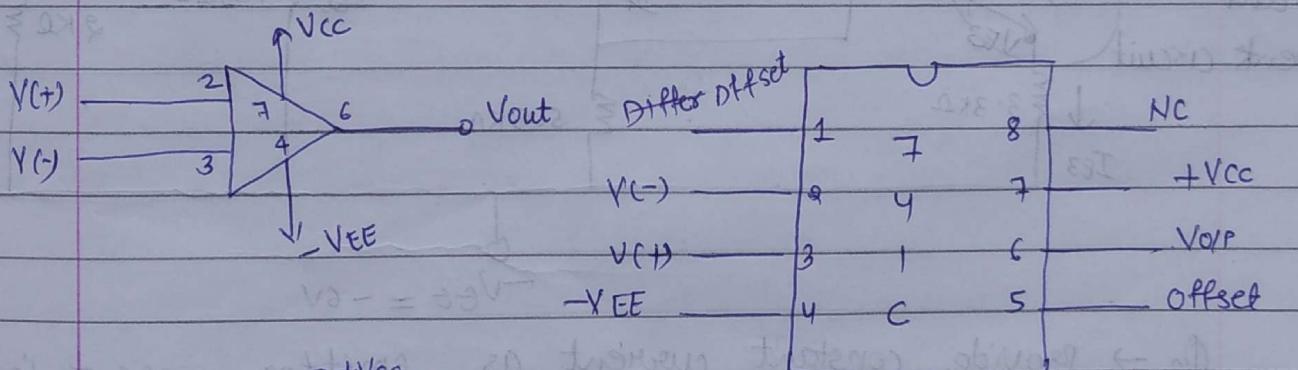
Block Diagram & circuit symbol of OP-amp:



(6) Block Diagram of a typical op-amp

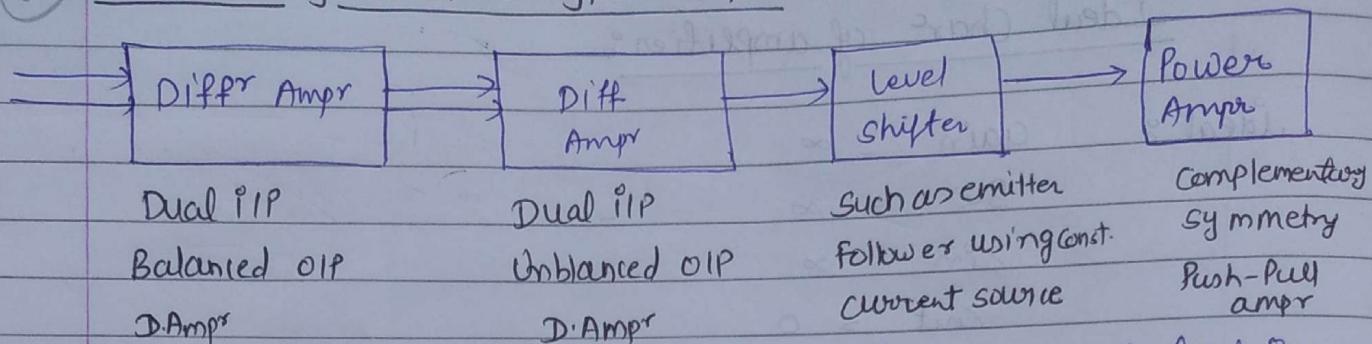

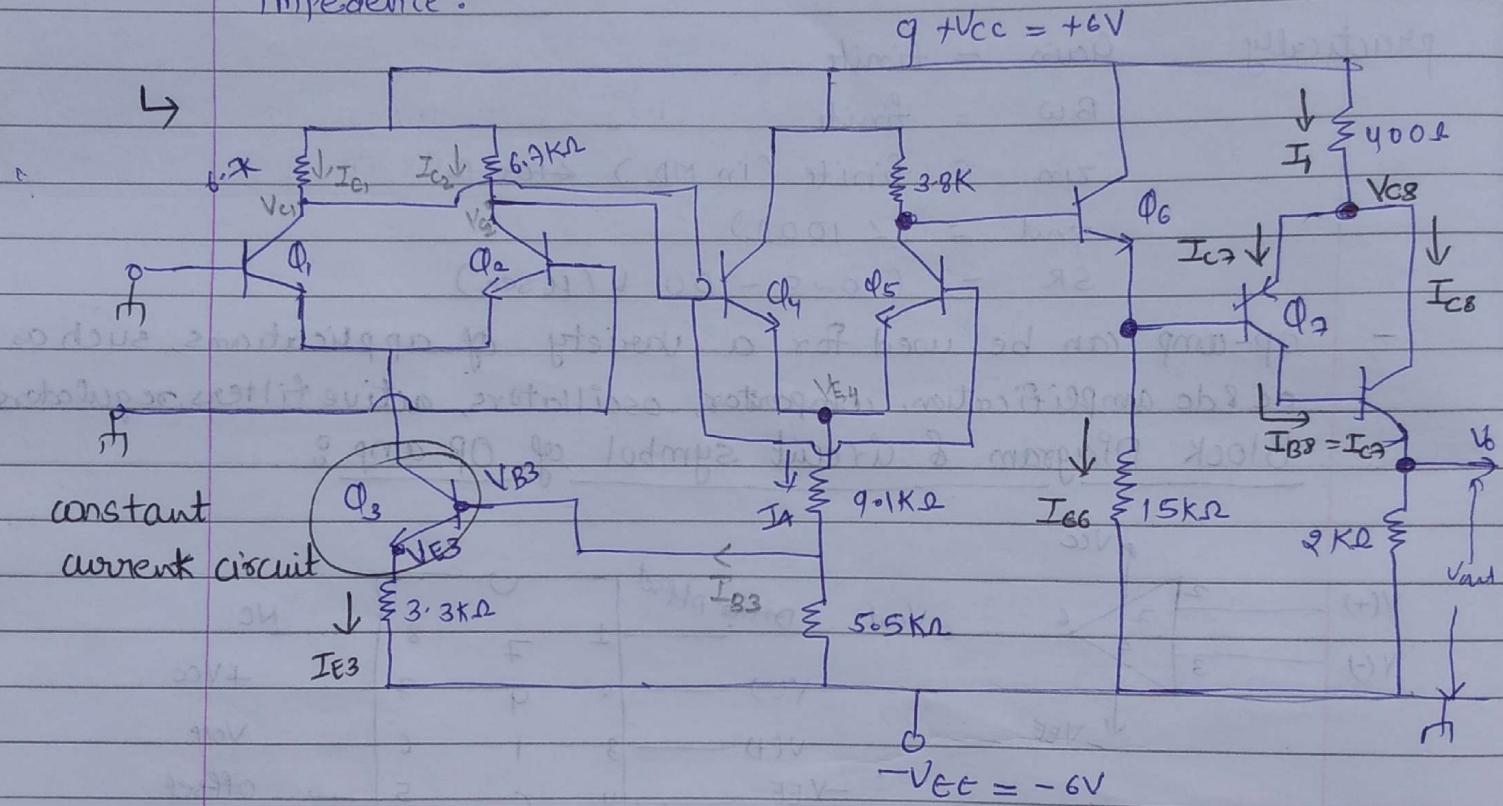* Purpose of two differential amplifiers is high gain & high PIP impedance.



$\Phi_3 \rightarrow$ provide constant current as emitter current is constant.

Φ_1 Determine collector current of every transistor & dc oip voltage ; when PIP=0

$$V_{C1} = V_{CC} - I_{C1} (6.7K) = 6 - I_{C1} (6.7)$$

$$V_{E4} = V_{C1} - V_{BE5}$$

$$I_4 = \frac{V_{E4} - (-V_{EE})}{(9.01 + 5.5)K} = \frac{V_{E4} + 6}{14.6K}$$

$$= \frac{V_{C1} - V_{BE5} + 6}{14.6K} = \frac{6 - I_{C1}(6.7) - 0.7 + 6}{14.6K}$$

$$I_4 = \frac{11.3 - (6.7K) I_C}{14.6K}$$

$$V_{B3} = (5.6K) I_4 - V_{EE} = \frac{5.5}{14.6} [11.3 - 6.7K I_C] + 6.09$$

$$V_{E3} = V_{B3} - V_{BE3} = 10.25 - 2.52K I_C$$

$$= V_{B3} - 0.7 = 9.55 - 2.52K I_C$$

$$V_{E3} = (5.5K) I_4 + (-6) - 0.7$$

$$I_{E3} = \frac{V_{E3} - (-V_{EE})}{3.3K\Omega} = \frac{3.55 - 2.52K I_C}{3.3K\Omega}$$

$$I_{E3} = 0.07 \times 10^{-3} - 0.25 I_C$$

$$I_{E3} = 2 I_C$$

$$2.75 I_C = 1.07 \times 10^{-3}$$

$$I_C = 388 \times 10^{-6} A$$

$$R_{E1} = 900$$

$$R_{E1} > = 900$$


$$388 \times 10^{-6} A = 388 \times 10^{-6} \times 900$$

$$350 \times 10^{-3} V =$$

$$350 \times 10^{-3}$$

using voltage divider rule obtain the biasing voltages

$$2.0V = 2.0V \quad 2.0V = 90$$

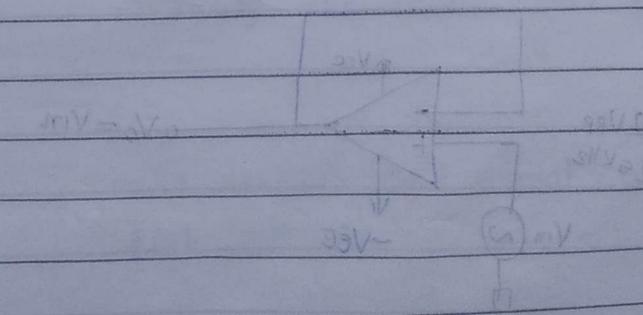


10)

OP-amp IC-741 parameters

OP-amp is linear IC's and 741 IC is general purpose IC

Input offset voltage :

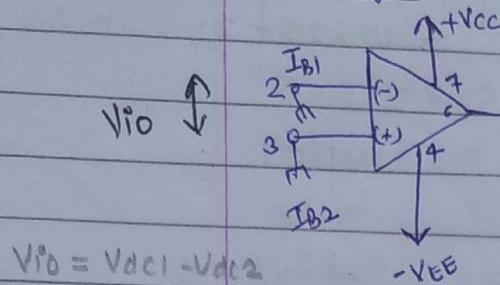


$$V_o = A(V_1 - V_2)$$

$$V_{IO} = V_{DC1} - V_{DC2}$$

- IIP offset is dc voltage

for IC 741 $V_{IO} = 5mV / 6mV$

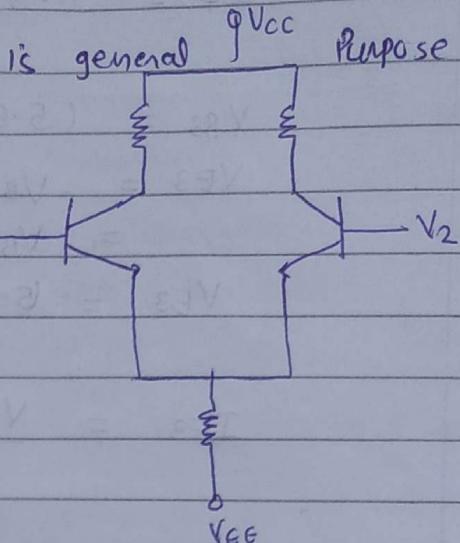

IIP offset current :

I_{B1} & I_{B2} are in nA.

IIP offset current $I_{IO} = |I_{B1} - I_{B2}| = 200nA$

Bias Current $I_B = I_{B1} + I_{B2} = 500nA$

IIP capacitance : $C = 1.4PF (741C)$

$$R_{IIP} = 1M\Omega$$

$$R_{OIP} = < 100\Omega$$


Open loop voltage gain = OIP Voltage
differ iIP voltage

$$= \frac{V_O}{V_{ID}}$$

$$= 2 \times 10^5$$

Slew rate \rightarrow is defined in data sheet at unity gain.
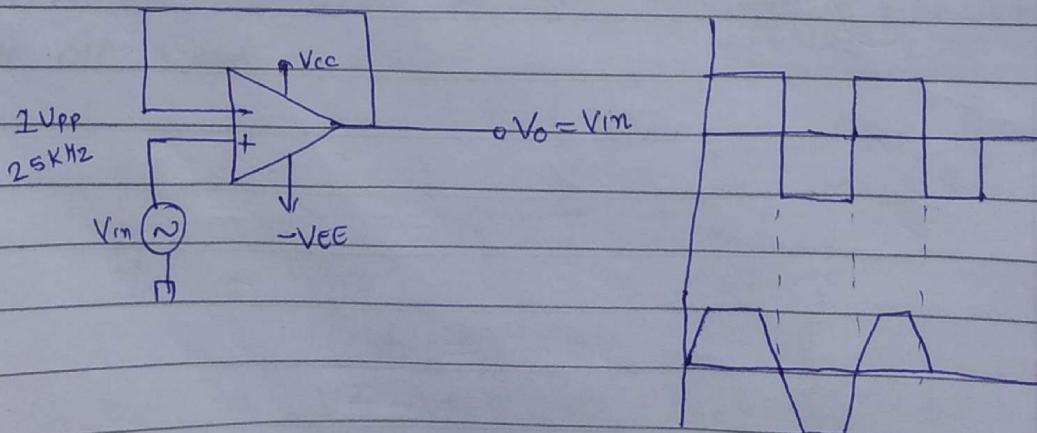
$$SR = \frac{dV_{out}}{dt} \text{ V/μs} = 0.5 \text{ V/μs}$$




$\text{I}_{\text{CM}} = \pm 13\text{V}$ $\text{I}_{\text{SC}} = 2.5\text{mA}$ Power consumption = 8.5mW
 $\text{CMRR} = 90\text{dB}$ $\text{V}_{\text{IO}} = 6\text{mV}$ Slew rate = $0.5\text{V}/\text{MS}$
 $\text{SVRR} = 150\mu\text{V}/\text{V}$ $\text{I}_{\text{IO}} = 200\text{nA}$
 Large signal gain = 2×10^5 $\text{I}_S = 2.8\text{mA}$

Output Voltage

$$|V_{\text{O}}| < |V_{\text{cc}}|$$

$$V_{\text{out}} = \pm 13\text{V}$$

CMRR:

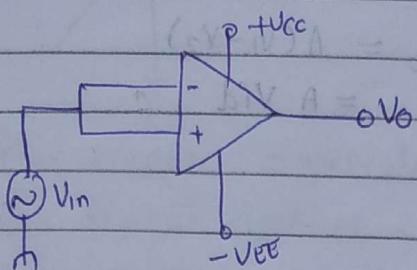

$$V_O = A_d (V_1 - V_2) + A_c V_C$$

practically $A_d = \infty$ & $A_c = 0$

$$\text{CMRR} = \frac{A_d}{A_c} = 90\text{dB}$$

$$V_C = \frac{V_L + V_2}{2}$$

SVRR & PSRR:

SVRR \rightarrow Supply voltage rejection ratio

PSRR \rightarrow Power supply rejection ratio

$$[\text{SVRR} = \text{PSRR}] = \frac{\Delta V_{\text{IO}}}{(\Delta V - \Delta V)} \text{ mVolts/Volt}$$

$\Delta V \rightarrow \text{supply voltage}$

$$(\text{SVRR})_{\text{dB}} = \left(\frac{1}{\Delta V / \Delta V} \right)$$

Short circuit Protection:

$$I_{\text{SC}} = 2.5\text{mA}$$

Power dissipation $I_{\text{source}} = 2.8\text{mA}$ (Supply current)


- its analogue ic's \rightarrow we supply only 5-15V.

- $i_{\text{IP+noise}}$ \rightarrow Amplifier \rightarrow amplify the noise also.

$i_{\text{IP+noise}}$ \rightarrow OP-Amp \rightarrow only amplify the signal - when CMRR is high

- CMRR gives the knowledge about how efficient the op-amp for rejection of noise.

Equivalent circuit of op-amp

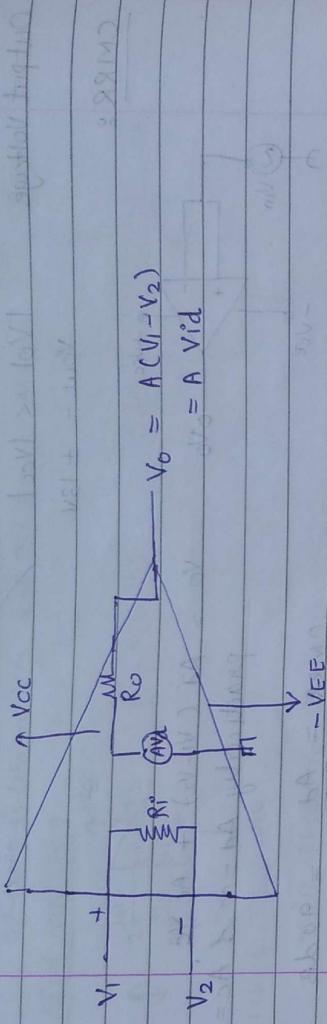


Open loop configuration:



(i) Differential Amp.

(ii) Inverting


(iii) Non-inverting

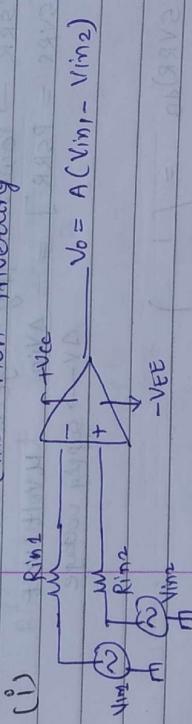

(i)

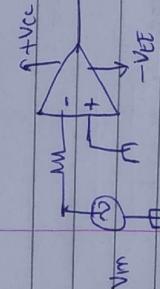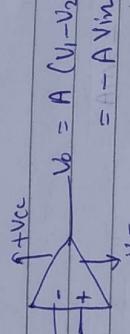

(ii)

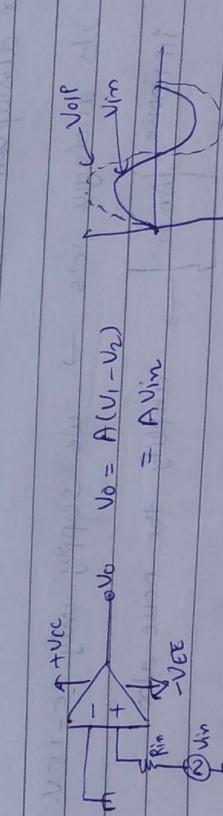

$$V_o = A(V_1 - V_2)$$

$$|V_o| < |V_{cc}|$$

$$A = 2 \times 10^5$$

$$V_{cc} = 15V$$


$$A = 2 \times 10^5$$

Date: 25-July
Page:

Open loop: - used in non linear application as compare

Closed loop: " linear " as adder, subtractor

charge (110) V_o

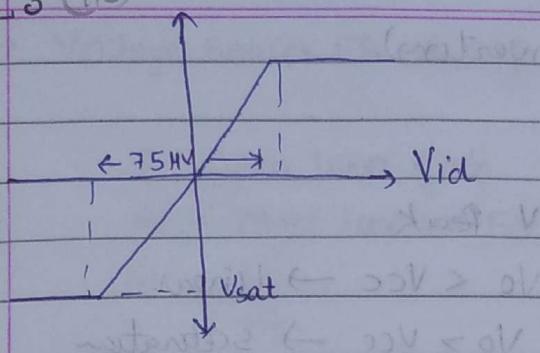

for linear application, $V_{id} \leq 75 \text{ mV}$
 $V_{id} > 75 \text{ mV}$, then op-amp will goes on saturation region.

- for linear application, open loop conf. is not used becauz for linear application $V_{id} \leq 75 \text{ mV}$, which is difficult to achieve (very small range).

Exg- (i) $V_{in1} = 5 \text{ mV}$ dc (ii) $V_{in1} = 10 \text{ mV}$ sine wave

$$V_{in2} = -7 \text{ mV}$$

$\frac{741}{C}$

$$A = 2 \times 10^5$$

$$V_{in2} = 20 \text{ mV}$$

rms value

Sol: $V_{out} = A [V_{in1} - V_{in2}]$
 $= 2 \times 10^5 [5 + 7] \mu$
 $= 24 \times 10^5 \times 10^{-6}$
 $= 2.4 \text{ V dc}$



$$V_{out} = 2 \times 10^5 [-10] \text{ m}$$

$$= -2 \times 10^5 \times 10^{-2}$$

$$= -2 \text{ kV (rms)}$$

$$V_m = V_{rms} \times \sqrt{2}$$

Linear

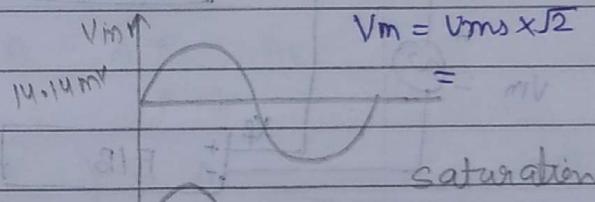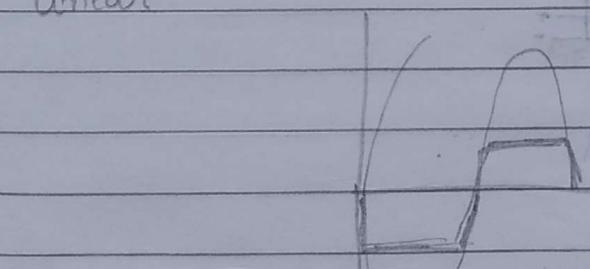

switched operation

clip the O/P because $|V_{out}| > |V_{cc}| - V_{sat}$

because $|V_{out}| > V_{cc}$

(ii) $V_{in1} = 20 \text{ mV}$ dc (inverting amp)

$$V_{out} = A (V_{in1} - V_{in2})$$

$$= -AV_{in2}$$

$$= -2 \times 10^5 \times 20 \times 10^{-3}$$

$$= -40 \times 10^2 = -4000 \text{ V dc}$$

V_{out}

-1MV

saturation

Date 28-July
Page

$$V_{in} = -50 \text{ mV Peak} \quad (\text{inverting})$$

$$V_o = 25 - A V_{in}$$


$$= 25 - 2 \times 50 \times 10^{-6} \times 10^5$$

$$= 25 - 100 \times 10^{-1} = 15 \text{ mV Peak}$$

V_{out}


$V_o < V_{cc} \rightarrow \text{Linear}$

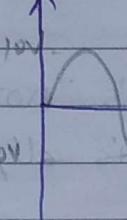$V_o > V_{cc} \rightarrow \text{Saturation}$




feed back configuration:

① Voltage Series:

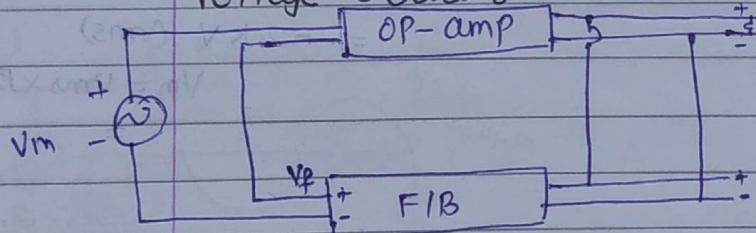


②

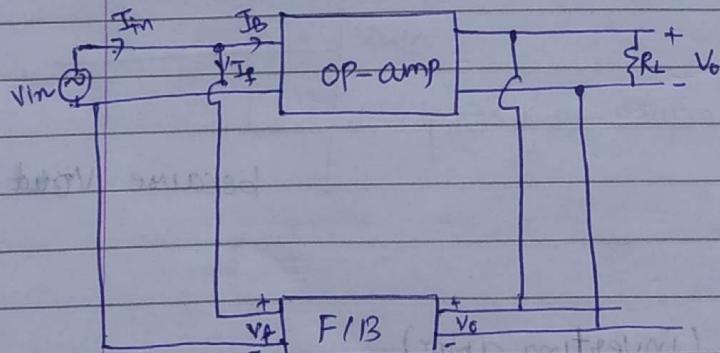

Voltage Shunt:

In OP-Amp:

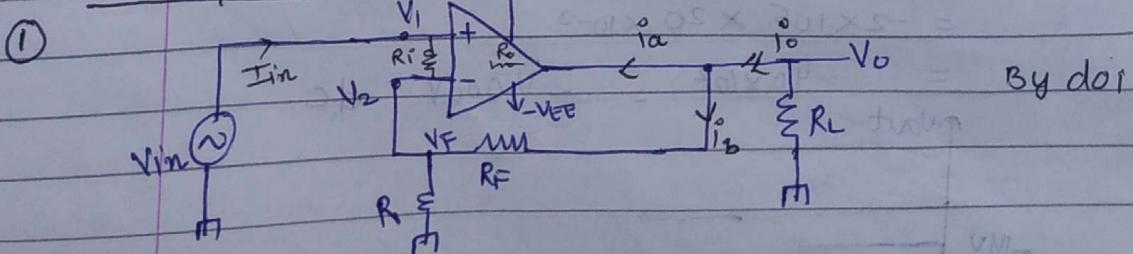

→ Voltage Series FB OP-amp / Non-inverting amp

A - Open loop gain

gain:

AF - Close loop or Feedback gain

$$AF = \frac{V_o}{V_{in}}$$

$$\textcircled{A} \quad V_1 = V_{in}$$

$$V_2 = V_f = \frac{R_L}{R_L + R_F} V_o$$

$$V_o = A(V_1 - V_2)$$

$$\text{So, } AF = A \left(\frac{V_1 - V_2}{V_1} \right) = A \left(1 - \frac{V_2}{V_{in}} \right)$$

$$AF = A \left(1 - \frac{R_L V_o}{V_{in} (R_L + R_F)} \right)$$

$$AF = A - A \frac{R_L}{R_L + R_F} \cdot AF$$

$$AF \left[1 + A \frac{R_L}{R_L + R_F} \right] = A$$

$$AF = \frac{A(R_L + R_F)}{R_L + R_F + A R_L}$$

$\therefore A R_L \gg R_L + R_F$

$$\text{So, } AF = \frac{R_L + R_F}{R_L} = \boxed{\frac{1 + R_F}{R_L} = AF}$$


If $AF = 11$

$$\text{then } R_F = 10 R_L$$

$$(i) \quad R_L = 1k \quad ; \quad R_F = 10k$$

$$(ii) \quad R_L = 5k \quad ; \quad R_F = 50k$$
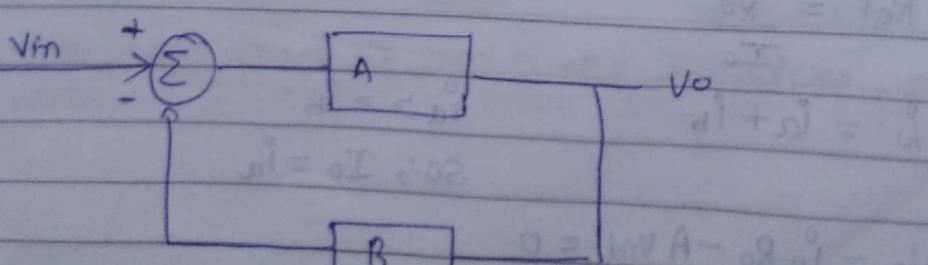
$$(iii) \quad R_L = 100\Omega \quad ; \quad R_F = 1k$$



$$\boxed{B = \frac{V_F}{V_O} = \frac{R_I}{R_I + R_F}} \rightarrow \text{gain of feedback circuit}$$

$$A_F = \frac{A}{1 + A \frac{R_I}{R_I + R_F}} = \boxed{\frac{A}{1 + AB}} = \frac{V_{out}}{V_{in}}$$

In ideal condition :-

$$V_O = AV_{id}$$

ideally A is infinite

$$V_{id} = \frac{V_O}{A} \cong 0 \quad (AV - V) A = 0V$$

$$(V_1 - V_2) = 0 \quad (AV - V) A = 0A \quad V_{in} = V_F = \frac{R_I}{R_I + R_F} V_O$$

$$A_F = \frac{V_O}{V_{in}} = \frac{1 + R_F}{R_I}$$

O/P impedance :-

$$R_{if} = \frac{V_{in}}{I_{in}}$$

$$(R_I + R_F) A = I_{in} A$$

$$R_I + R_F \ll R_A \quad \therefore V_O = AV_{id}$$

$$A(V_1 - V_2) = V_{out} = \frac{A}{1 + AB} V_{in}$$

$$\frac{V_{id}}{V_{in}} \times \frac{1}{AB + 1} \frac{V_{in}}{I_{in}} = \frac{V_{id}}{I_{in}}$$

$$\boxed{R_{if} = (1 + AB) R_i}$$

O/P impedance :-

$$R_{of} = \frac{V_O}{I_O}$$

$$I_O = I_a + I_b$$

$$I_a \gg I_b$$

$$\text{so, } I_O = I_a$$

$$V_O - I_O R_O - A V_{id} = 0$$

$$V_{id} = V_1 - V_2 = 0 - V_F$$

By doing short to V_{in} for finding the R_{of}

- When gain = 1 $\Rightarrow (1+AB) \approx A$, follower \Rightarrow non inverting ampr

$$A_F = 1; f_F = f_{OA}$$
$$R_{IF} = R_A/A; V_{OOL} = \pm V_{sat}/A$$
$$R_{OF} = R_O/A$$


Date _____
Page _____

1-Aug-08

$$\Rightarrow V_{id} = -V_F$$


$$\beta = \frac{V_F}{V_o}$$

$$R_{OF} = \frac{R_O}{1+AB}$$

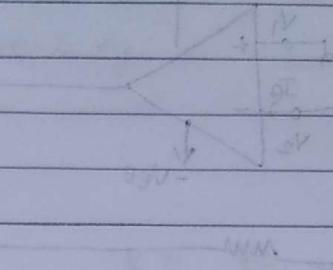

Bandwidth

Gain \uparrow

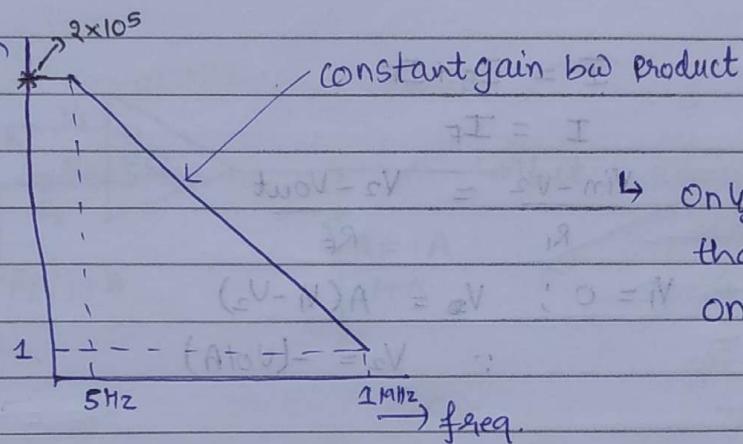

\Rightarrow Only single break freq.
that's 3dB from that
only BW \times gain = constant

for open loop op-amp : $A = 2 \times 10^5$; $f_0 \rightarrow$ single break away freq.

$$BW = 5 \text{ Hz}$$

Bandwidth is used in non-inverting feedback ampr

$$2 \times 10^5 \times 5 = 1 \text{ MHz} = \text{for open loop}$$

$$\text{Unity gain BW} = 1 \times 1 \text{ MHz}$$



$$UGB (\text{Unity gain Bandwidth}) = A f_0 \\ = A_F f_F$$

$$f_F = \frac{A f_0}{A_F} = f_0 (1 + BA)$$

$$V_{toil} = \pm \frac{V_{sat}}{1+AB} \quad (\text{OIP offset voltage})$$


$V_{sat} \rightarrow$ total OIP voltage swing

②

Voltage shunt FB op-amp / inverting ampr

(bandwidth maintain) $\Delta V = 1V$

$$\Delta I = T \cdot \Delta V$$

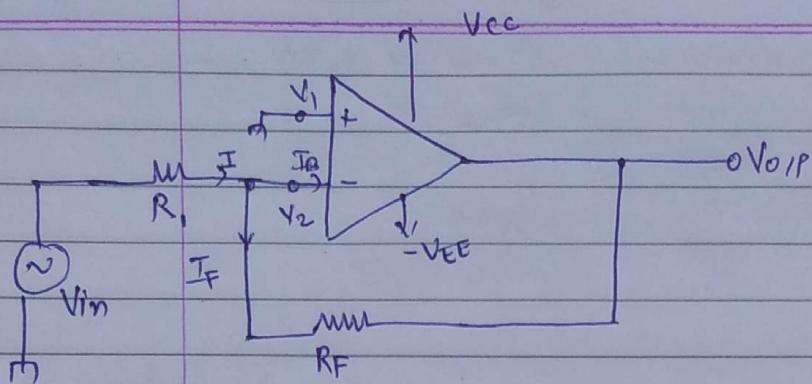

$$I = I_B + I_F$$

$$I = I_F$$

$$\frac{V_{in} - V_2}{R_1} = \frac{V_2 - V_{out}}{R_F}$$

$$V_1 = 0; V_2 = A(V_1 - V_2)$$

$$\therefore V_2 = -(V_{out}/A)$$

$$\frac{V_{in} - V_2}{R_1} - \frac{V_2}{R_F} = -\frac{V_{out}}{R_F}$$

$$\frac{V_{in}}{R_1} + \frac{V_{out}}{R_F} + \frac{V_2}{A} \left(\frac{1}{R_1} + \frac{1}{R_F} \right) = 0$$

$$\frac{V_{in}}{R_1} = -V_{out} \left[\frac{1}{R_F} + \frac{1}{AR_1} + \frac{1}{AR_F} \right] = 0$$

$$\frac{AR_1 + R_F + R_1}{(AR_1 R_F) R_1} = -\frac{V_{out}}{V_{in}} = AF$$

$$\frac{R_1(1+A) + R_F}{R_1(1+A) + R_F} = AF$$

$$AF = \frac{V_{out}}{V_{in}} = -\frac{R_F A}{R_1 + R_F + A R_1}$$

$$\therefore AR_1 \gg R_1 + R_F$$

$$\therefore AF = -R_F / R_1$$

I_B

$$I_B = V_{out} / R_1$$

ideally very high gain $A = \infty$

$$V_{id} = 0$$

$$V_1 = V_2 \text{ (virtually ground)}$$

$$\therefore I = I_F$$


Op impedance: - V_{in} is shorted

- same as non-inverting

$$R_{of} = \frac{R_o}{1+BA}$$

Pip impedance:
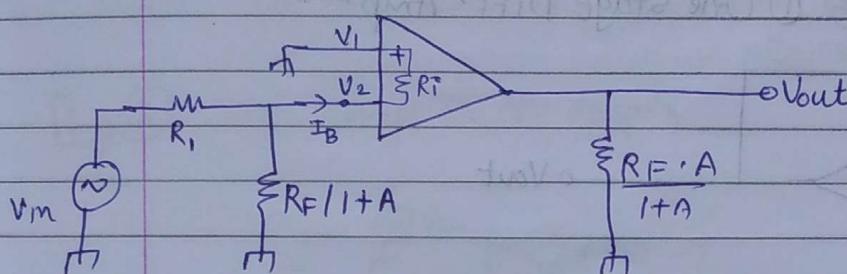
$$K = \frac{RF}{R_i + RF} \rightarrow \begin{array}{l} \text{Voltage} \\ \text{attenuation} \\ \text{factor} \end{array}$$



$$R_i^f = R_i + \left(\frac{RF}{1+A} \parallel R_i \right) \quad : A \approx \infty$$

Gains

$$AF = \frac{V_{out}}{V_{in}} = \frac{-R_F A}{R_i + R_F}$$

$$AF = \frac{-AK}{1+AB} \quad (K \rightarrow \frac{RF}{R_i + R_F})$$

frequency f_f

$$f_f = (AB+1)f_0$$

$$U_{GB} = Af_0 \Rightarrow f_0 = \frac{U_{GB}}{A}$$

$$\text{so, } f_f = \frac{U_{GB}}{AK} (1+AB)K$$

$$f_f = \frac{U_{GB} \cdot K}{AF} \rightarrow \text{inverting}$$


$$f_f_{\text{NON}} = \frac{U_{GB}}{AF} \rightarrow \text{non-inverting}$$

- BW is higher for non-inverting amp. because $\omega_L < 1$

$$f_f \text{ non} = \frac{1}{2\pi R_f C_{AC}} = \frac{U_{Q_B}}{A_{RF}^2}$$

By eqn ① & ②

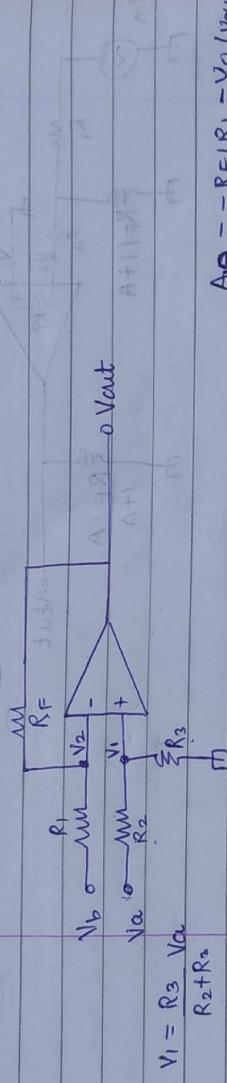Differential Amp ① ② One Stage Differ Amp



$$A_{DIF} = -R_f / R_1 = V_{out} / V_1$$

$$R_{IFx} = R_1$$

$$R_{IFy} = R_2 + R_3$$

$$V_{ob} = -R_f V_{ob} \quad \rightarrow \quad V_{ob} = \frac{R_3}{R_2 + R_3} V_1$$

\rightarrow V_{ob} active (non inverting) ; V_{ob} grounded

$$V_{oaa} = \left(1 + \frac{R_f}{R_1} \right) V_1$$

$$V_{oaa} = \left(1 + \frac{R_f}{R_1} \right) \left(\frac{R_2}{R_2 + R_3} \right) V_1$$

Let assume $R_3 = R_f$ & $R_2 = R_1$

$$V_{oaa} = \left(1 + \frac{R_f}{R_1} \right) \left(\frac{R_f}{R_1 + R_f} \right) V_1$$


$$V_{oaa} = \frac{R_f}{R_1 + R_f} V_1$$

Hence we get diff. imp. impedance when connected to different terminals.

Hence while we connect $V(+)$ & $V(-)$ together voltage impedance won't match. So avoid this problem some modification is done.


non-invert $V(+)$: $R_{IF1} = R_1(1+A\beta) \quad ?$

inverting $V(-)$: $R_{IF2} = R_1$

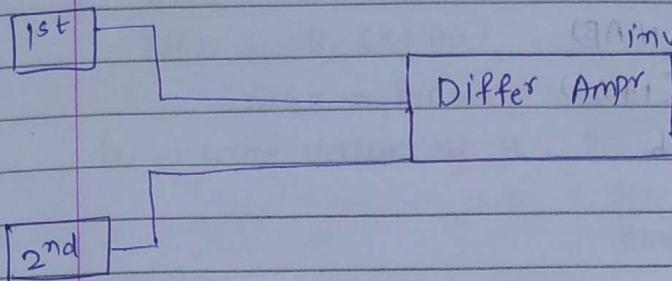

- Loading impedance matching is not done for Differ Amp.

L(2) Two stage Differ Amps

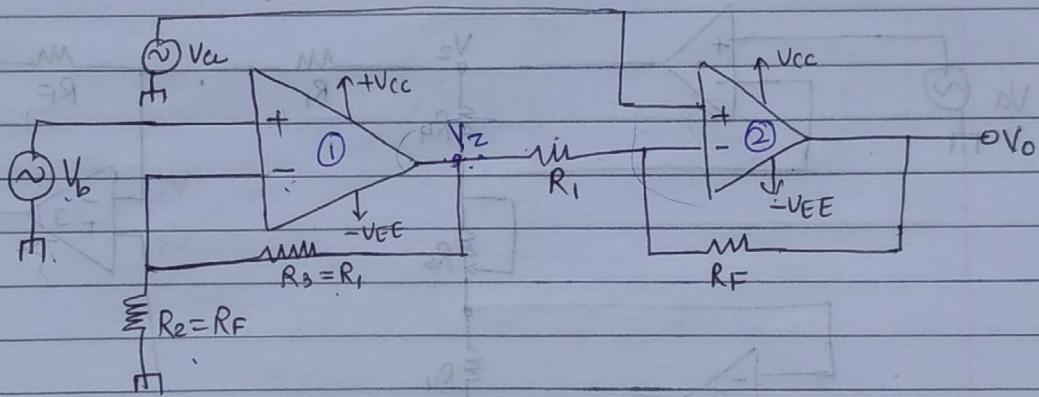

Op-amp ① is non-inverting amp.

Op-amp ② is differential amp.

$$V_z = \left(1 + \frac{R_F}{R_1} \right) V_b$$

$$V_{out} = -\frac{R_F}{R_1} V_z + V_a \left(1 + \frac{R_F}{R_1} \right)$$

(when $V_a=0$) (when $V_z=0$)
superposition theorem

$$V_{out} = -\frac{R_F}{R_1} \left[1 + \frac{R_1}{R_F} \right] V_b + V_a \left(1 + \frac{R_F}{R_1} \right)$$

$$= -\frac{R_F}{R_1} \cdot V_b - V_b + V_a + V_a \frac{R_F}{R_1}$$


$$= - \left[\left(1 + \frac{R_F}{R_1} \right) (V_a - V_b) \right]$$

$$R_{iFA} = R_i(1+AB)$$


$$R_{iFB} = R_i(1+AB)$$

$$R_{iFA} \neq R_{iFB}$$


\Rightarrow ③ Three stage Diff Amp:

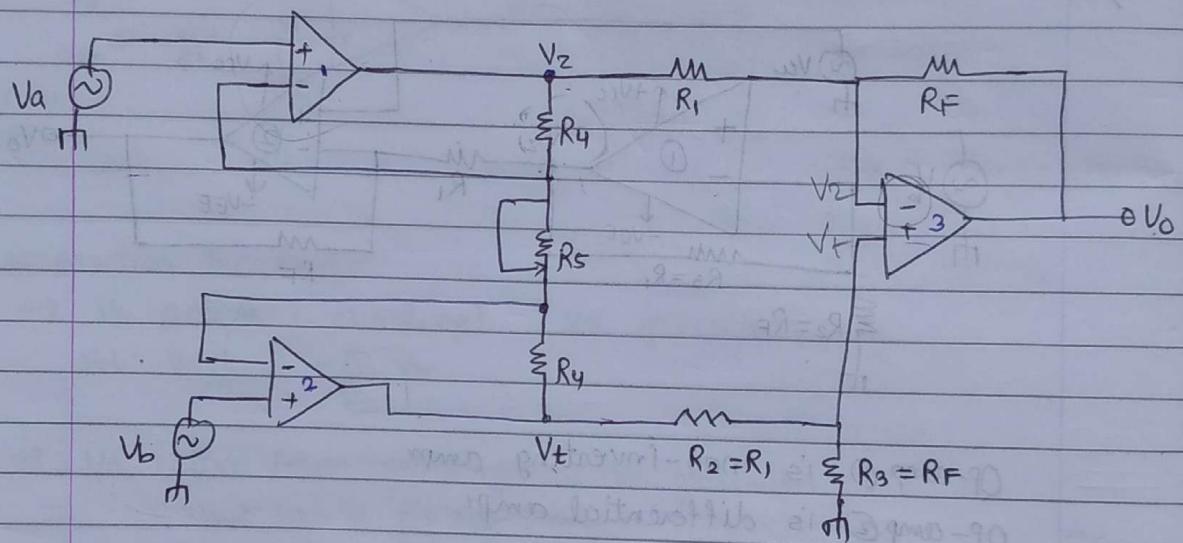

① When $V_b = 0$

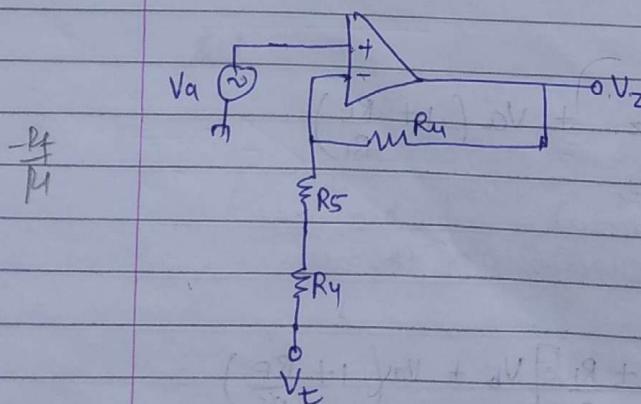

② When $V_a = 0$

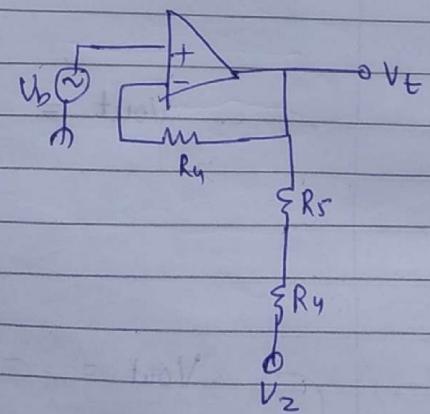

$$\textcircled{1} \quad V_z = V_a \left[1 + \frac{R_y}{R_y + R_S} \right] + V_t \left[-\frac{R_y}{R_y + R_S} \right]$$

$$\textcircled{2} \quad V_t = V_b \left[1 + \frac{R_y}{R_y + R_S} \right] + V_z \left[-\frac{R_y}{R_y + R_S} \right]$$

$$R_{ifA} = R_1 (1 + AB)$$

$$R_{ifB} = R_1 (1 + AB)$$

$R_{ifA} = R_{ifB}$ (both are coming from op-amp)

becuz same value of B , $R_{ifA} = R_{ifB}$

$$\frac{AV}{AV - 1} = \frac{V}{V - B} \rightarrow \frac{R_4}{R_4 + R_5} = \frac{1}{1 + B} \rightarrow \frac{R_4}{R_4 + R_5}$$

$$(3) V_{out} = V_z \left(-\frac{RF}{R_1} \right) + V_t \left(1 + \frac{RF}{R_1} \right)$$

$$V_o = - \left(1 + 2R_y \right) \frac{RF}{R_1} V_{ab}$$

$$V_{ab} = V_a - V_b$$

$$AV - 1 = 0V$$


$$0 > 0V$$

$$0 < 0V$$


$$AV > V$$


$$AV < V$$

Switched

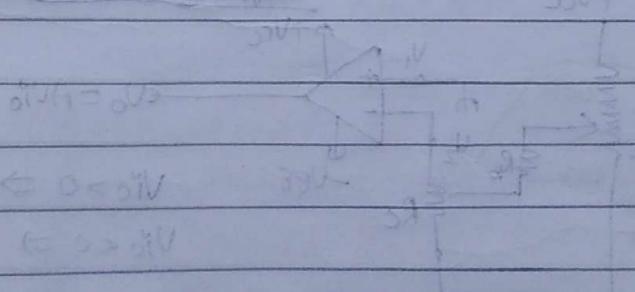

op-amp only (i)

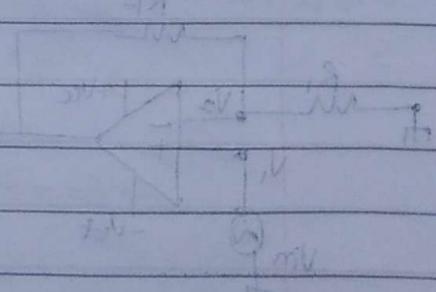

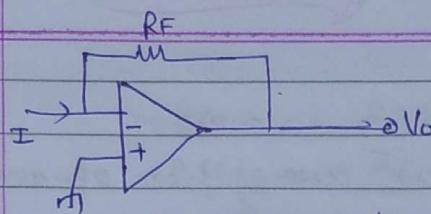

P.I.P \rightarrow Current

O.I.P \rightarrow Voltage

Application : n/a

- Solar Panel


- fiber optic comm^m

- DAC

$$V_o = -\frac{R_f}{R_1} V_{in}$$

$$= -R_f \cdot I_{in}$$

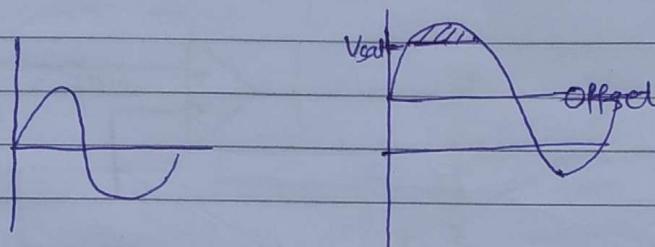OFFSET VOLTAGE - Compensating n/w Design:



By offset
our signal is
clip because of Vsat.

$$V_{io} = V_1 - V_2$$

$$V_{io} > 0$$


$$V_{io} < 0$$

$$V_1 > V_2$$


$$V_1 < V_2$$

- if non-inverting ampr, then offset voltage comp. n/w connected to inverting terminal. if inverting then, non-inverting comp n/w

(i) Non inverting:

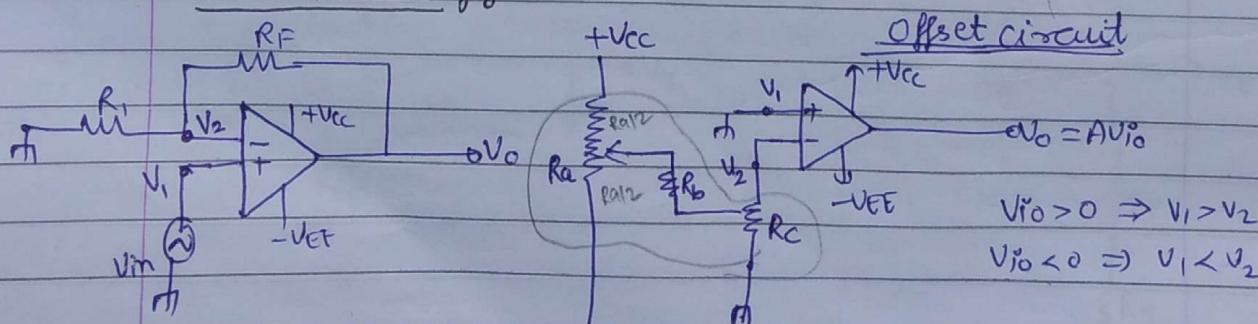

Thevenin ckt:

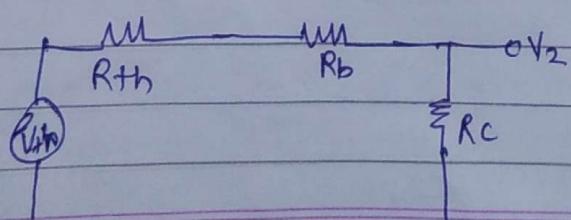

$$R_{th} = \frac{R_a R_b}{R_a + R_b}$$

$$R_{th} = R_a / 4$$

$$V_{2i} = \frac{R_c V_{th}}{R_c + R_b + R_{th}}$$

$$V_{th} = |V_{cc}| = |V_{ee}|$$

$$\text{So, } V_{io} = \frac{R_c V}{R_c + R_b + R_{th}}$$

Note: R_c is very small (because current is less by voltage div rule)

$$R_b > R_a > R_{th} \quad (\text{Assumption})$$

$$\text{So, } R_c + R_b + R_{th} \approx R_b$$

then

design equation:

$$V_{io} = \frac{R_c V}{R_b}$$

$$\text{for IC LM307: } V_{io} = 10 \text{ mV}$$

$$V = 10 \text{ V}$$

$$\frac{R_c}{R_b} = 1 \text{ m} \Rightarrow R_b = 1000 R_c$$

$$\text{Let assume } R_c = 10 \Omega$$

$$R_b = 10 \text{ k}\Omega$$

$$R_a = 1 \text{ k}\Omega$$

$$R_b > R_{th}$$

$$R_b = 10 R_a / 4$$

$$\text{So } R_a = 4 \text{ k}\Omega$$

$$R_c = 100 \Omega$$

$$R_b = 100 \text{ k}\Omega$$


$$R_a = 10 \text{ k} ; R_b = 10 R_a$$

$$\therefore R_b > R_{th}$$

$$R_b = 10 R_{th}$$

$$= 10 R_a / 4$$

Non
Inverting


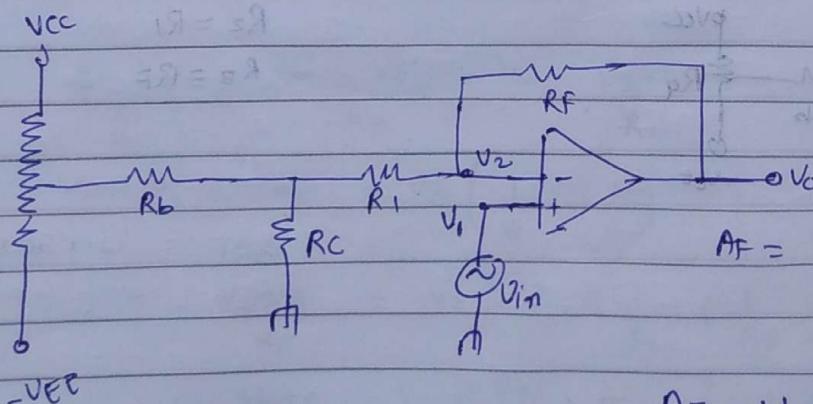


$$A_f = 1 + \frac{R_F}{R_1} \quad (\text{without compensation})$$


$$A_f = 1 + \frac{R_F}{R_1 + R_C} \quad (\text{with comp.})$$

so R_C should be very less, because its ^{does} not affecting the gain of feedback.

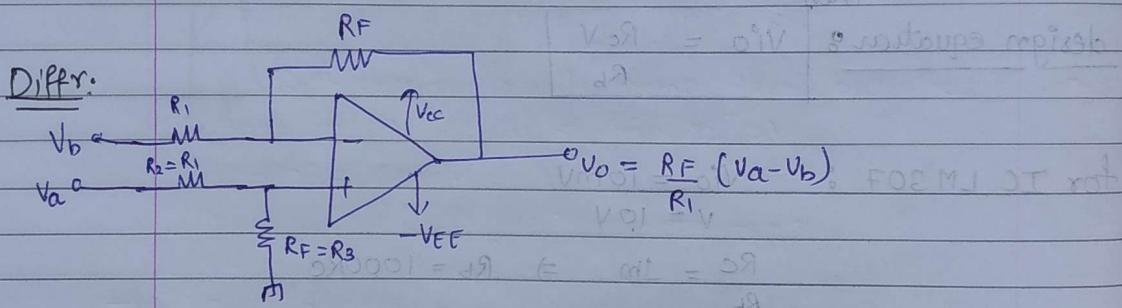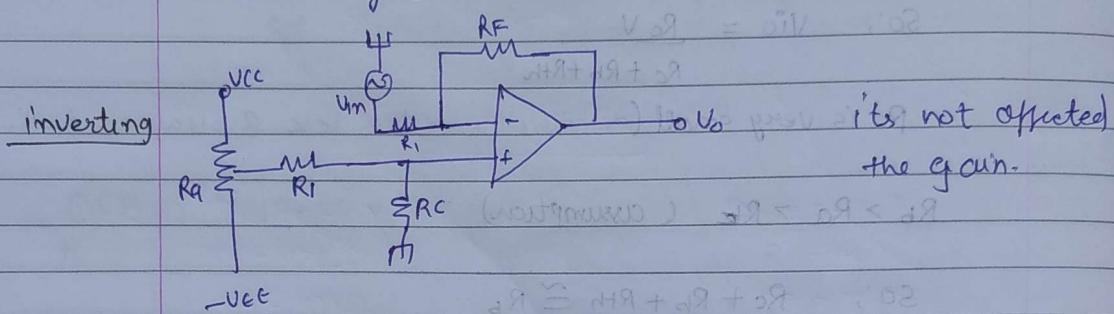- gain of the amp, will not change by changing the value of R_C is very less.




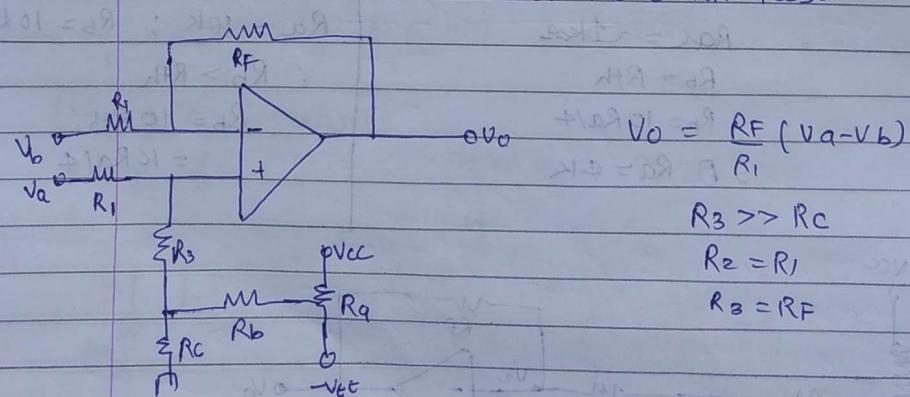- when we connect compensating n/w to non-inverting terminal than its effect the CMRR less.




$$V_{OOT} = f(V_{IO}, I_B, I_{IO})$$

Date 22-Aug
Page

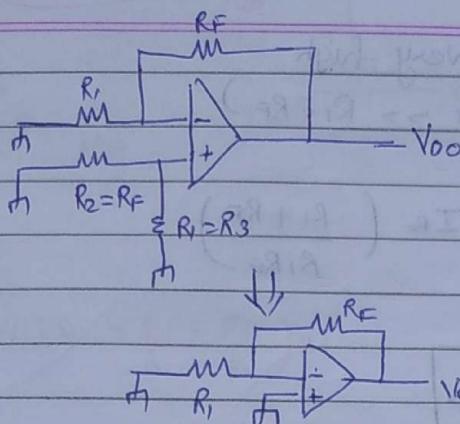

(non-inverting)

$$V_{OO} = \frac{R_F}{R_1} V_{IO}$$

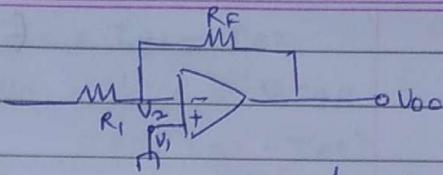

(inverting)

$$V_I = 0$$


$$V_2 = \frac{R_1}{R_1 + R_F} V_O$$

$$V_{IO} = |V_I - V_2| = |V_2|$$

$$V_{OO} = \left(1 + \frac{R_F}{R_1}\right) V_{IO} \rightarrow \text{for inverting amp} / \text{non inverting amp}$$

~~Amplifier gains always depends on~~

~~RF ratio > 100, can see separation~~

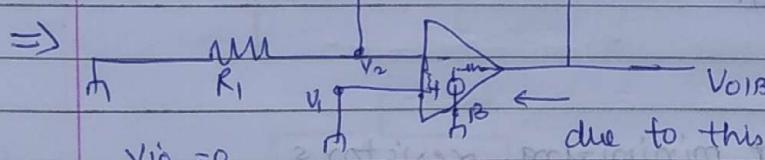

due to this ground, we can say RF & R_1 are in parallel.

$$\therefore V_2 = \left(\frac{R_1 R_F}{R_1 + R_F}\right) I_B$$

$$A_V V_I = 0$$

R_o = very small

\therefore AB whole terminal is grounded $\Rightarrow R_F \parallel R_1$


$$\frac{0 - V_2}{R_1} + \frac{V_{OIB} - V_2}{R_F} = \frac{V_2 - 0}{R_1}$$

$$\frac{V_{OIB} - V_2}{R_F} = V_2 \left(\frac{1}{R_1} + \frac{1}{R_F} \right)$$

$$\frac{V_{OIB}}{R_F} = V_2 \left(\frac{1}{R_F} + \frac{1}{R_1} + \frac{1}{R_F} \right)$$

$$\frac{V_{OIB}}{R_F} = \left(\frac{R_1 R_F}{R_1 + R_F} \right) I_B \left(\frac{1}{R_1} + \frac{1}{R_F} \right)$$

$$(V_{OIB} - V_{IO}) + = 100V$$

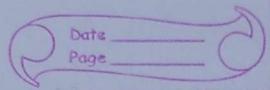

($\because R_i$ is very high)

$$R_i \gg R_1, R_F$$

$$\therefore \frac{V_{OIB}}{R_F} = \left(\frac{R_1 R_F}{R_1 + R_F} \right) I_B \left(\frac{R_1 + R_F}{R_1 R_F} \right)$$

$$\therefore V_{OIB} = (R_F) I_B$$

: Design - (1)

$$R_1 = 470\Omega$$

$$R_2 = 47k\Omega$$

Design - (2)

$$R_1 = 1K$$


$$R_F = 100K$$

$$\frac{R_1 + R_F}{R_F} = 101 \quad \frac{R_1}{R_F} = 101$$

Both designs provide same gain but the offset voltage in (1) will be less than in (2)
∴ (1) is good.

$\Rightarrow R_{oM} \rightarrow$ offset minimizing resistors

$$R_{oM} = R_1 || R_F$$

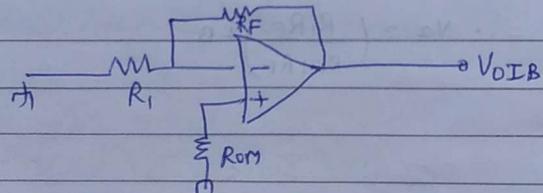

$$V_{OVT} = \left(1 + \frac{R_F}{R_1} \right) V_{IO} + R_F I_B$$

$$\textcircled{1} \quad V_{IO} = 6mV$$

$$I_B = 500nA$$

$$R_1 = 470\Omega$$

$$R_F = 47k\Omega$$

$$V_{OVT} = 0.629V$$

$$R_{oM} = 465.346\Omega$$

$$\textcircled{2} \quad V_{IO} = 6mV$$

$$I_B = 500nA$$

$$R_1 = 1K$$


$$R_F = 100K$$

$$V_{OVT} = 0.656V$$

$$R_{oM} = 990.099\Omega$$

EX:

Sol 18

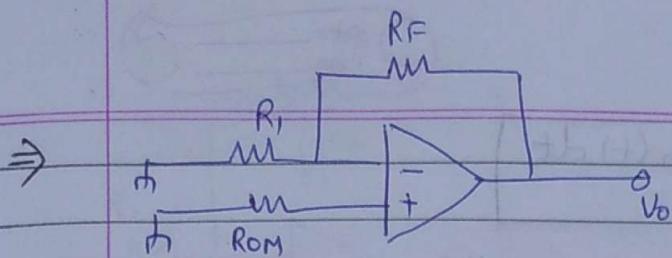

Date _____
Page _____

$$I_B = I_{B1} = I_{B2}$$

$$V_O = V_O I_{B1} + V_O I_{B2}$$

$$= R_F (I_B) - I_B$$

$$\boxed{V_O I_{B0} = R_F I_{B0}}$$

$$V_O I_{B1} = \left(1 + \frac{R_F}{R_1}\right) V_I$$

$$V_O I_{B2} = -R_F I_{B2}$$

$$= \left(1 + \frac{R_F}{R_1}\right) R_{OM} I_B$$

$$V_{O0T} = \left(1 + \frac{R_F}{R_1}\right) V_{I'0} + R_F I_{I'0}$$

$$I_{I'0} = |I_{B1} - I_{B2}|$$


$$\text{if } I_{B1} \neq I_{B2}$$

$$I_B > I_{I'0}$$

then

$$\boxed{V_{O0T} = \left(1 + \frac{R_F}{R_1}\right) V_{I'0} + R_F I_B}$$

EX:

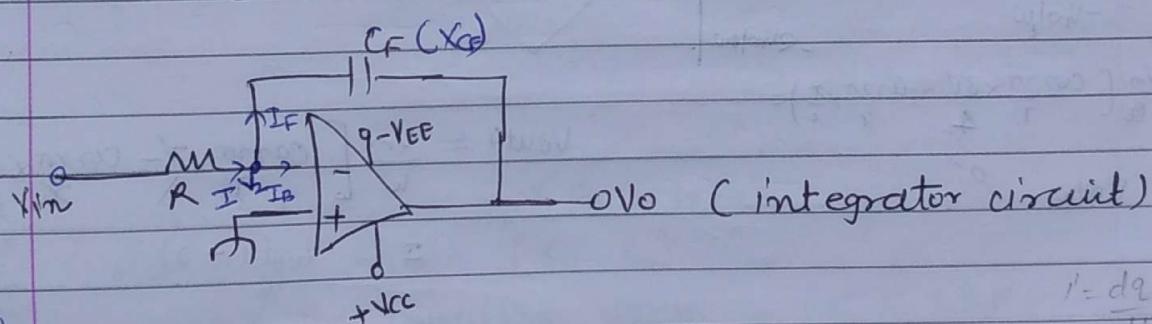

S018

① (if inverting then, node analysis)

$$I = I_B + I_F$$

$$I = I_F$$

$$\frac{V_{in} - V_2}{R} = C_F \frac{d}{dt} (V_2 - V_O) \quad \textcircled{1}$$

② (virtual ground concept in inverting)

$$V_1 = 0$$

(in inverting, virtual ground concept so $V_1 = 0$)



$$V_1 = V_2$$

(high gain)

$$\text{So, } V_2 = 0$$

$$\text{in eqn } \textcircled{1} \quad V_{in} = -C_F R \frac{d(V_O)}{dt}$$
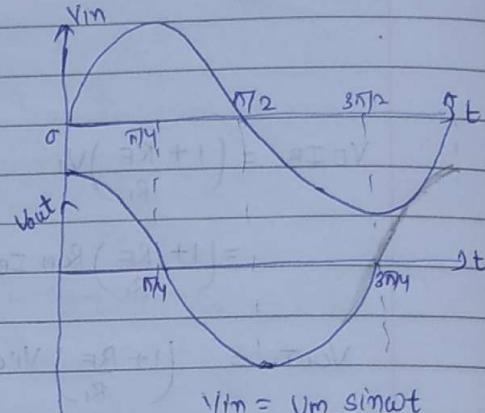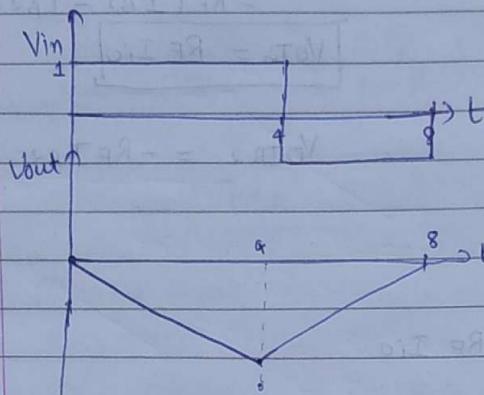
$$V_o = - \frac{1}{C_{ER_1}} \int V_{in}(t) dt$$



$$V_{out1} = \frac{V_m}{\omega} \left[\cos \frac{2\pi}{T} \times \frac{T}{4} - \cos \phi_0 \right]$$

$$= -V_m/\omega$$

$$V_{avg2} = \frac{U_m}{\omega} \left[\cos \frac{2\pi}{T} \times \frac{T}{2} - \cos \frac{2\pi}{T} \times \frac{T}{2} \right] = U_m$$



$$= -U_m / \omega$$

$$V_{out\ 3} = \frac{V_m}{2\pi} \left[\cos \frac{2\pi}{T_1} x 3T - \cos \frac{2\pi}{T_2} x T \right] =$$

$$= \sqrt{p_0} u_2$$

$$V_{out4} = \frac{V_m}{w} \left[\cos \omega t - \cos \omega t \cdot \frac{\pi}{2} \right]$$

$$= V_m (1 - 0)$$

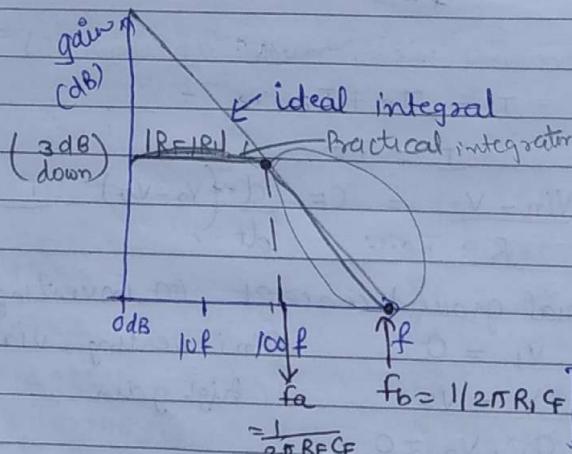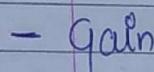


$$AF = \left| -\frac{Y_F}{R_1} \right|$$

$$= \left| \frac{-1/j\omega C_f}{R_1} \right|$$

$$A_F = \frac{1}{w R_1 C_F}$$

$$F \propto 1/f$$

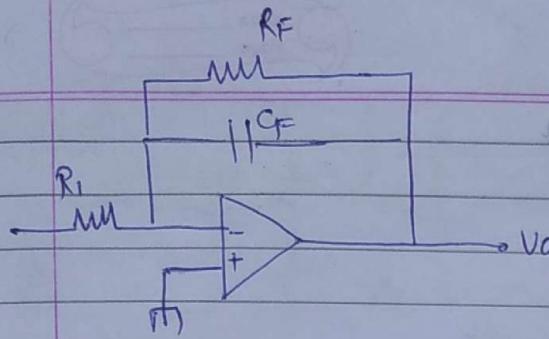- stability problem at low freq. bcz $f=0$, gain = ∞
So we have to improve our circuit



$$\text{With } D \gg 1, AF = \frac{1}{2\pi F R_i} = \frac{1}{j\omega C_F} \times RF$$

$$= \frac{1}{j\omega C_F} \times RF$$

$$\left(\frac{RF + j}{j\omega C_F} \right) R_i$$

$$AF = \frac{RF}{(RF j\omega C_F + 1) R_i}$$

3 dB down

$$AF = \frac{RF}{R_i(1 + j\omega C_F RF)} = \frac{1}{\sqrt{2}} \frac{RF}{R_i}$$

$$\sqrt{2} = 1 + j\omega C_F RF$$

$$0.065 = j\omega C_F RF \cdot f$$

$$f_a = \frac{1}{2\pi R_F C_F} \quad (\text{Practical})$$

$$f_b = \frac{1}{2\pi R_i C_F} \quad (\text{Ideal})$$

- $f_b > f_a \quad (f_b = 10 f_a)$

① Select the range (f_a, f_b)

② assume the capacitor value ($C < 1 \mu F$)


$$C_F = 0.1 \mu F \parallel (2\pi f_a) = 1$$


$$f_a = 1 \text{ kHz} = \frac{1}{2\pi R_F C_F} ; f_b = 10 \text{ kHz}$$

$$2\pi R_F = 1.59 \text{ k}\Omega$$

$$R_F = 10 R_i, \text{ so } R_i = 1.59 \Omega$$

③ $R_F > R_i$ and assume values of R_i

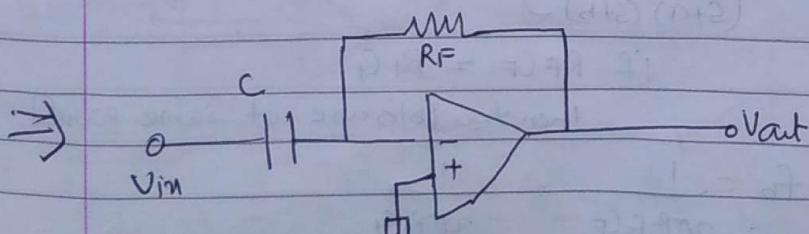

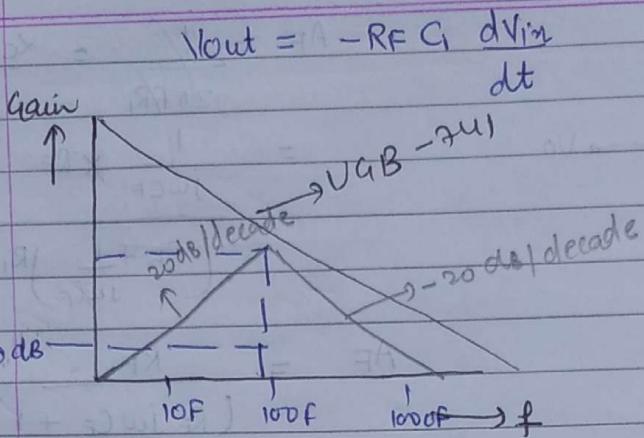

$$AF = RF / X_C$$


$$= RF / j\omega C$$

$$AF = 2\pi f RF C j$$

$$|AF| = 2\pi f RF C$$

$$AF \propto f$$

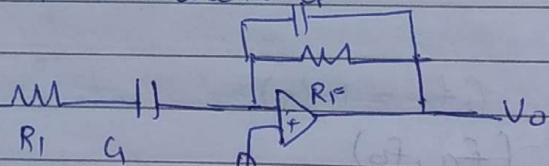- at high freq. it will may created problem bcz at high freq. if noise will added then it also transmitted or amplify with the high gain, which we don't want.



$$AF = (1/SC_F) \parallel RF$$

$$\frac{R_1}{R_1 + 1/SC_F}$$


$$AF = \frac{RF \cdot R_1 s}{(1 + RF SC_F)(R_1 G_S + 1)}$$

$$[\because H(s) = \frac{1}{(s+a)(s+b)}]$$


$$\text{if } RF C_F = R_1 G_S$$

then two poles are at same point

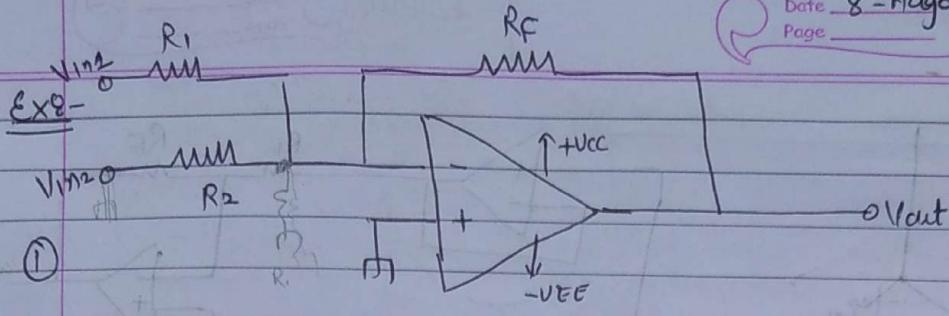
$$f_b = \frac{1}{2\pi R F C_F} = \frac{1}{2\pi R_1 G_S}$$



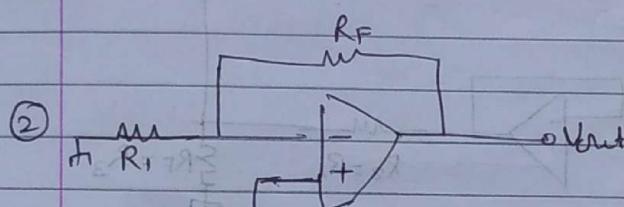Sol: $V_{out} = \frac{-RF}{R_1} V_{in1} - \frac{RF}{R_2} V_{in2} = \frac{-RF}{R_1} (V_{in1} + V_{in2})$



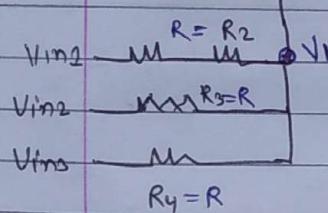
$$V_I = \frac{V_{in1} + V_{in2} + V_{in3}}{3}$$



$$V_{out} = \left(1 + \frac{RF}{R_1}\right) \left(\frac{V_{in1} + V_{in2} + V_{in3}}{3}\right)$$


"(Averaging Amp)"

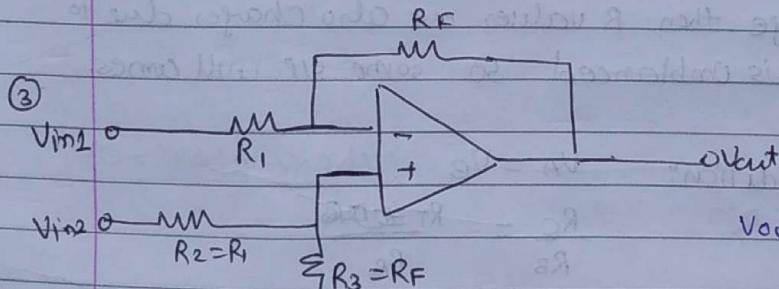

$$V_{out} = -RF V_{in1} + \left(1 + \frac{RF}{R_1}\right) \left(\frac{RF}{R_1}\right)$$

$$= -RF \left(\frac{V_{in1} - V_{in2}}{R_1}\right)$$

("Subtractor")

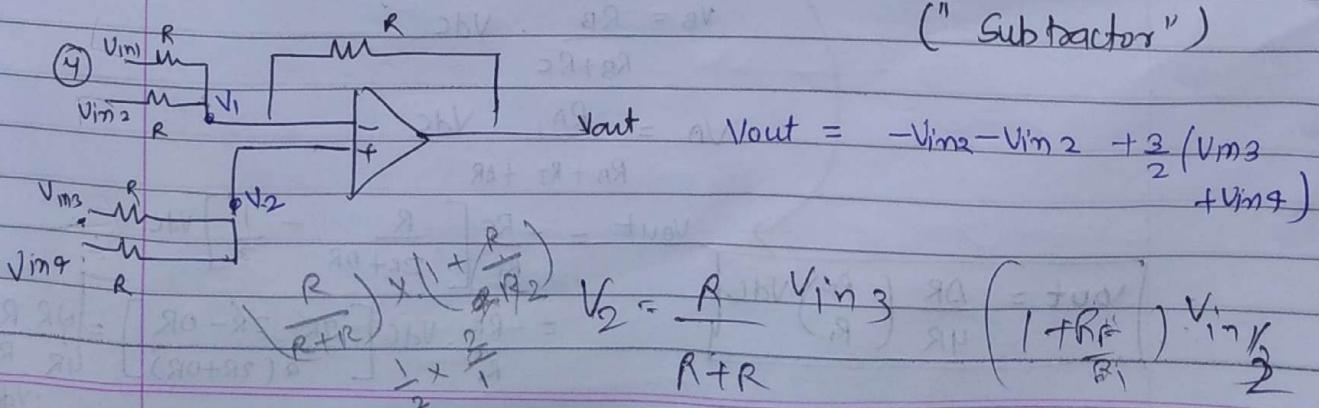


$$V_{out} = -V_{in2} - V_{in1} + \frac{3}{2} (V_{in3} + V_{in4})$$

$$V_2 = \frac{R}{R+R} V_{in3} \quad \left(1 + \frac{RF}{R_1}\right) \frac{V_{in1}}{2}$$

comparator → non linear
all → linear

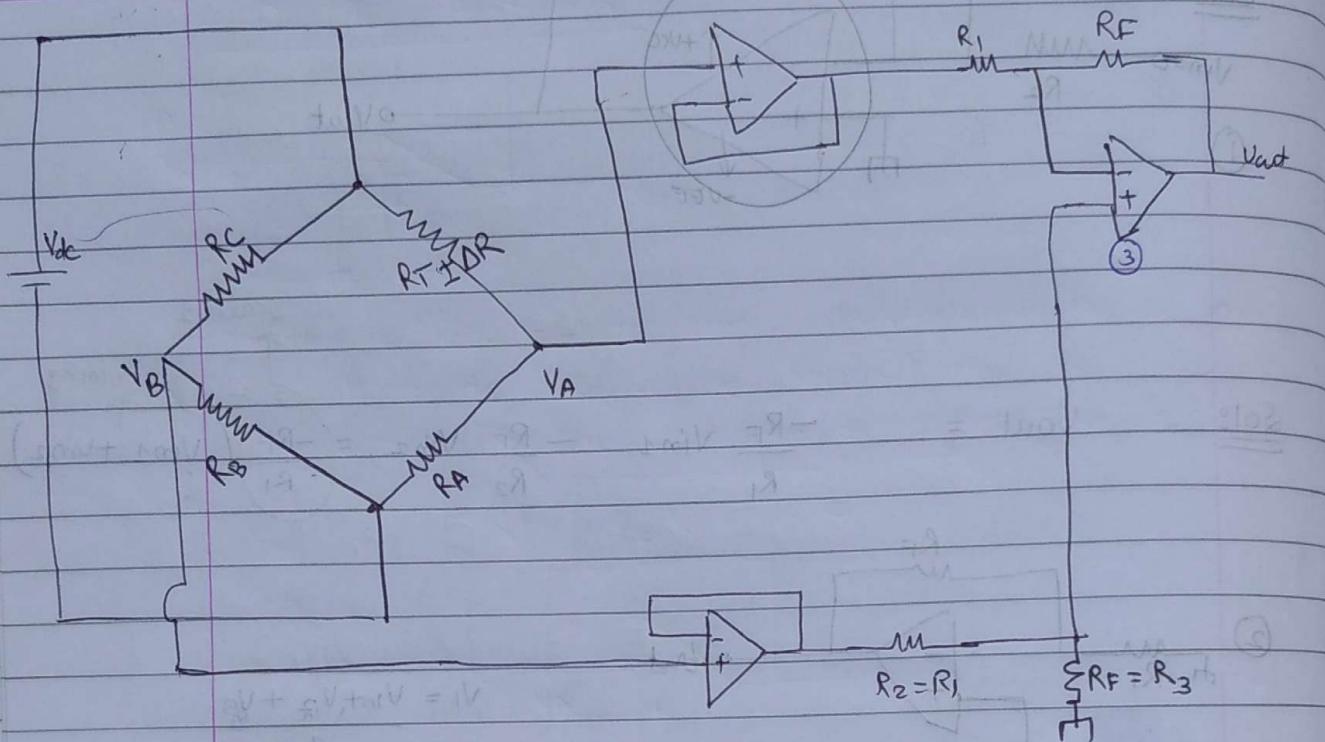Gain = 1
Voltage Follower
Date _____
Page _____



③ → differential ampl

if $V_A = V_B \rightarrow$ then $OIP = 0$

if temp is change then R values are also changes due to this bridge is unbalanced so some OIP will comes

- at balance condition:

$$V_A = \frac{R}{2R+DR} V_{DC}; V_B = \frac{V_{DC}}{2}$$

$$V_A = V_B + (\text{charge in temp} = 0)$$

$$\frac{R_C}{R_B} = \frac{R_T + DR}{R_B}$$

$$V_{out} = -RF/R_1 (V_A - V_B)$$

- at Unbalanced

$$V_A \neq V_B$$

$$V_B = \frac{R_B}{R_B + R_C} V_{DC}$$

$$V_A = \frac{R_A}{R_A + R_T + DR} V_{DC}$$

$$V_{out} = -\frac{RF}{R_1} \left[\frac{R}{2R+DR} - \frac{1}{2} \right] V_{DC}$$

$$V_{out} = \frac{DR}{4R} \left(\frac{RF}{R_1} \right) V_{DC}$$

$$= -\frac{RF}{R_1} \cdot V_{DC} \left[\frac{2R - 2R - DR}{4(2R+DR)} \right] = \frac{DR}{4R} V_{DC}$$


$$R = R(1 + \alpha \Delta T)$$

$$R - R' = \alpha \Delta T$$

$$\Delta R = \alpha \Delta T$$

Date _____
Page _____

Instrumentation Amplifier

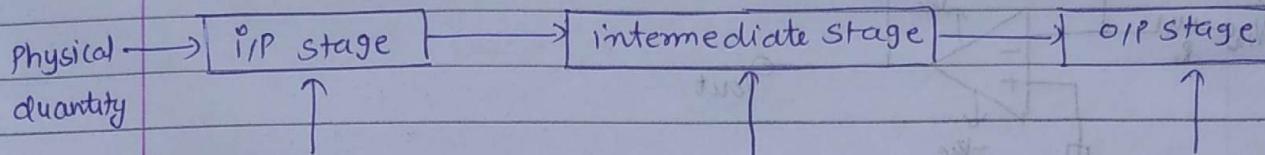

transducers instrumentation stage indicator

Ex :- temp^r coeff = $-1 \text{ K}^{-1}/\text{C}$

Reference temp^r = 25°C

$R_F = 4.7 \text{ k}\Omega$; $R = 100 \text{ k}\Omega$

$R_1 = 1 \text{ k}\Omega$; $V_{dc} = 5 \text{ V}$

(i) V_{out} at 0°C

(ii) V_{out} at 100°C

$$R = R'(1 + \alpha \Delta T)$$

$$R - R' = \alpha \Delta T \cdot R'$$

$$\Delta R = R' \times \Delta T$$

$$R' = R(1 + \alpha \Delta T)$$

$$R' - R = R_2 \Delta T$$

$$\Delta R = R_2 \Delta T$$

Sol: (i)

$$\Delta R = 25 \text{ k}\Omega$$

$$V_{out} = \frac{\Delta R}{4R} \left(\frac{R_F}{R_1} \right) V_{dc} = \frac{25 \times 10^3}{4 \times 100 \times 10^3} \left(4.7 \right) \times 5$$


$$= 1.46 \text{ V}$$

(ii) $\Delta R = -75 \text{ k}\Omega$

$$V_{out} = -\frac{75 \times 10^3}{4 \times 100 \times 10^3} \left(4.7 \right) \times 5 = -4.38 \text{ V}$$

$$(2A+1)\Delta T = H$$

$$A = \frac{H}{2}$$

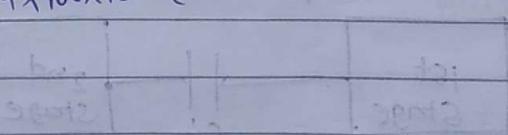


$$H = 2A$$


<math display="block

Date 12-Sep
Page



DC / AC Amplifier

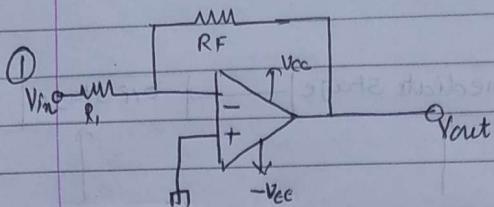

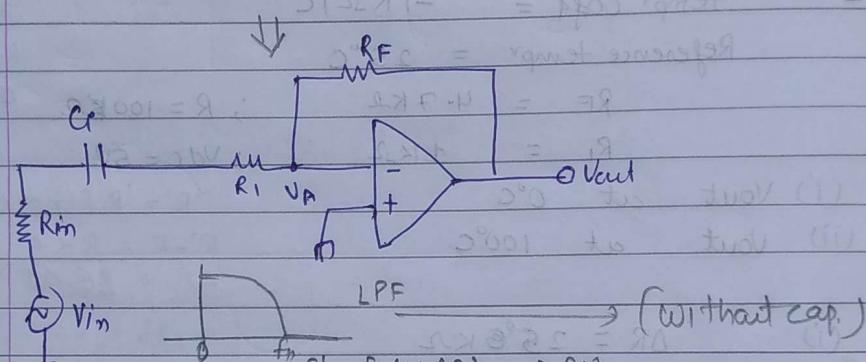- this is ac and dc amp, which amplify the ac as well as dc. So if we required only ac, then we have to use capacitor to remove the dc amplified




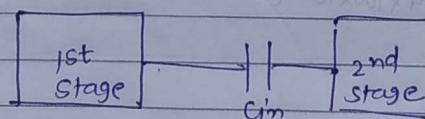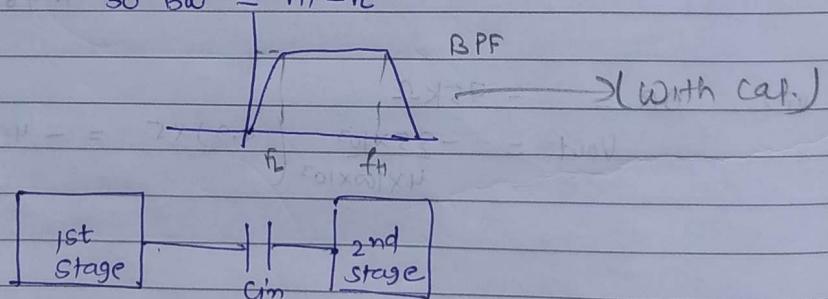due to dc, it's not amplify the ^{dc} signal due to C_F
so BW = $f_H - f_L$



$$f_H = f_O(1 + A_1 \beta)$$


$$f_L = ?$$

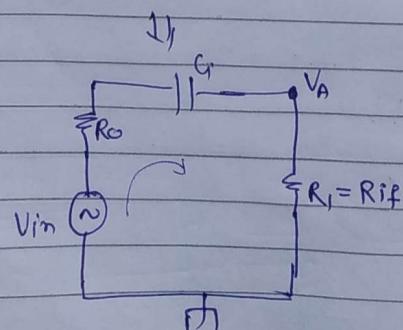

$$V_A = \frac{R_i}{R_i + R_o + 1/j\omega C} \cdot V_o$$


$$V_{out} = -\frac{R_F}{R_I} V_A$$

$$\therefore V_A = \frac{j 2\pi f R_I C_1}{j(f/f_L) + 1} V_m$$

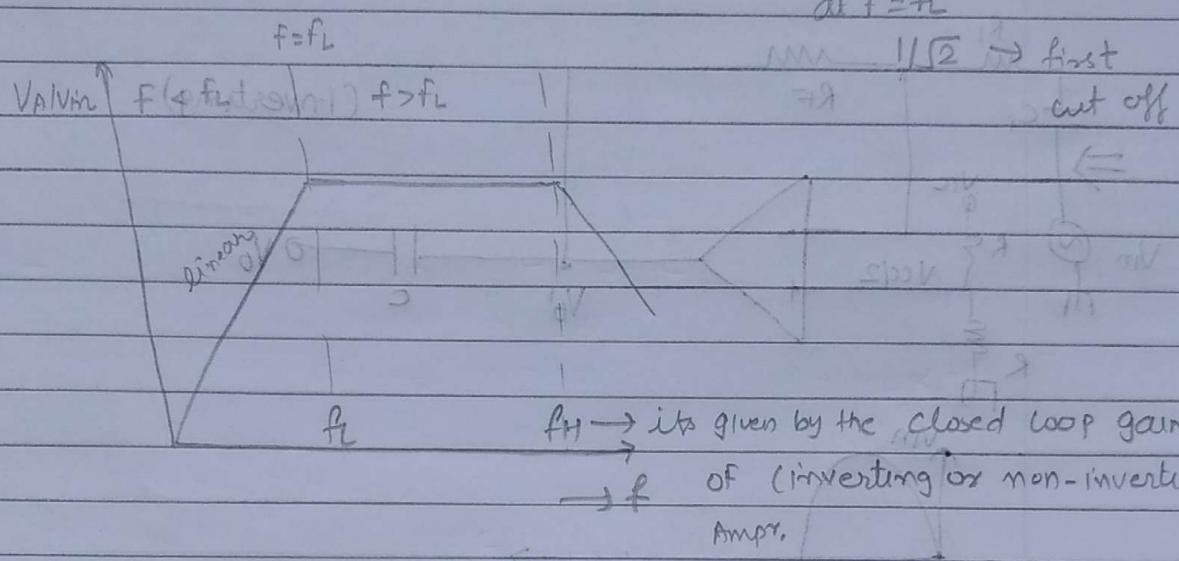

Ex 0

$$R_F = 1k\Omega ; R_I = 100\Omega ; R_o = 50\Omega \therefore C = 0.1\text{HF}$$

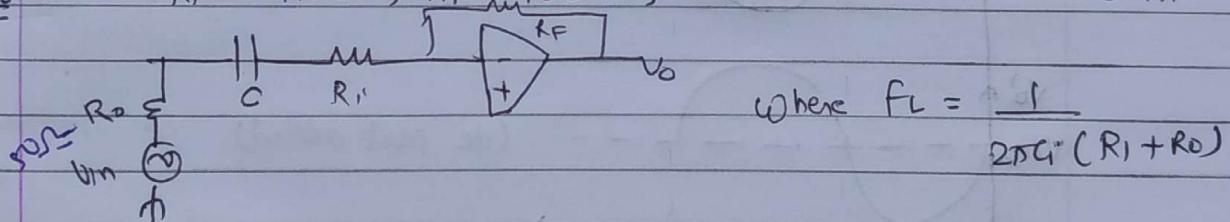

Sol 0

$$f_F = f_0(1 + AB)$$

$$f_L = ?$$

$$V_{GB} = 1\text{MHz}$$

$$f_H = ?$$

$$f_F = \frac{(V_{GB})K}{A_F}$$

$$BW = (?)$$

$$K = \frac{R_I}{R_I + R_F} = \frac{100}{100 + 10} = 0.1$$





$$A_F = -R_F/R_I = 1k/100 = 10$$

$$\text{so}; f_F = \frac{1 \times 10^6 \times 0.1}{10 \times 10}$$


$$= 10 \text{ kHz}$$

$$f_H = f_F(1 + AB)$$
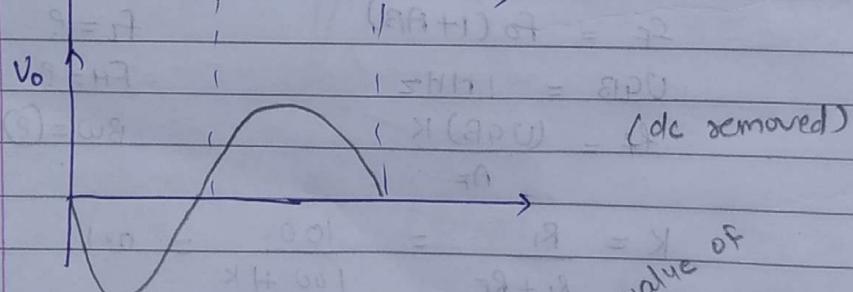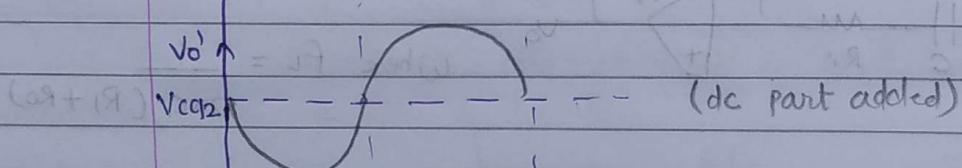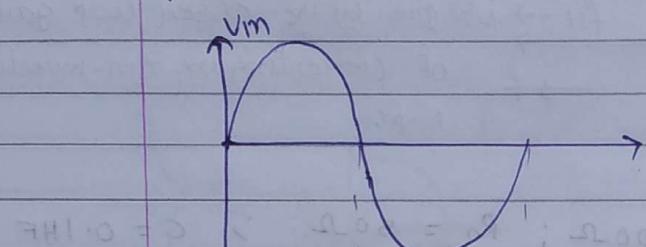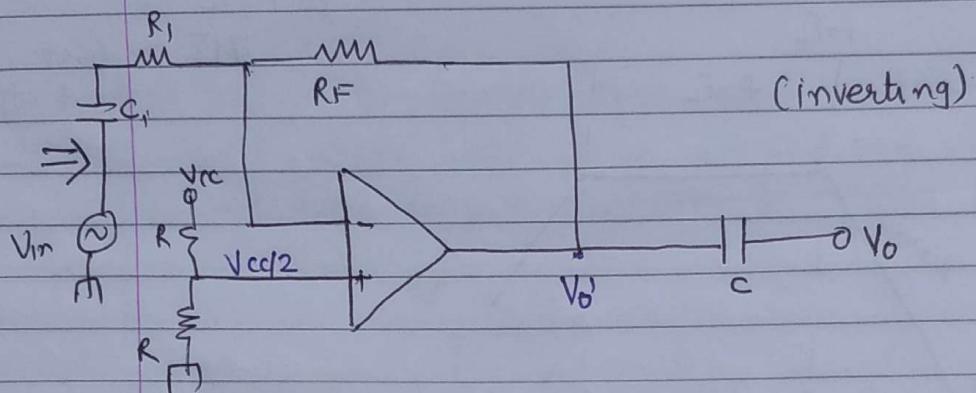
$$f_L = \frac{10^6}{2\pi(0.1)(100 + 50)}$$




non-inverting

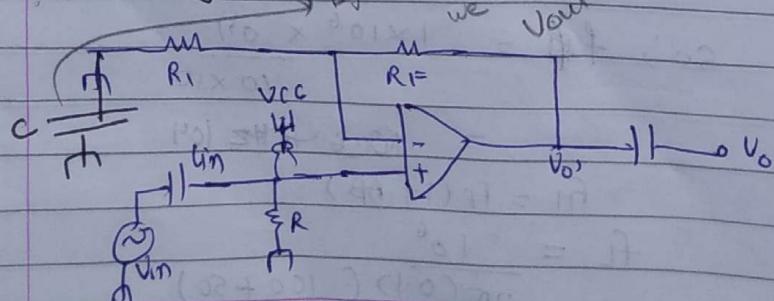




5 NOV 2013

Date _____
Page _____

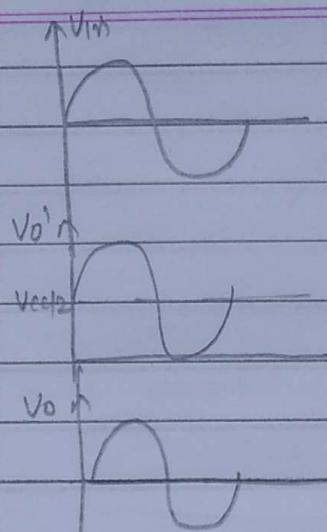


When $V_{in} = 0$

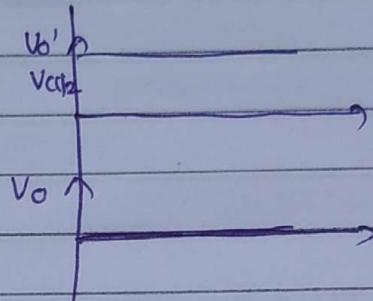

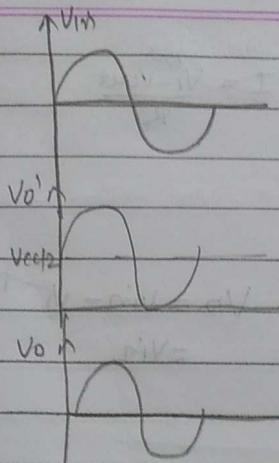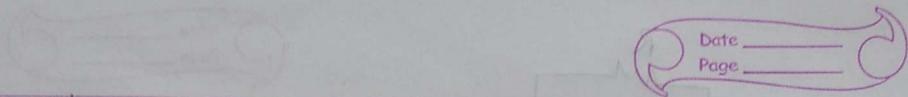


When $V_{in} = 0$

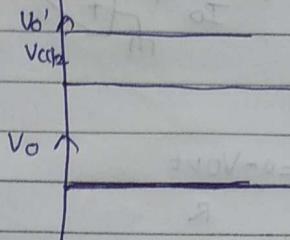

Log Amplifier 8

19-Aug

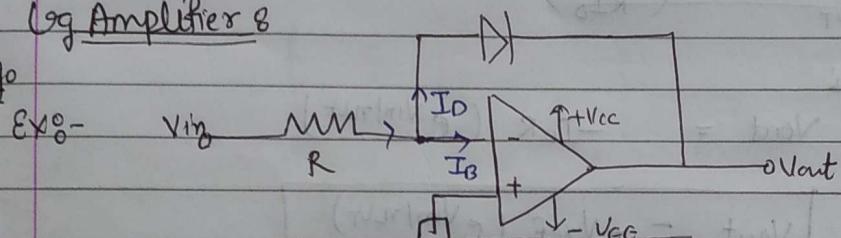

current across
the diode

$$i_d = I_0 (1 + e^{V_D / mV_T})$$

$$m=1 \rightarrow Ge$$

$$m=2 \rightarrow Si$$

$$V_D = 26 \text{ mV}$$

By applying node Kirchhoff's (KCL)

$$\frac{V_{in}}{R} - I_B - I_D = 0$$

$$\frac{V_{in}}{R} = I_0 (e^{V_D / mV_T} - 1) \approx I_0 \cdot e^{V_D / mV_T}$$


$$\frac{V_{in}}{R} = I_0 e^{-V_{out} / mV_T}$$

$$\ln\left(\frac{V_{in}}{R}\right) - \ln I_0 = -\frac{V_{out}}{mV_T}$$

$$V_{out} = mV_T \left[\ln \frac{I_0 R}{V_{in}} \right] \quad \text{- thermal stability}$$

logarithmamp:
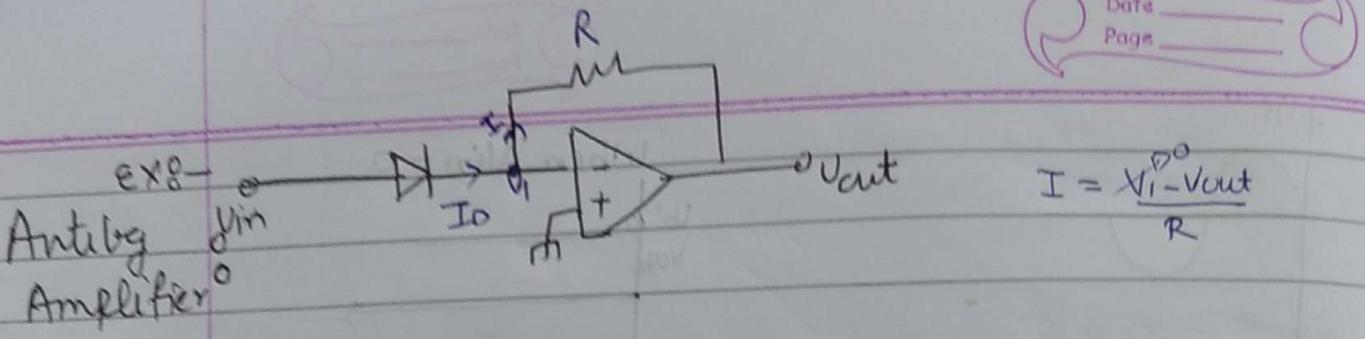
$$V_{out} = mV_T \ln \frac{V_{in}}{V_{ref}}$$



$$I_D = \frac{V_{out}}{R}$$

$$V_D (e^{\frac{V_D}{mVT}} - 1) = -\frac{V_{out}}{R}$$

$$I_D (e^{\frac{V_{in}}{mVT}}) = -\frac{V_{out}}{R}$$

$$\frac{V_{in}}{mVT} = \frac{\ln(V_{out})}{R I_D}$$

$\frac{V_{in}}{mVT}$


$$V_{out} = -I_D R (e^{\frac{V_{in}}{mVT}})$$

antilog amp^{re} $V_{out} = -V_{ref} (e^{\frac{V_{in}}{mVT}})$

Ex8

$$y = A \cdot B$$

"Multiplier"

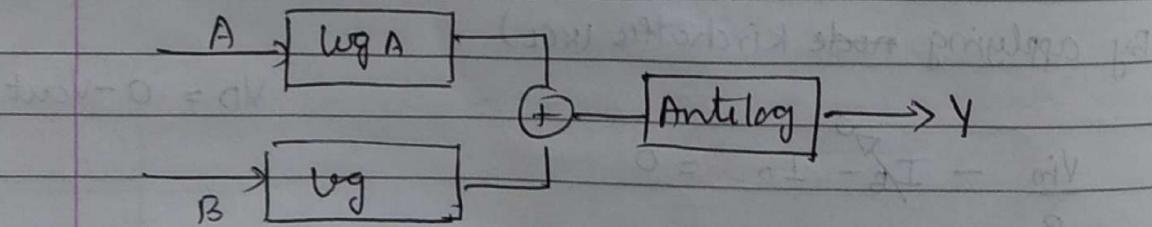


- square root


- square

- temp controller Ckt - instrumentation

- Analog weight scale

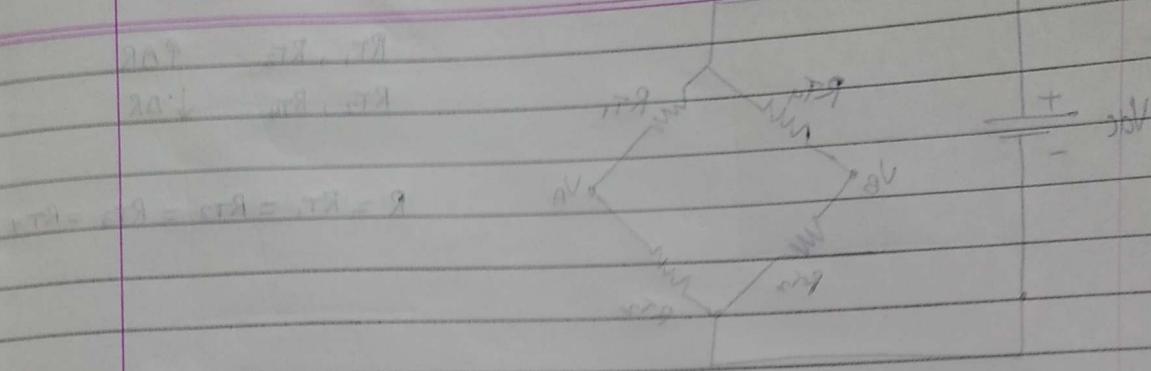

Ex 8-

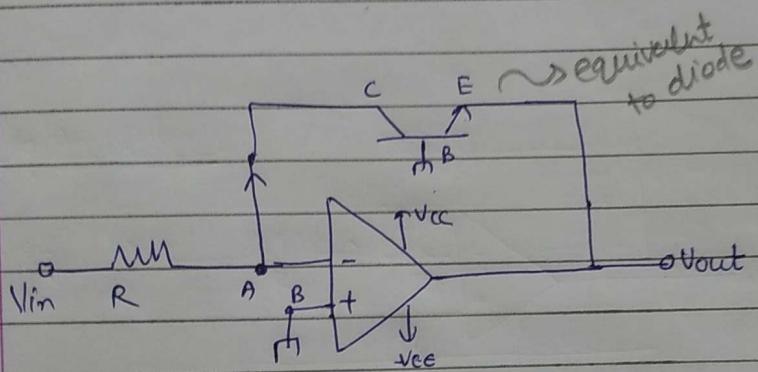


- common base NPN
transistor

$$V_{BE} = 0 - V_{out}$$

$$V_{CE} = V_{in} - V_B$$

$$= 0 - 0 = 0$$

- Log Amp with transistor

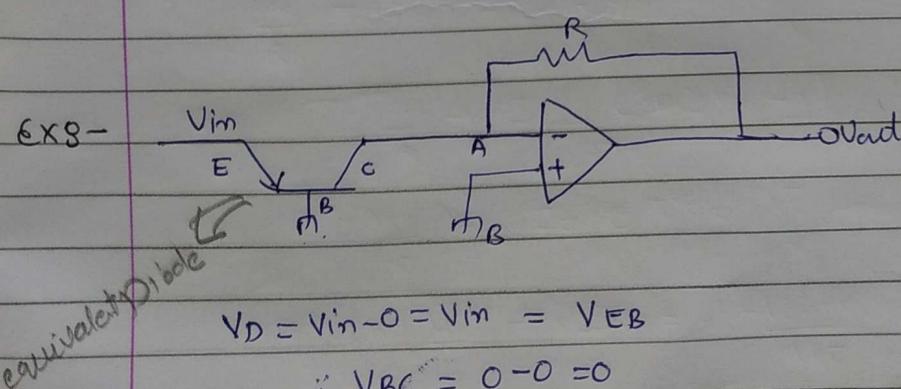

- common base
PNP transistor


- Anti log amp with transisitor

\Rightarrow Analog weight scale; (instrumentation amp)

Date
Page

Po No

260

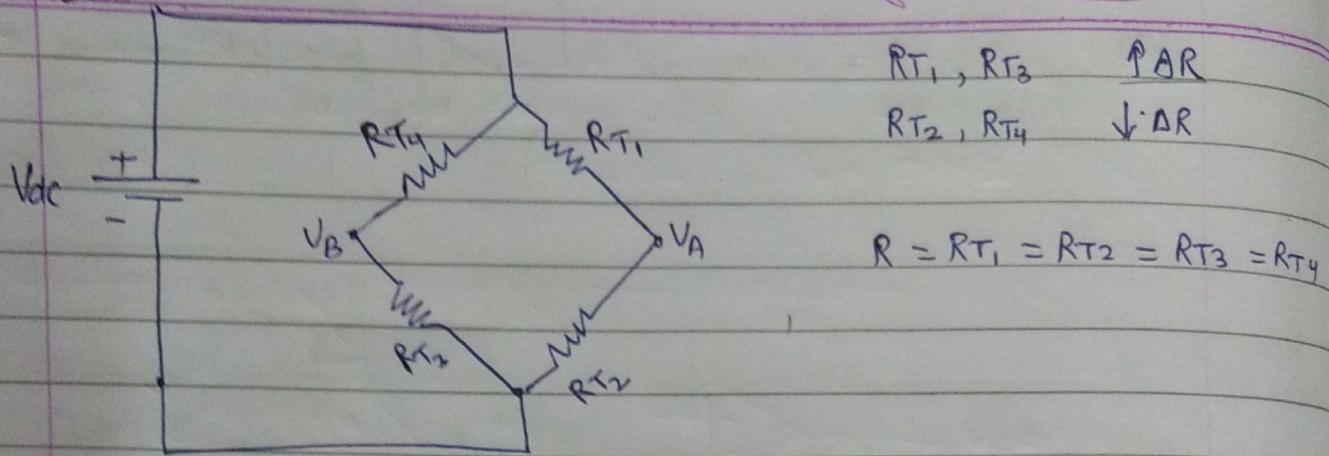


$$V_A = \frac{RT_2 - DR \cdot V_{DC}}{-DR + RT_2 + RT_1 + DR}$$

$$V_B = \frac{RT_3 + AR \cdot V_{DC}}{DR + RT_3 + RT_4 - DR}$$

$$\text{So; } V_{AB} = V_A - V_B \\ = \left(\frac{DR}{R} \right) V_{DC}$$

$$V_{out} = \left[-\frac{RF}{R_1} \right] \cdot V_{AB} \\ = \frac{RF}{R_1} \cdot \frac{DR}{R} \cdot V_{DC}$$

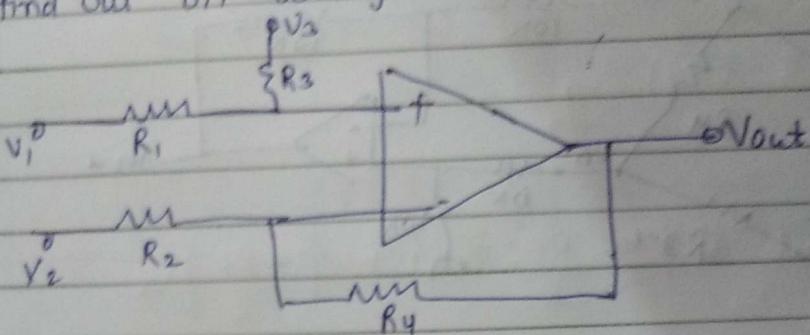Ex 8- for the CKT shown in fig. OIP voltage $V_o = a_1 V_1 + a_2 V_2 + a_3 V_3$ (i) calculate a_1, a_2 & a_3 also (ii) find out OIP voltage if R_4 is short circuit, open circuit and (iii) find out OIP voltage if R_1 is short circuit.



(i) Superposition theorem

$$V_{o1} = \left(\frac{1 + R_4}{R_2} \right) V_1 \times \frac{R_3}{R_3 + R_1} a_1$$

$$V_{o2} = -\frac{R_4}{R_1} V_2 a_2$$

$$V_{o3} = \left(\frac{1 + R_4}{R_2} \right) \frac{R_1}{R_1 + R_3} V_3 a_3$$

$$V_{out} = V_{o1} + V_{o2} + V_{o3}$$

(ii) $R_4 \rightarrow$ short circuit

then $R_4 = 0$

$$V_{out} = V_1 \left(\frac{R_3}{R_3 + R_1} \right) + V_3 \left(\frac{R_1}{R_1 + R_3} \right)$$

$R_4 \rightarrow$ open circuit

$$R_4 = \infty$$

open loop configuration

$$V_{out} = V_{out}$$

(iii)


$R_1 \rightarrow$ short circuit

$$R_1 = 0$$

Ex :- for the ckt. shown in fig calculate o/p voltage

(i) $R_1 = R_2 = R_3 = R_4 = 1\text{K}\Omega$

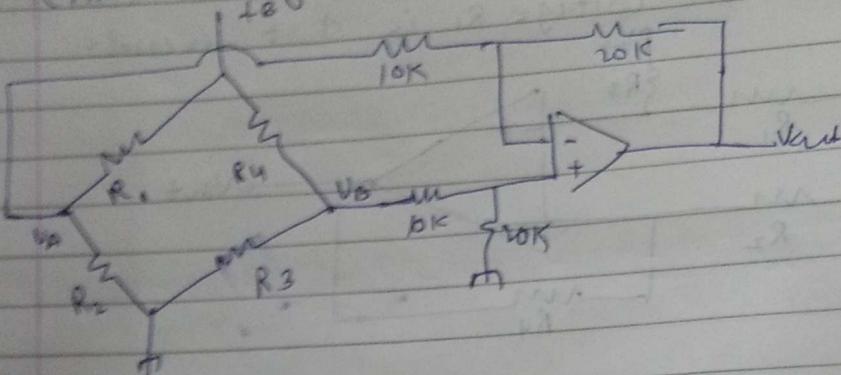(ii) $R_1 = R_2 = R_3 = 2\text{K}\Omega$, $R_4 = 2.2\text{K}\Omega$



Sol: $V_{out} = \frac{-RF}{R_1 + RF} V_A + \left(1 + \frac{RF}{R_1} \right) \times \frac{V_B}{V_A}$

∴ bridge at balance $V_A = V_B = 0$

So, $V_{out} = 0$


(iii) bridge at unbalance

$$V_A = \frac{R_2 \times 8}{R_1 + R_2} = \frac{2 \times 8}{4} = 4$$

$$V_B = \frac{R_3 \times 2}{R_4 + R_3} = \frac{2 \times 2}{2 + 2.2} = 0.9$$

$$V_{out} = -0.54\text{V}$$

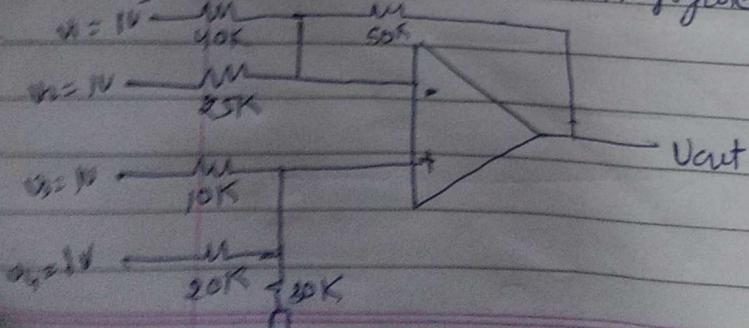Ex :- for the ckt. shown in figure calculate o/p voltage




$$\underline{\text{Soln}} - V_{O1} = \frac{-50}{40} \times (1)$$

$$V_{O2} = \frac{-50}{95} (1)$$

$$V_{O3} = \left(1 + \frac{50}{40 \parallel 25} \right) \left(\frac{30K \parallel 20K}{30K \parallel 20K + 10K} \right) \times (1)$$

$$V_{O4} = \left(1 + \frac{50}{40 \parallel 25} \right) \left(\frac{10K \parallel 30K}{30K \parallel 10K + 20K} \right) \times (1)$$

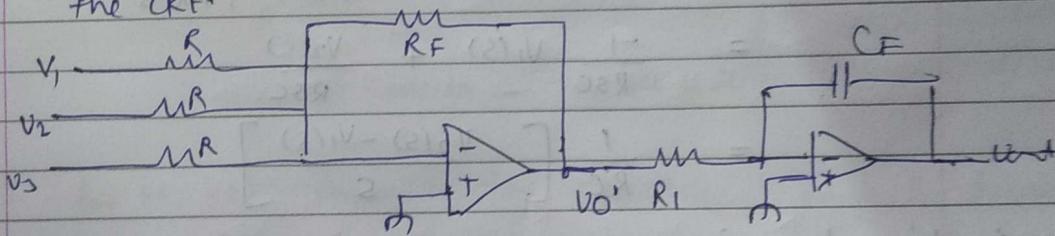Q. Calculate oip voltage V_o also identify two of the ckt.



Soln


$$V_{O'} = \frac{-RF}{R} (V_1 + V_2 + V_3)$$

$$V_{out} = \frac{1}{CF R_1} \int V_{O'}(t) dt$$

$$= \frac{RF}{R_1} \int (V_1 + V_2 + V_3) dt$$

Ex 9-

Identify the func

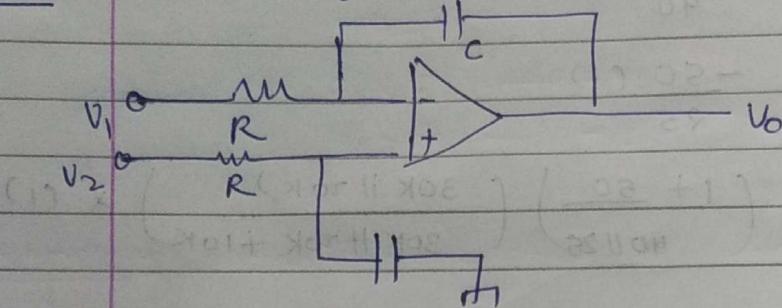

Sol 9

$$V_{out} = -\frac{RF}{R} V_1(s) + \left(1 + \frac{RF}{R}\right) V_x$$

$$= \frac{-1/sC}{R} V_1(s) + \left(1 + \frac{1/sC}{R}\right) \left(\frac{1/sC}{1/sC + R}\right) V_2(s)$$

$$= \frac{-V_1(s)}{RSC} + \left(1 + \frac{1}{RSC}\right) \frac{1}{1 + RSC} V_2(s)$$

$$= \frac{-1}{RSC} V_1(s) + \frac{V_2(s)}{RSC}$$


$$= \frac{1}{RC} \left[\frac{V_2(s) - V_1(s)}{s} \right]$$

in time domain

$$V_{out}(t) = \frac{1}{RC} \int [V_2(t) - V_1(t)] dt$$

Ex 9-

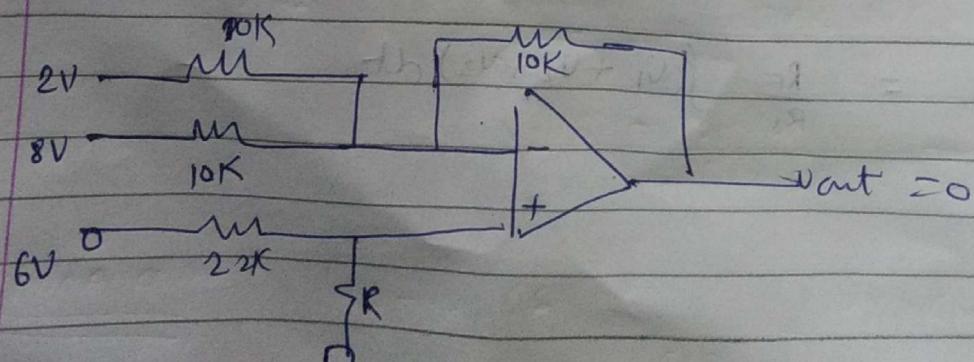Calculate the value of R for the circuit shown in fig. if O/P voltage is 0.



Sol:

$$V_{out} = \frac{-10K}{10K} (2) + \left(\frac{-10}{+10} \right) (8) + \left(1 + \frac{10K}{10K//10K} \right) \cdot \left(\frac{R}{R+22K} \right) \times 6$$

$$\therefore V_{out} = 0$$

$$0 = -10 + \left(1 + \frac{10K}{5K} \right) \left(\frac{R}{R+22K} \right) \times 6$$

$$10 = \frac{R}{(R+22K)} \cdot 18$$


$$\frac{10}{18} = \frac{R}{R+22K}$$

$$10R + 220 = 18R$$

$$8R = 220$$

$$R = 220/8 = 6.62 K\Omega$$

Ex 8- for the ckt. shown in fig. identify which R decide the polarity of O/P voltage.

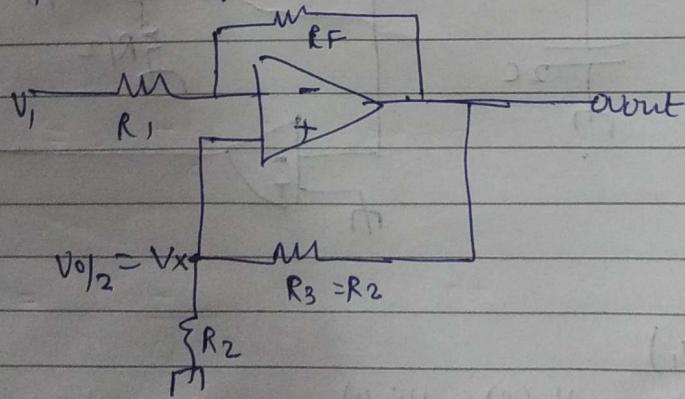

Sol 8

$$V_{out} = -\frac{R_f}{R_1} V_i + \left(1 + \frac{R_f}{R_1} \right) V_x$$


$$\Rightarrow -\frac{R_f}{R_1} V_i + \left(1 + \frac{R_f}{R_1} \right) \frac{R_2}{R_3 + R_2} V_o$$

$$= V_i + 2(V_o - V_i)$$

$$V_o = \frac{2RF}{RF - R_1} V_i$$

$R_1 < RF \rightarrow +ve$
 $R_1 > RF \rightarrow -ve$

Example: identify the fun of figure

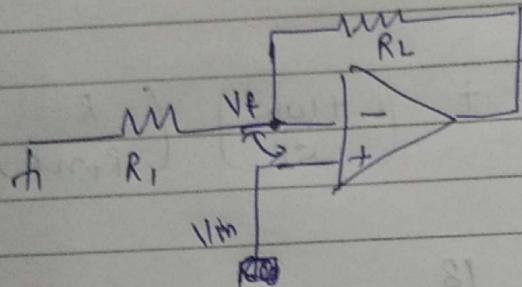


Sol:

$$V_f = V_{in} \quad (\text{virtual ground})$$

$$I_o R_L = V_{in}$$

$$I_o = V_{in} / R_L$$

Voltage \rightarrow current converter

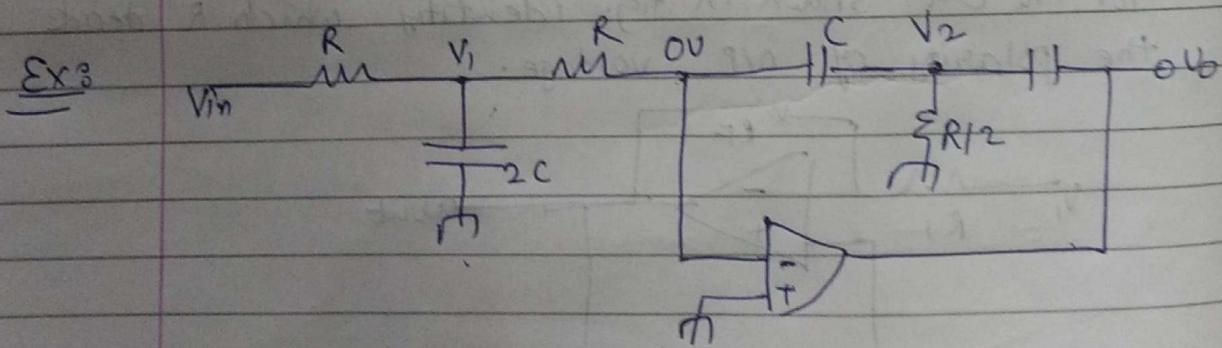


Sol: (Node at V_1)

$$\frac{V_1(s) - V_{in}(s)}{R} + \frac{Q \cdot s \cdot V_1(s)}{C} + \frac{U_L}{R} = 0$$

$$V_1(s) = \frac{V_{in}(s)}{Q(1 + SRC)} \quad (1)$$

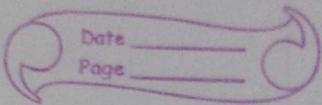node at V_2 $(V_2 - V_o)Cs + V_2 \cdot \frac{U_L}{R_{12}} + V_2 \cdot Cs = 0$



$$V_2(s) = \frac{RCS}{2(1+RCS)} V_0(s)$$

at 0 node

$$V_1(s) = -RCS V_2(s) \quad \text{--- (3)}$$

By ~~hit~~ solving the eq: (1), (2) & (3)


$$\Rightarrow V_0(s) = \frac{-1}{R^2 C^2 s^2} V_{in}(s)$$

(time domain)


$$V(t) = \text{double integration} (s^2 \rightarrow \text{double integral})$$

29-July

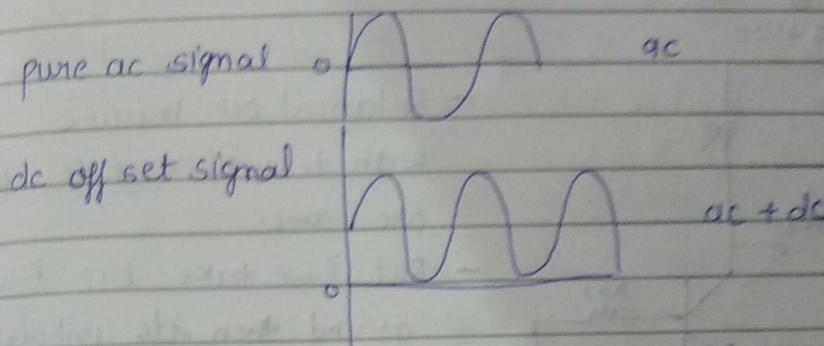⇒ By Using level shifter, we can remove dc from ac



Block Diagram of OP-AMP

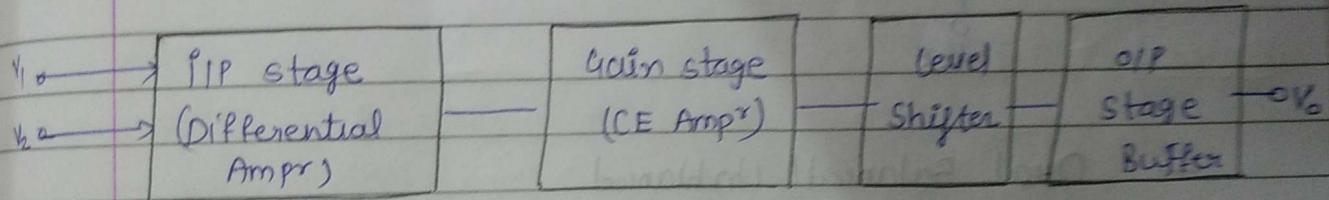

↳ common mode signal $V_{cm} = \frac{V_1 + V_2}{2}$

↳ differential signal $V_{id} = V_1 - V_2$

↳ Differential gain AD is high [10^4 to 10^5]
Common mode gain ACM is low [0]

↳ Common mode regulation ratio (CMRR) = $\frac{AD}{ACM} \approx \infty$


↳ $Z_{in} = (1 \text{ to } 2 M\Omega)$

- In Op-amp we don't have coupling capacitor so op-amp can amplify the ac and dc both.
- ACM is attenuation, not gain
- Op-amp would always amplify the $V_{id} = V_1 - V_2$

$$V_o = V_{id} A_d + V_{cm} A_{cm}$$

$$CMRR = \frac{A_d}{A_{cm}}$$

Differential Amplifier (PN-2)

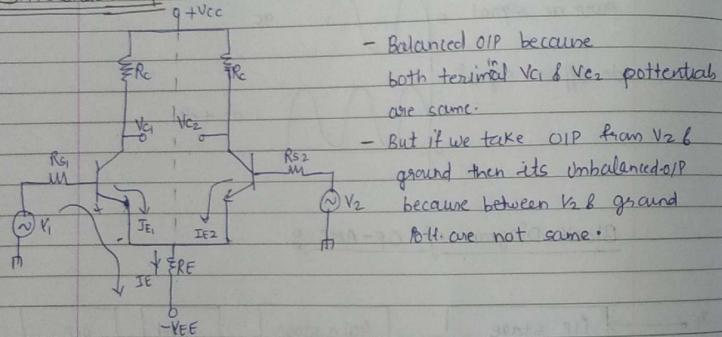

- Dual Balanced / Unbalanced
Single " " "

dc analysis:

I_{EQ}

$$\star V_1 \text{ & } V_2 \text{ ac supply } = 0$$

$$I_{E1} = I_{E2}$$

$$I_E = I_{E1} + I_{E2}$$

$$I_C = I_E (\kappa=1)$$

$$I_E = \beta I_B$$

$$\text{Applying } I_B R_S + V_{BE} + \beta I_E R_E - V_{EE} = 0$$

$$\text{Kirchhoff's Law } I_E R_S + I_E R_E + V_{BE} - V_{EE} = 0$$

Law

$$I_E \left(R_S + \frac{R_E}{\beta} \right) = V_{EE} - V_{BE}$$

$$I_{EQ} = \frac{V_{EE} - V_{BE}}{(R_E + R_S/\beta)}$$

$$V_{CF} = V_C - V_F \\ = V_{CC} - I_C R_C - (V_{BE})$$

$$V_{CE} = V_{CC} + V_{BE} - I_C R_C$$

ac analysis:

- Small signal gain A_d, A_{cm}
all dc value are ground.

(a) for calculating A_d :

$$V_o = A_d V_d + A_{cm} V_{cm}$$

$$V_1 = V_{S1/2} \text{ & } V_2 = -V_{S1/2}$$


$$V_{id} = \frac{V_S + V_S}{2} = V_S$$

$$V_{cm} = 0$$

$$\text{So then } A_d = \frac{V_o}{V_{id}} = \frac{V_o}{V_S}$$


Gain balanced

$$A_{d1} + A_{d2} = A_d = 2 A_{d1}$$

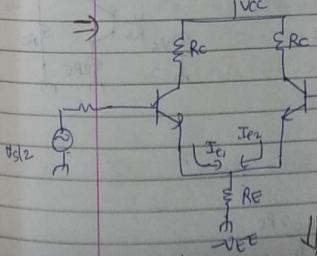

$I_{E1} \downarrow, I_{E2} \uparrow$
so potential drop across $R_E = 0$
so emitter terminal will be ground.

equivalent circuit:

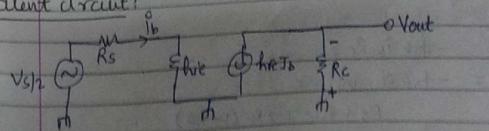

$$V_{out} = - \beta R_L I_B R_C \quad (1)$$

$$V_S = I_B (R_S + \beta R_E) \quad (2)$$

$$\text{So; } V_{out} = - \beta R_L \frac{V_S}{R_S + \beta R_E}$$

$$A_d = \frac{V_{out}}{V_s} = -\frac{h_{FE}R_C}{2(h_{FE} + R_S)}$$


(B) for calculating A_{cm} :

$$V_{id} = 0$$

$$V_1 = V_s; V_2 = V_s \quad V_{CM} = V_s$$


$$V_{out} = V_{CM} A_{cm}$$

$$V_{out} = V_s A_{cm}$$

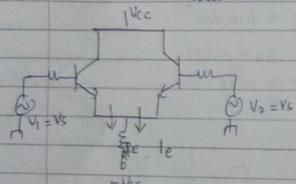

- current is double $2i_e$
so voltage across R_E
 $i_E = 2R_E I_E$

Equivalent circuit:

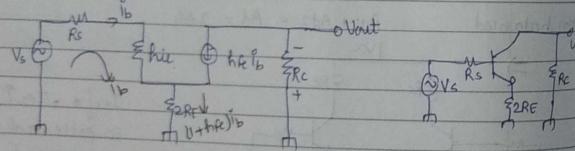

$$i_E = (1 + h_{FE}) i_b$$

$$V_s = (R_S + h_{FE}) i_b + (1 + h_{FE}) i_b \cdot 2R_E$$

$$V_s = [R_S + h_{FE} + 2R_E(1 + h_{FE})] i_b$$

$$V_{out} = -h_{FE} i_b R_C$$

$$= -h_{FE} R_C V_s$$

$$R_S + h_{FE} + 2R_E(1 + h_{FE})$$

$$\frac{V_{out}}{V_s} = A_{cm} = -\frac{h_{FE} R_C}{R_S + h_{FE} + 2R_E(1 + h_{FE})}$$

(C) OIP impedance:

$$Z_{out} = R_C$$

(D) ΩIP impedance:

$$i_b = \frac{V_s}{2(R_S + h_{FE})} \quad \text{from (A)}$$

$$Z_m = 2(R_S + h_{FE})$$

- By removing the second signal $V_2 = 0$
 $V_1 = V_s$

Example 8 Determine diff. amp. OIP voltage when $V_1 = 300 \mu V$

$V_2 = 240 \mu V$; diff. gain = 5000; CMRR = (A) 100 (B) 105
Calculate OIP voltage.

Sol:

$$V_{id} = V_1 - V_2 = 60 \mu V$$

$$V_{cm} = \frac{V_1 + V_2}{2} = 270 \mu V$$

$$(A) \quad CMRR = 100 = \frac{A_d}{A_{cm}}$$

$$\Rightarrow A_{cm} = 50$$

$$\text{So, } V_o = 60 \times 5000 + 270 \times 50$$

$$= 1441 \mu V + 135 \mu V = 1576 \mu V = 0.1576 V$$

$$(B) \quad CMRR = 105 = \frac{A_d}{A_{cm}}$$

$$\Rightarrow A_{cm} = \frac{5000}{105} = 5 \times 10^3 = 5 \times 10^{-2}$$

$$V_o = 60 \times 5000 + 5 \times 10^{-2} \times 270 .$$

$$= 1441 \mu V + 0.35 \mu V = 1441.35 \mu V$$

$$= 0.144135 V$$

Example 8 dual OIP balanced OIP Diff. amp. $f_{id} = 2.8 \text{ kHz}$

$$V_{S1} = 30 \mu V \text{ P-P } 1 \text{ kHz}$$

$$V_{S2} = 40 \mu V \text{ P-P } 1 \text{ kHz}$$

$$V_{CC} = 15 V \quad V_{EE} = -15 V$$

$$R_C = 4.9 K \quad R_E = 6.8 K \quad R_S = 100 \Omega \quad h_{FE} = 100$$

Calculate A_d , A_{cm} , Operating Point, CMRR, V_{out} , R_{in} , R_{out}

Sol 8

$$\text{Operating Point} \quad I_{EQ} = \frac{V_{EE} - V_{BE}}{(R_E + R_S/\beta)} = \frac{15 - 0.9}{(6.8K + 100/100)} = 1.05 \text{ mA}$$

$$I_C \approx I_E \quad V_{CE} = V_{CC} - I_C R_C + V_{BE} = 15 + 0.9 - 4.7K \times 2.3 \text{ mV} = 4.29 \text{ V}$$

$$A_d = -\frac{\beta R_C}{R_S + R_E + 2R_F(1+\beta)} = -\frac{100 \times 4.7K}{2(2.3K + 100)} = -81.03$$

$$A_{cm} = -\frac{\beta R_C}{R_S + R_E + 2R_F(1+\alpha)} = -\frac{100 \times 4.7K}{100 + 2.3K + 2 \times 6.8K(1+10)} = -0.34$$

$$\text{CMRR} = \frac{A_d}{A_{cm}} = 2383.2$$

$$R_{in} = 2(R_S + R_E) = 2(100 + 2.3K) = 5.6 \text{ k}\Omega$$

$$R_{out} = R_C = 4.7K$$

$$V_{out} = A_d V_{id} + V_{cm} A_{cm}$$

$$V_{id} = V_1 - V_2 = 30 \text{ mV}$$

$$V_{cm} = \frac{V_1 + V_2}{2} = 270 \text{ mV}$$

$$V_{out} = 8.4 \text{ V}$$

Example 8 In a Differential amp $R_C = 2.2K$, $R_E = 4.7K$, $R_{in1} = R_{in2} = 50 \Omega$, $\beta = 100$; $V_{cc} = 10 \text{ V}$, $-V_{EE} = -10 \text{ V}$, $V_{BE} = 0.95 \text{ V}$ find out operating point

Sol 8

$$I_{EQ} = \frac{V_{EE} - V_{BE}}{(R_E + R_S/\beta)} = \frac{10 - 0.95}{(4.7K + 50/100)} = 0.98 \text{ mA}$$

$$V_{CE} = V_{CC} + V_{BE} - I_C R_C = 10 + 0.9 - (0.98 \times 2.2) = 8.54 \text{ V}$$

Example 8 P/P Voltages $V_1 = 300 \text{ mV}$, $V_2 = 240 \text{ mV}$

Diffr gain is 3000 and CMRR is 10^3 find V_{out} :

$$V_d = V_1 - V_2 = 60 \text{ mV}$$

$$V_{cm} = \frac{V_1 + V_2}{2} = 270 \text{ mV}$$

$$\text{CMRR} = \frac{A_d}{A_{cm}}$$

$$\Rightarrow A_{cm} = \frac{3000}{10^3} = 3$$

$$V_{out} = V_d A_d + V_{cm} A_{cm} = 60 \times 3000 + 270 \times 3 = 0.18 \text{ V}$$

$$\text{B) } \Rightarrow A_{cm} = \frac{3000}{10^4} = 0.3$$

$$V_{out} = 60 \times 3000 + 0.3 \times 270 = 0.18 \text{ V}$$

Improvement in CMRR:



$$\text{CMRR} = \frac{A_d}{A_{cm}}$$

$$A_{d1} = -\frac{R_E R_C}{2(R_S + R_U)}$$


$$A_{d2} = -\frac{R_E R_C}{R_S + R_U + 2R_E(1 + A_{d1})}$$

$$CMRR = \frac{R_S + R_U + 2R_E(1 + A_{d1})}{2(R_S + R_U)}$$

100 dB $\Rightarrow 20 \log 10^5$

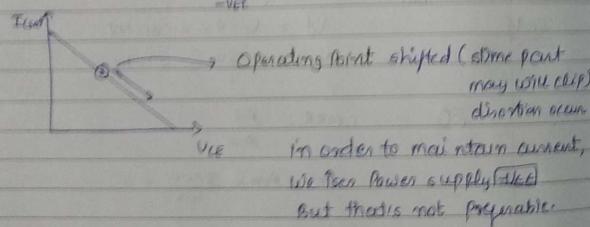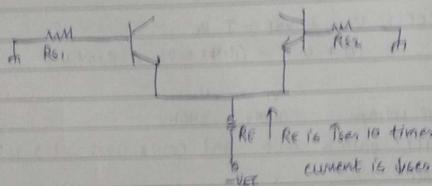

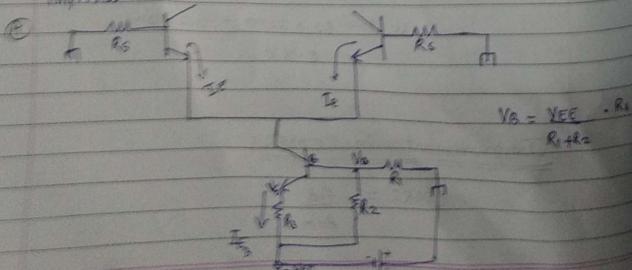- So we change R_E with active resistor "constant current source" current mirror this improves CMRR.
- By changing the R_E , I_E is not change, I_{BE} is lesser, then CMRR improves.




$$V_B = V_{EE} - \frac{R_S}{R_S + R_U} R_U$$

19-Aug

To avoid effect of T_{ceo} in current due to temp., diodes are added instead of resistors R_S .

(6)

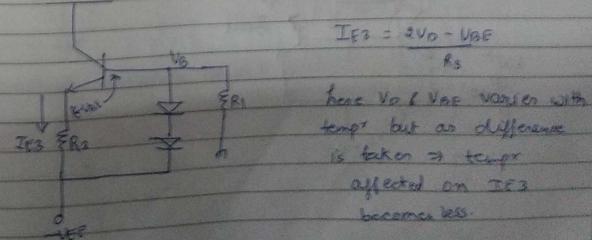

$$I_{E3} = \frac{2V_0 - V_{BE}}{R_S}$$

here V_0 & V_{BE} varies with temp. but as difference is taken \Rightarrow temp. affected on I_{E3} becomes less.

Techniques used for controlling current size due to temp
is called temp compensation.

Date _____
Page _____


$$V_B = -V_{EE} + 2V_D$$

$$V_E = V_B - V_{BE}$$


$$= -V_{EE} + 2V_D - V_{BE}$$

$$I_{EB} = \frac{V_E + V_{EE}}{R_3} = \frac{-V_{EE} + 2V_D - V_{BE} + V_{EE}}{R_3}$$

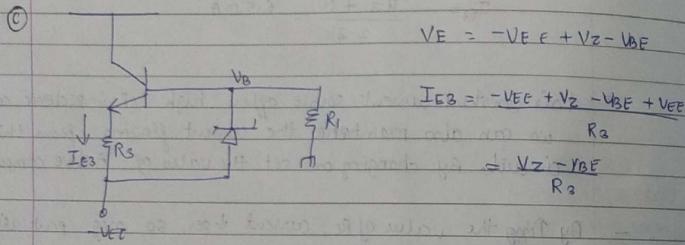⇒ instead of 2 diodes, a zener diode can also be used





Current Mirror:

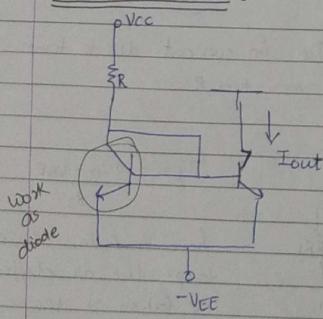


Used for biasing purpose.

Level Shifters: (IN 42)

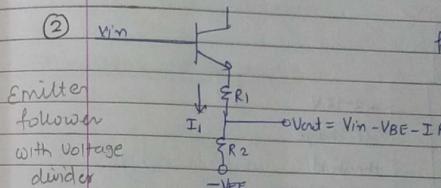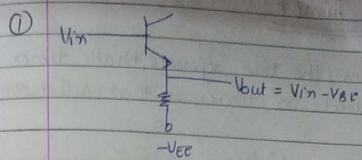


∴ we use active resistors.

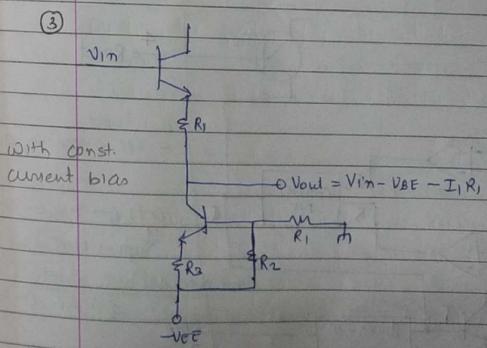

(4) Completely removes dc offset.


- thermal runaway heat sinks

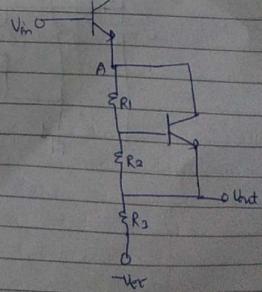


555 Timer

- a device which gives the time reference, that is timer.
- 3 resistors of $5\text{ k}\Omega$ is used in timer, so that's called as 555 timer.
- they are used for voltage divider.

pin diagram:

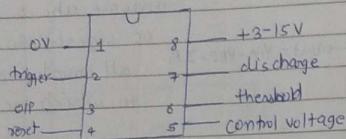


Monostable:

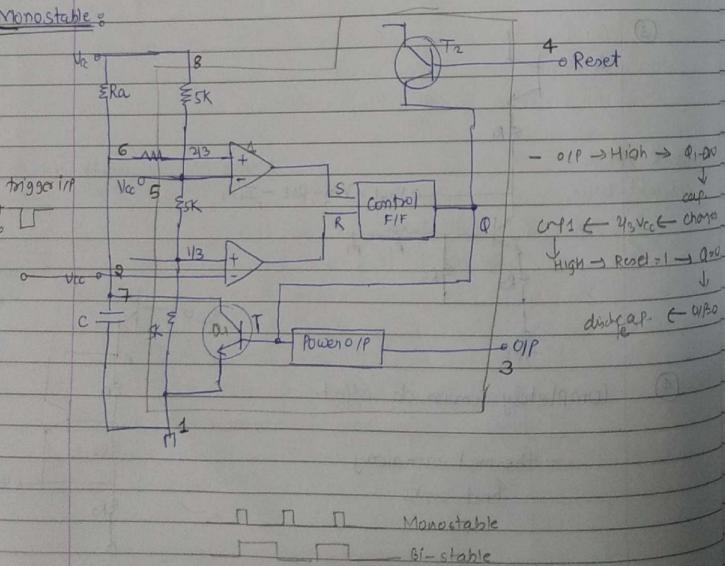

Application:

- Random flashers
- A light dimmer
- A car tachometer
- traffic lights
- infrared remote control

Monostable O/P voltages:

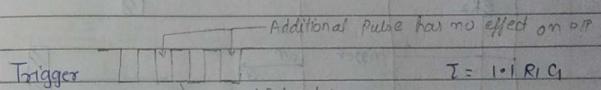

$$T = 1.1 R_1 C_1$$

Cap. voltage

O/P


Reset

A Reset Pulse applied during timing interval terminates the O/P pulse

9-Sep-0


Astable multivibrator:

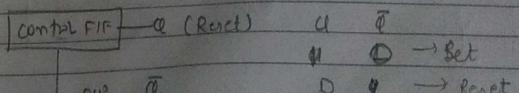- cap. is charged $C(R_a + R_b) \rightarrow$ charging time $1/2 V_{cc} \rightarrow 2/3 V_{cc}$
- at starting $V_c = \frac{1}{2} V_{cc} \rightarrow$ op-amp (2) \rightarrow control FF (0)
- high = O/P \leftarrow transistor $\leftarrow T_1 (0)$
- slow OFF



Set $\rightarrow 1$

Reset $\rightarrow 0$

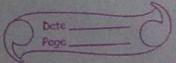

When $Q = 1, V_{cc} = 0$; $T_1 \rightarrow$ cap discharge, set

$T_2 \rightarrow Q = 0, V_{cc} = 1 \rightarrow T_2 \rightarrow$ cap open, capacitor charge

$V_C \approx 12 \text{ Vcc}$

$$T_p = 1.1 R_2 C$$


Random flashers

A light dimmer

Infrared remote control

Expt 1: Monostable 555 Timer is required to produce a time delay within a slot of a 10Hz timing cap is used. Calculate the value of the resistor required to produce a min off time delay of 800ms.

$$R = \frac{T}{1.1 \times f} = \frac{800 \times 10^{-3}}{1.1 \times 10 \times 10^{-3}} =$$

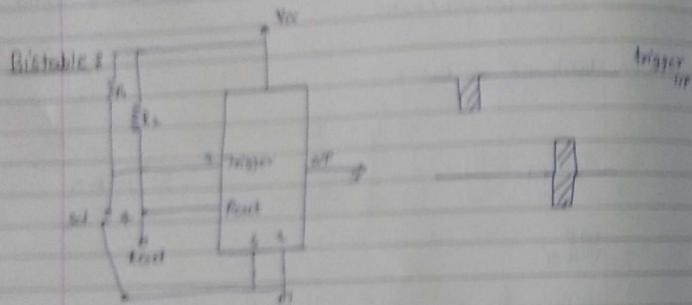

Expt 2: Design a square wave gen, by using astable multivibrator, when $f = 10\text{kHz}$ & duty cycle 50%.

Astable multivibrator

$$\tau_1 = 0.69 (R_A + R_B)C$$

$$\tau_2 = 0.69 R_B C$$

$$T = 0.69 (R_A + R_B)C$$

$$f_0 = 1/T = 1.45 (R_A + R_B)C$$


$$\therefore \text{duty cycle} = \frac{\tau_1}{T} = \frac{R_A + R_B}{R_A + 2R_B} \times 100$$

Current Mirror (Q18)

The circuit in which the off current is forced to equal the on current is said to be a current mirror circuit.

$$\text{In Gate} \rightarrow \text{Current mirror} \leftarrow -T_{\text{sink}}$$

$$I_{\text{in}} = I_{\text{sink}}$$

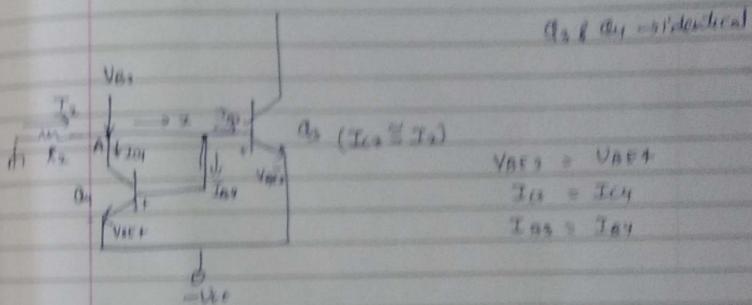

$$\text{at node A}, \quad I_2 = I_3 + I_{D4} \\ = I_{C3} + I_{B2} + I_{D4} = I_{C3} + 2I_{D3} \\ = I_{C3} + 2 \left(\frac{I_{C3}}{\beta_{DC}} \right)$$

$$I_2 = I_{C3} \left[1 + \frac{2}{\beta_{DC}} \right] \quad \text{is very low}$$

$$I_2 \approx I_{C3}$$

Kirchoff's voltage law's

$$-I_2 R_2 - V_{BE3} + V_{EE} = 0$$

$$I_2 = \frac{V_{EE} - V_{BE}}{R_2}$$

* for satisfactory operation of the circuit, two identical transistors are necessary.